

CSE261: Computer Architecture

10. Processor (3): Multicycle Implementation

Seongil Wi

HW2 will be Released Soon!


2



Implementing single-cycle datapath and control

Recap: Datapath with Control


3

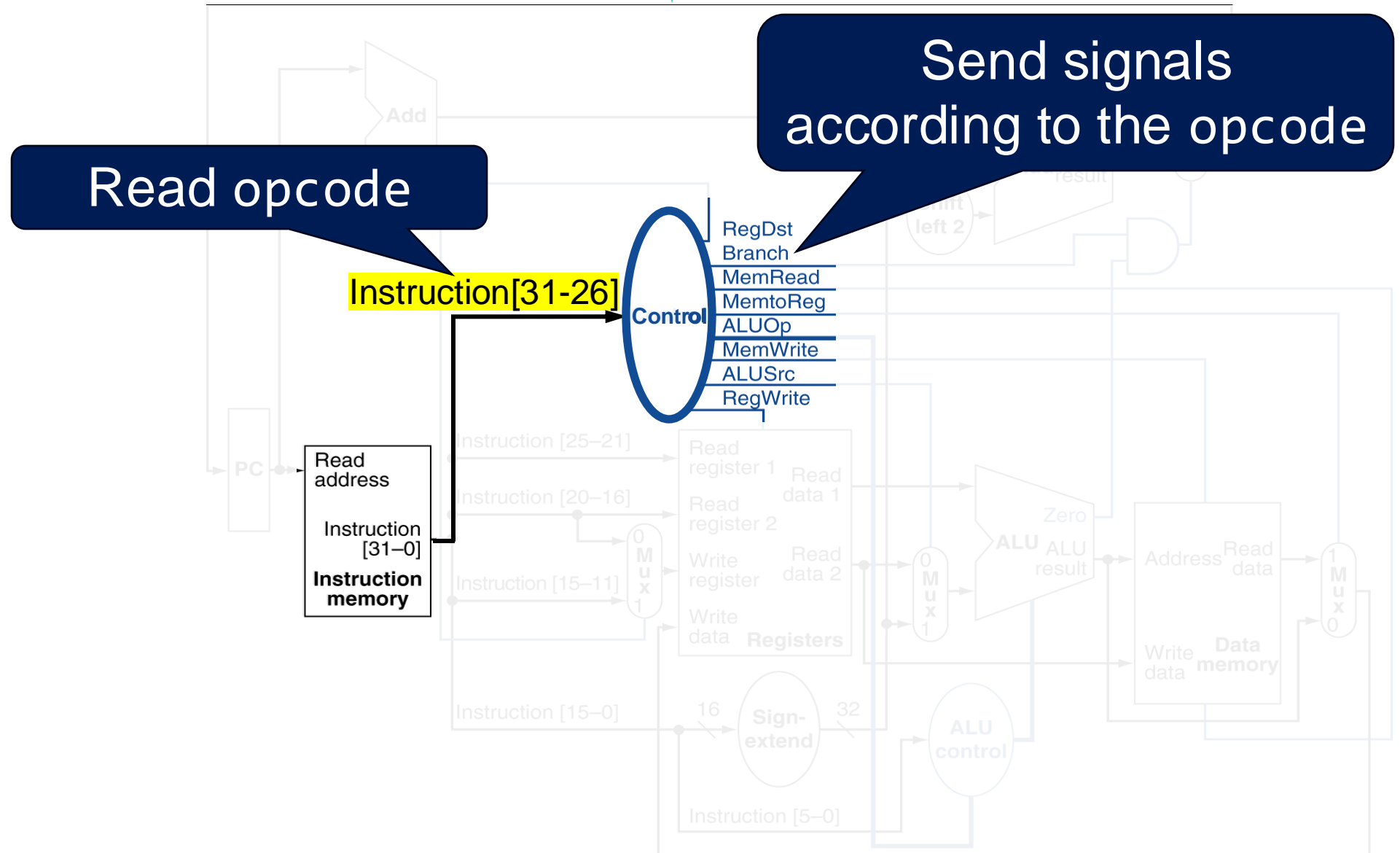

Recap: Introduction to ALU Control


- The ALU operation signals must be provided differently based on the instruction

 Arithmetic / Logic
Instructions
(R-format)




Depending on the
instruction

lw, sw
(I-format)

 

Addition


beq
(I-format)

 

Subtraction


Recap: Introduction to ALU Control

 - The ALU operation signals must be provided differently based on the instruction



Recap: Single Cycle Implementation


6

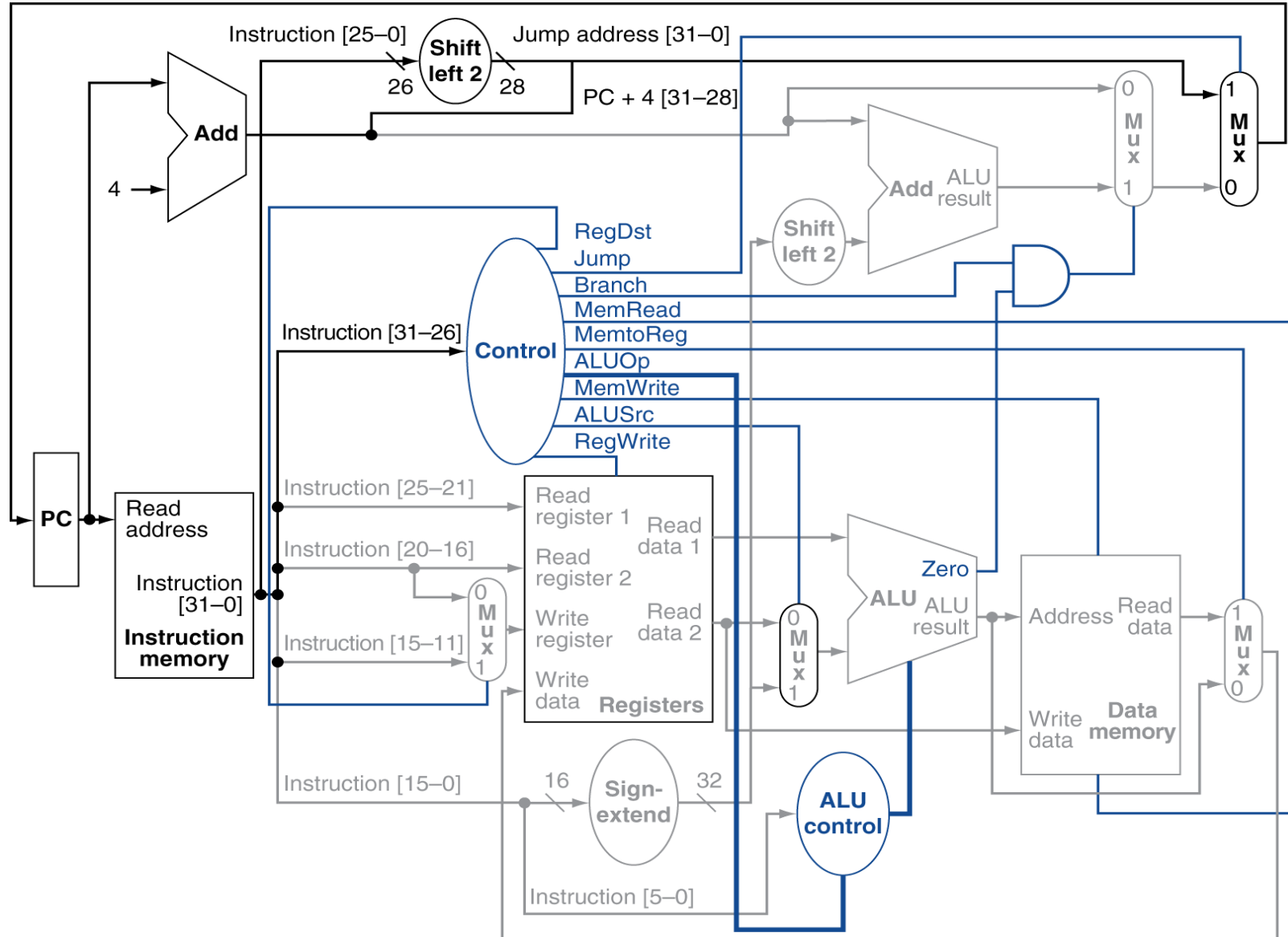

Recap: Single Cycle Datapath

We have considered a ***single clock cycle datapath***

 
- Each instruction is executed in one clock cycle in the CPU



Let's look at the detailed scenario

Recap: Single Cycle Datapath

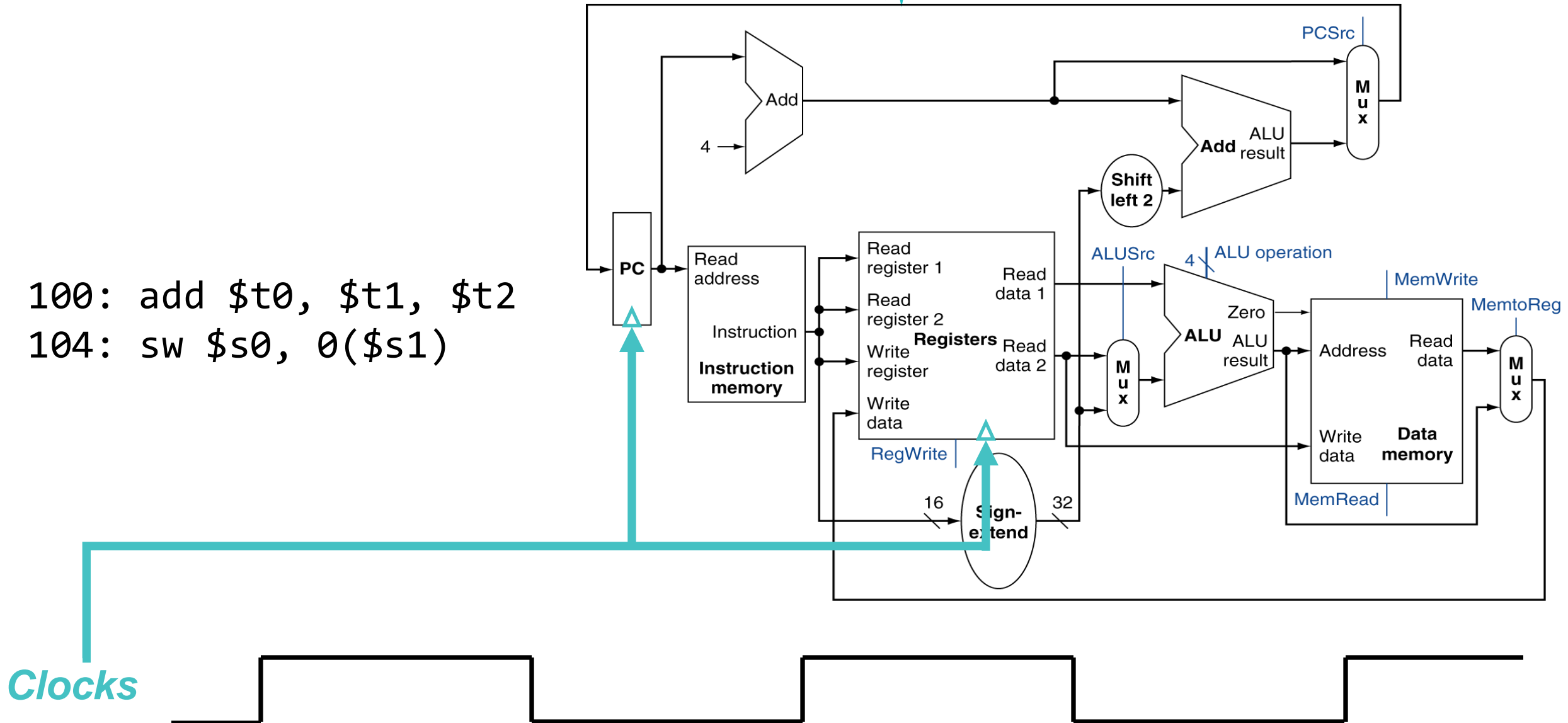
100: add \$t0, \$t1, \$t2
104: sw \$s0, 0(\$s1)



(Before Execution) `add $t0, $t1, $t2`

9

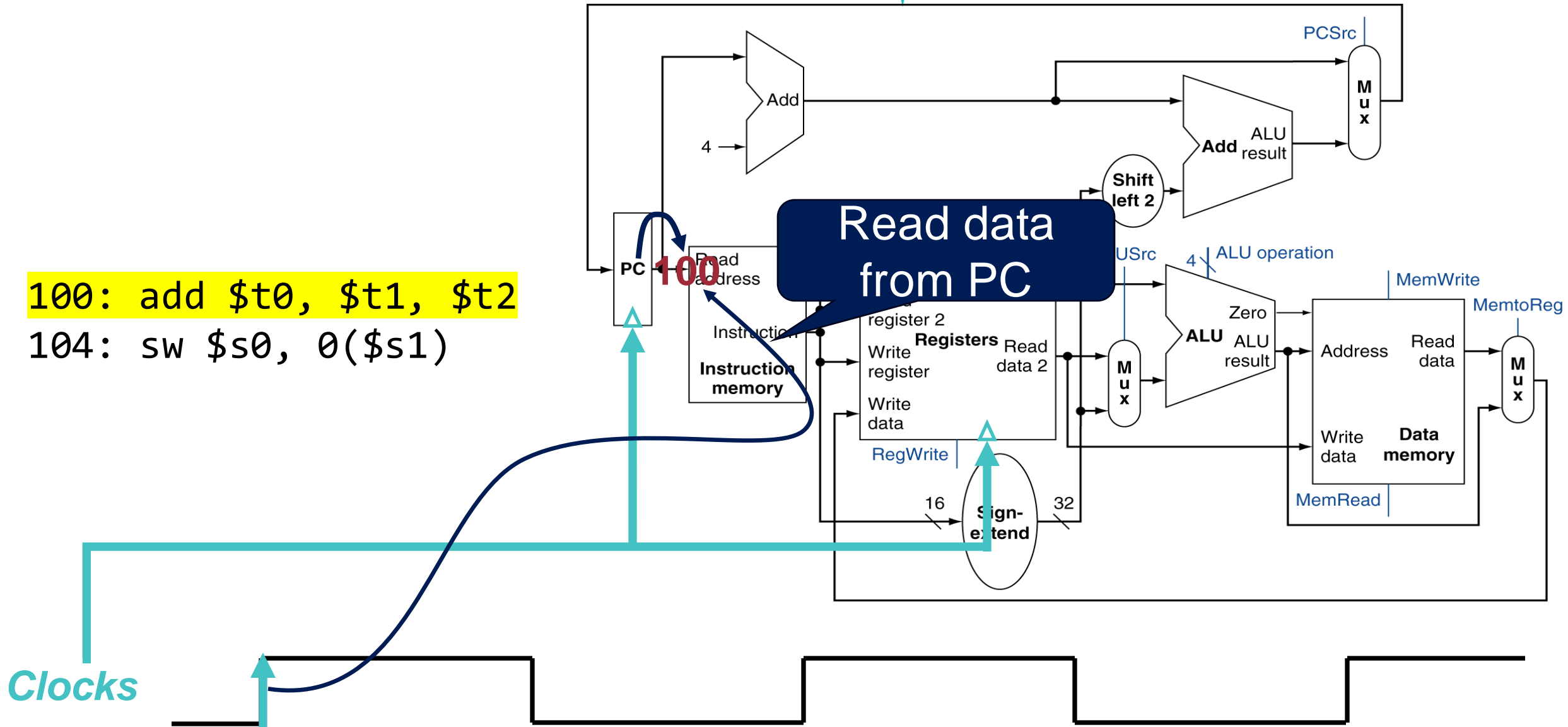100: `add $t0, $t1, $t2`
104: `sw $s0, 0($s1)`




(Execution) add \$t0, \$t1, \$t2


```
100: add $t0, $t1, $t2
104: sw $s0, 0($s1)
```

Wait until all computations
in the combinational circuit
have settled down

Clocks

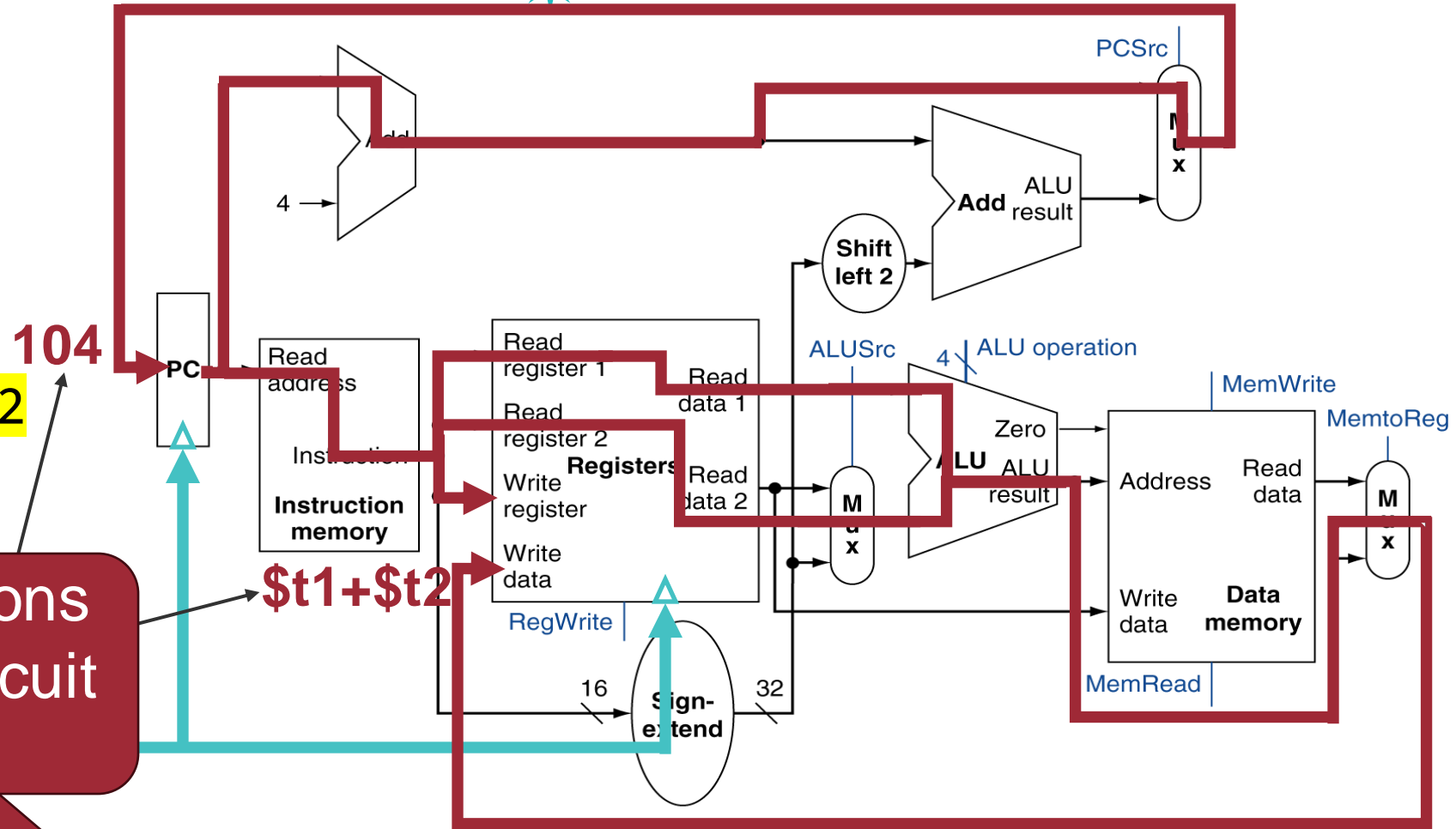


(Before Execution) `sw $s0, 0($s1)`

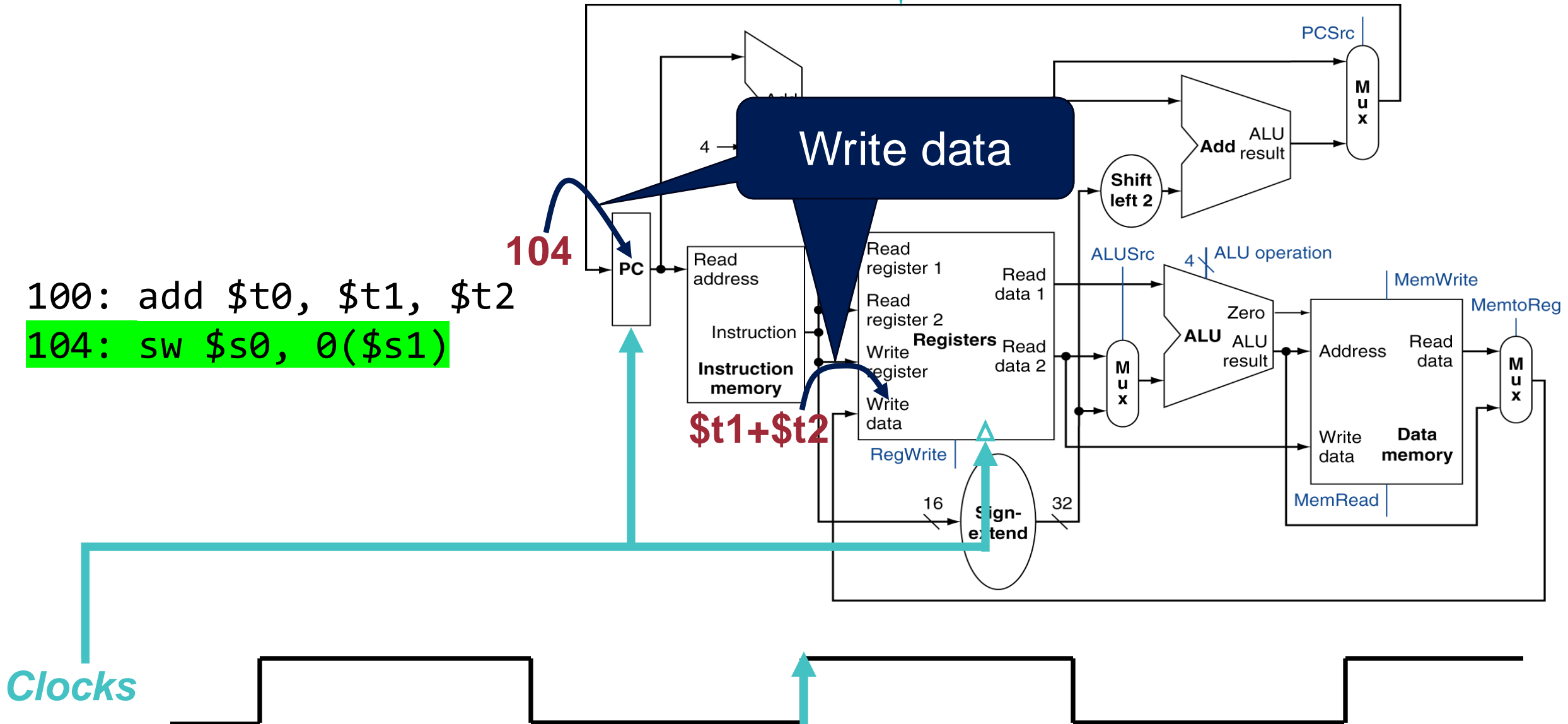

Recap: Critical Path

12

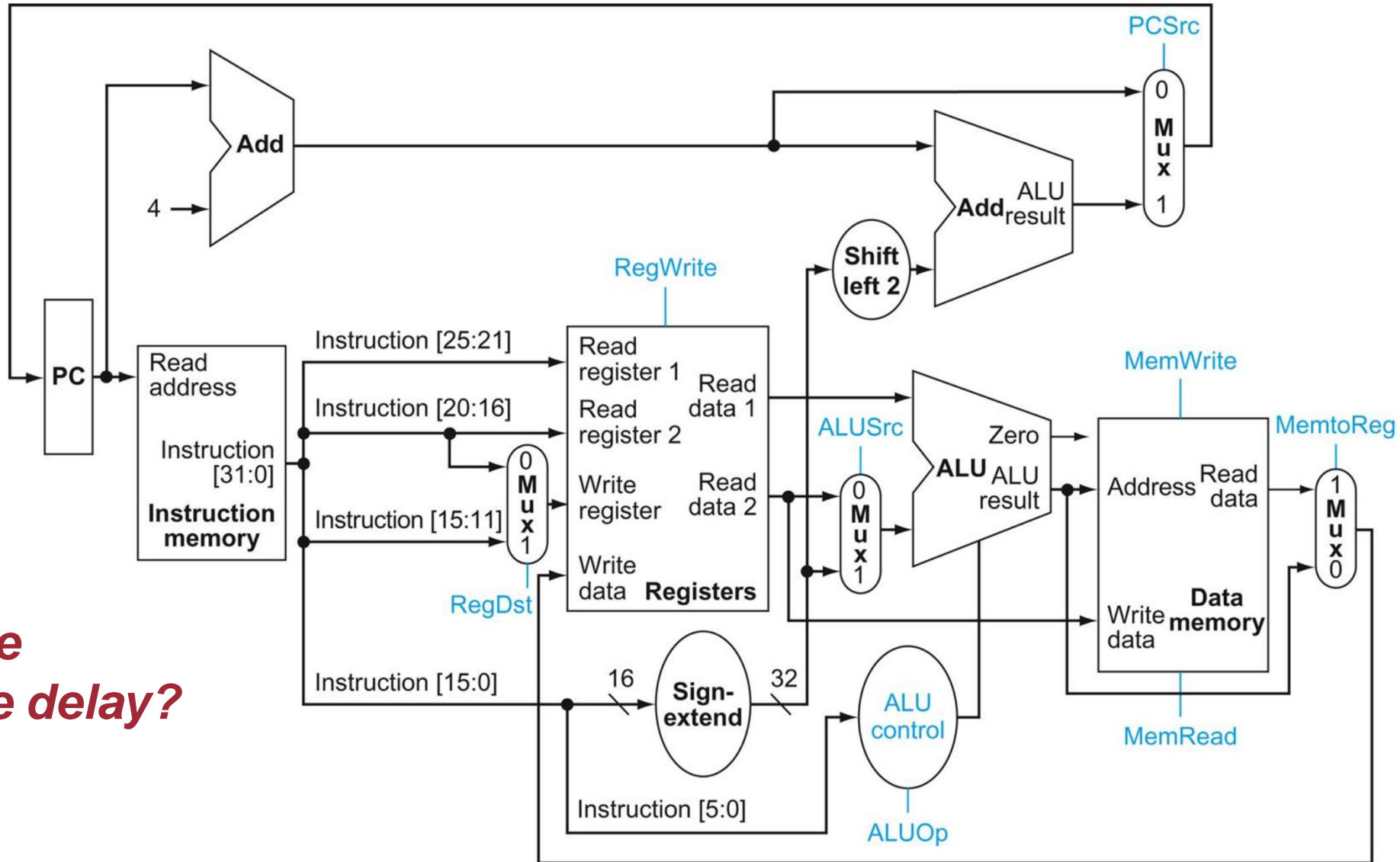


What is the worst case delay?

Recap: Critical Path

13



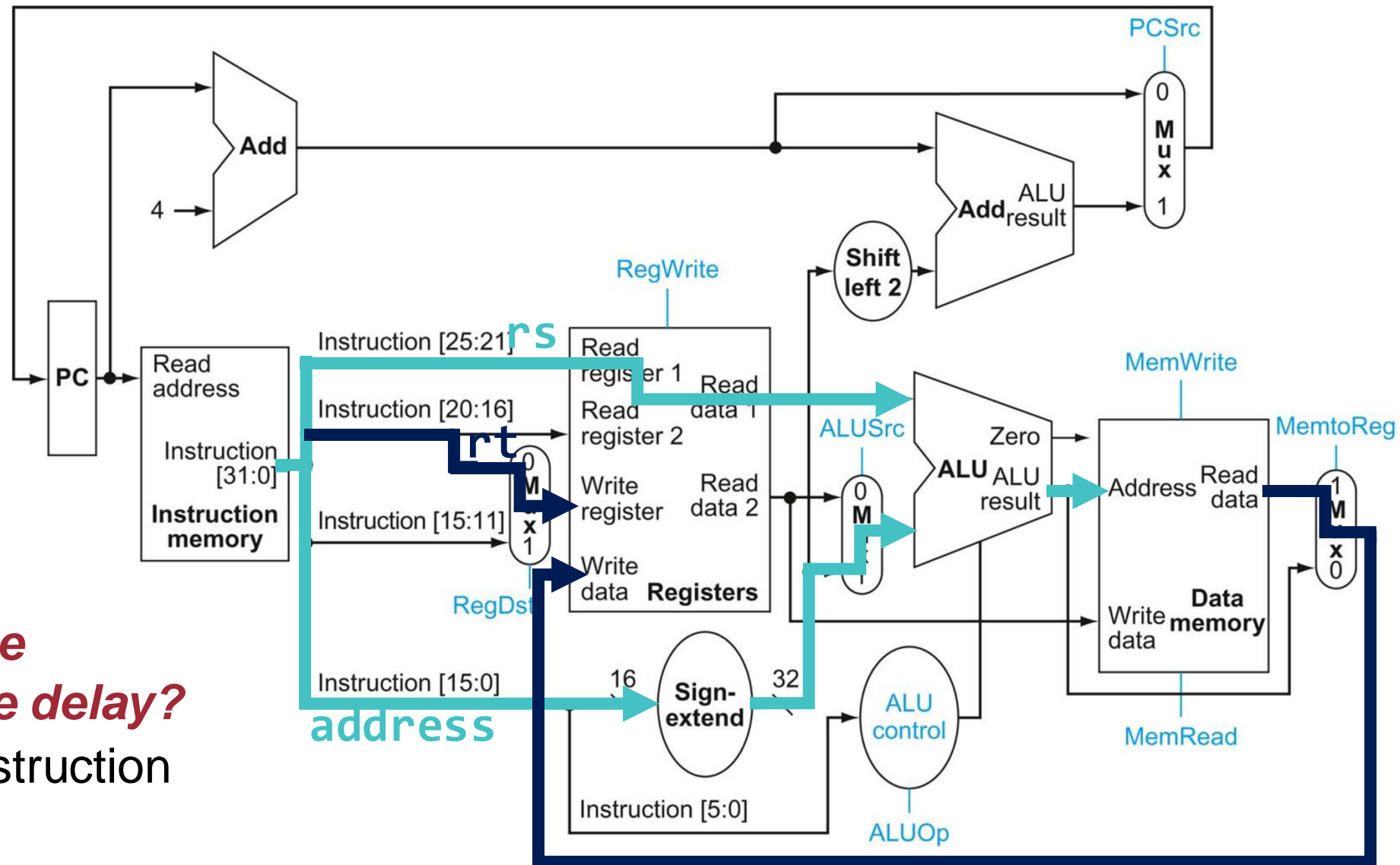What is the worst case delay?
lw instruction



Recap: Critical Path

- Calculate cycle time assuming negligible delays except:
 - Memory access (200ps), ALU (100ps), Register access (50ps)

Instruction	Functional units used by the instruction class					
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back	
R-type	200ps	50ps	100ps		50ps	➔ 400ps
Load word	200ps	50ps	100ps	200ps	50ps	➔ 600ps
Store word	200ps	50ps	100ps	200ps		➔ 550ps
Conditional Branch	200ps	50ps	100ps			➔ 350ps
Jump	200ps					➔ 200ps

Discussion Points (1): Critical Path

Critical path!

The clock cycle time (period) with single clock will be determined by the longest instruction, which is 600ps

		decode	Execution	Access	Write-back	
R-type	200ps	50ps	100ps		50ps	→ 400ps
Load word	200ps	50ps	100ps	200ps	50ps	→ 600ps
Store word	200ps	50ps	100ps	200ps		→ 550ps
Conditional Branch	200ps	50ps	100ps			→ 350ps
Jump	200ps					→ 200ps

Limitation of a Single-Cycle Datapath

- Clock Cycle Time = 600ps

Even though it could finish early, it has to wait for 600ps

Instruction	Functional units used by the instruction				
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back
R-type	200ps	50ps	100ps		50ps
Load word	200ps	50ps	100ps	200ps	50ps
Store word	200ps	50ps	100ps	200ps	
Conditional Branch	200ps	50ps	100ps		
Jump	200ps				

Limitation of a Single-Cycle Datapath

- Clock Cycle Time = 600ps

Even though it could finish early, it has to wait for 600ps


Instruction	Functional units used by the instruction				
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back
R-type	200ps	50ps	100ps		50ps
Load word	200ps	50ps	100ps	200ps	50ps
Store word	200ps	50ps	100ps	200ps	

Why a Single-Cycle Implementation is Not Used Today?

Although the CPI is 1, the overall performance of a single-cycle implementation is likely to be poor, since the clock cycle is too long.

Another Disadvantage of Single-Cycle Implementation

19

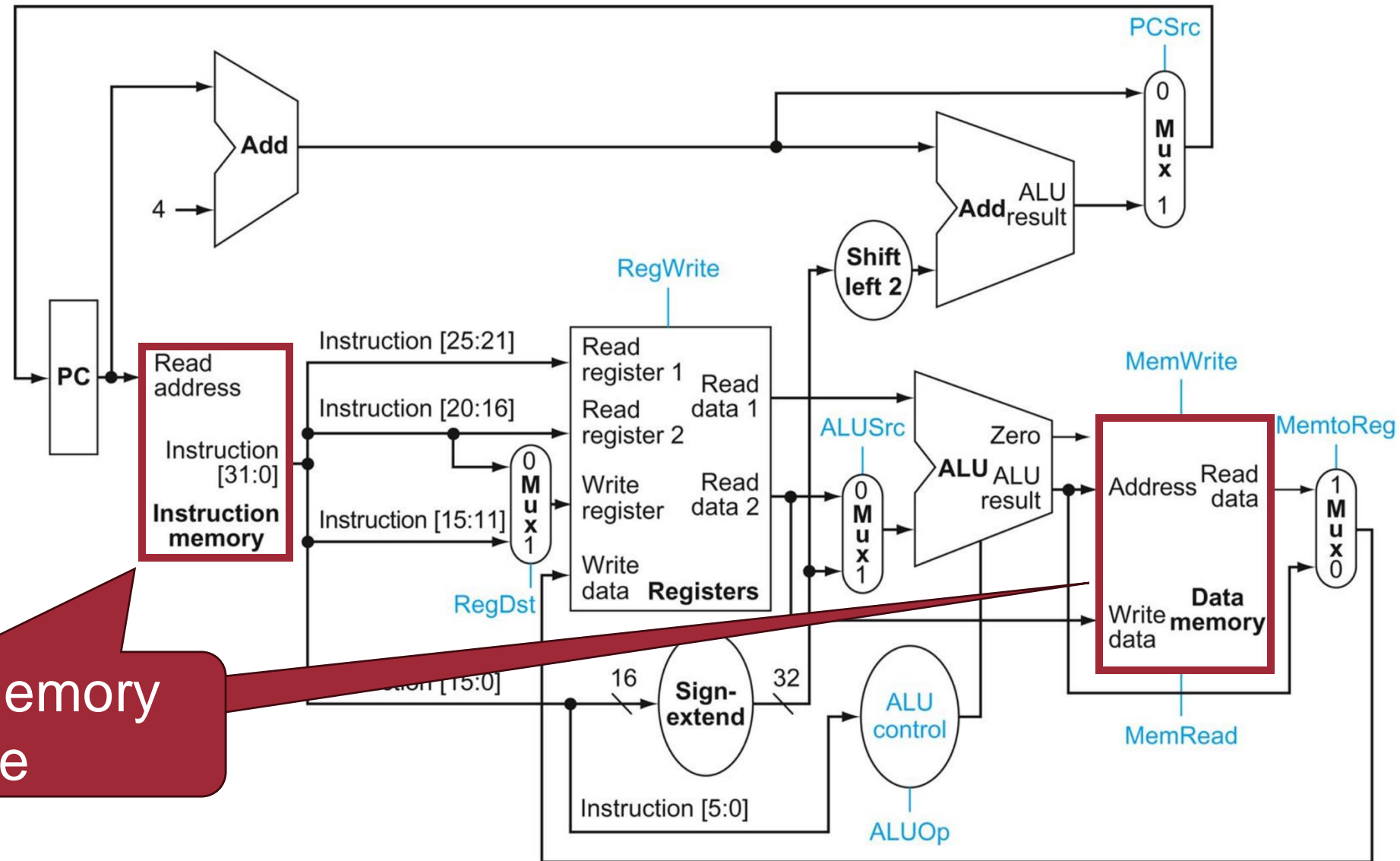

Redundant memory hardware

How can we address this issue?

Single-Cycle
Implementation




**Multicycle
Implementation**

Today's topic


Multicycle Implementation: Intuition

 - An instruction is executed in multiple clock cycles



Multicycle Implementation: Intuition

 
- An instruction is executed in multiple clock cycles



Multicycle Implementation: Intuition

- An instruction is executed in multiple clock cycles

 
```
lw $2, 4($1)  
j ELSE  
beq $2, $3, ELSE
```



Multicycle Implementation: Intuition

- An instruction is executed in multiple clock cycles

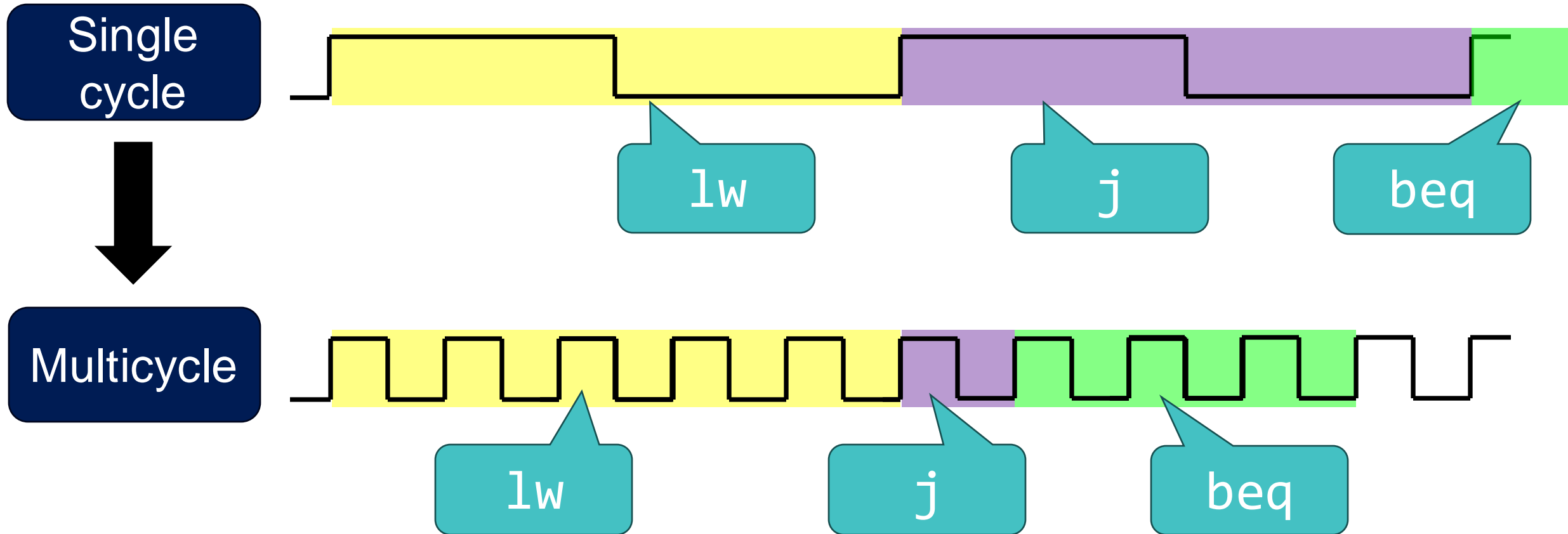
```
lw $2, 4($1)  
j ELSE  
beq $2, $3, ELSE
```



Multicycle Implementation: Intuition *


25

 Different instructions take different numbers of cycles!





Multicycle Implementation: Intuition

Datapath

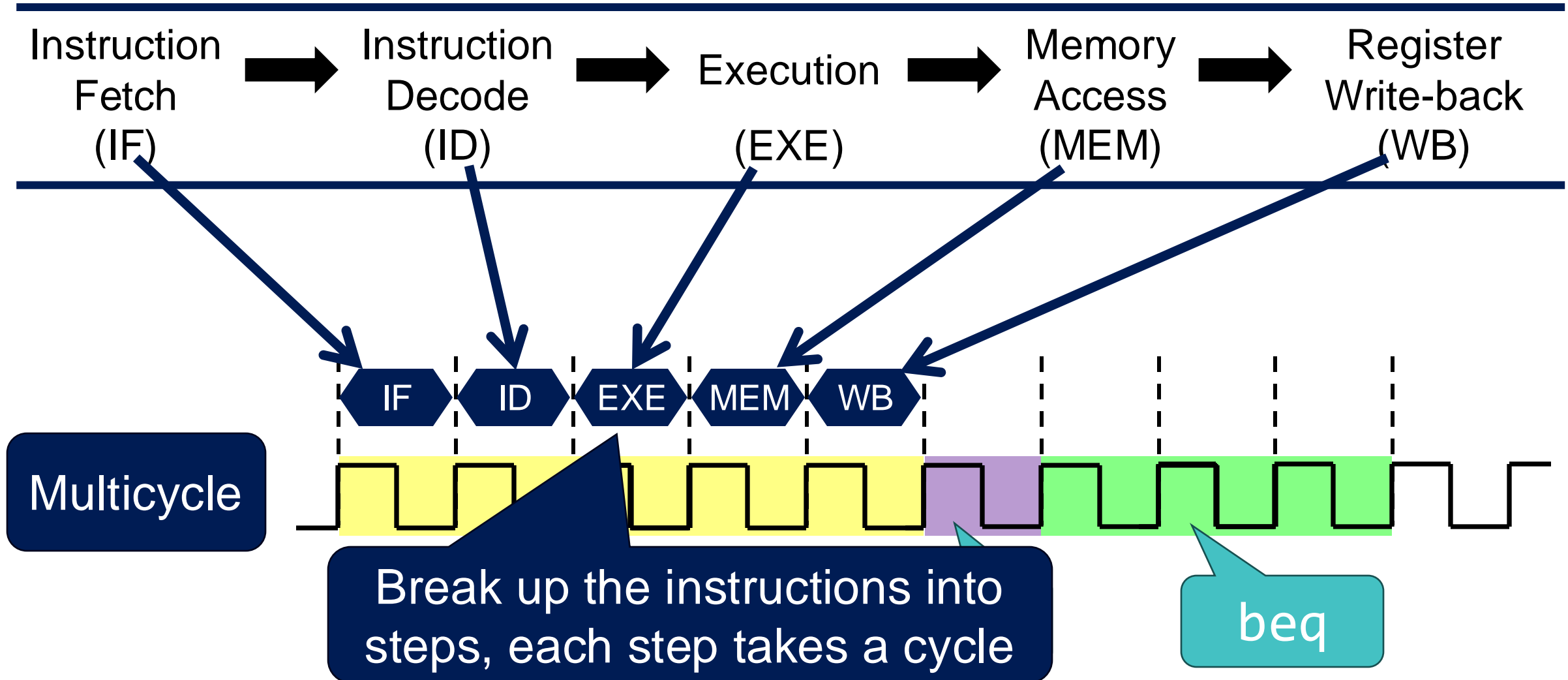

Multicycle Implementation: Intuition

Datapath

  

Multicycle Implementation: Overview




- **An instruction is executed in multiple clock cycles**
 - Different instructions take different numbers of cycles
 - Make cycle time smaller

How it can be possible?
→ Introduce additional internal registers

Multicycle Implementation: Overview

- **An instruction is executed in multiple clock cycles**
 - Different instructions take different numbers of cycles
 - Make cycle time smaller

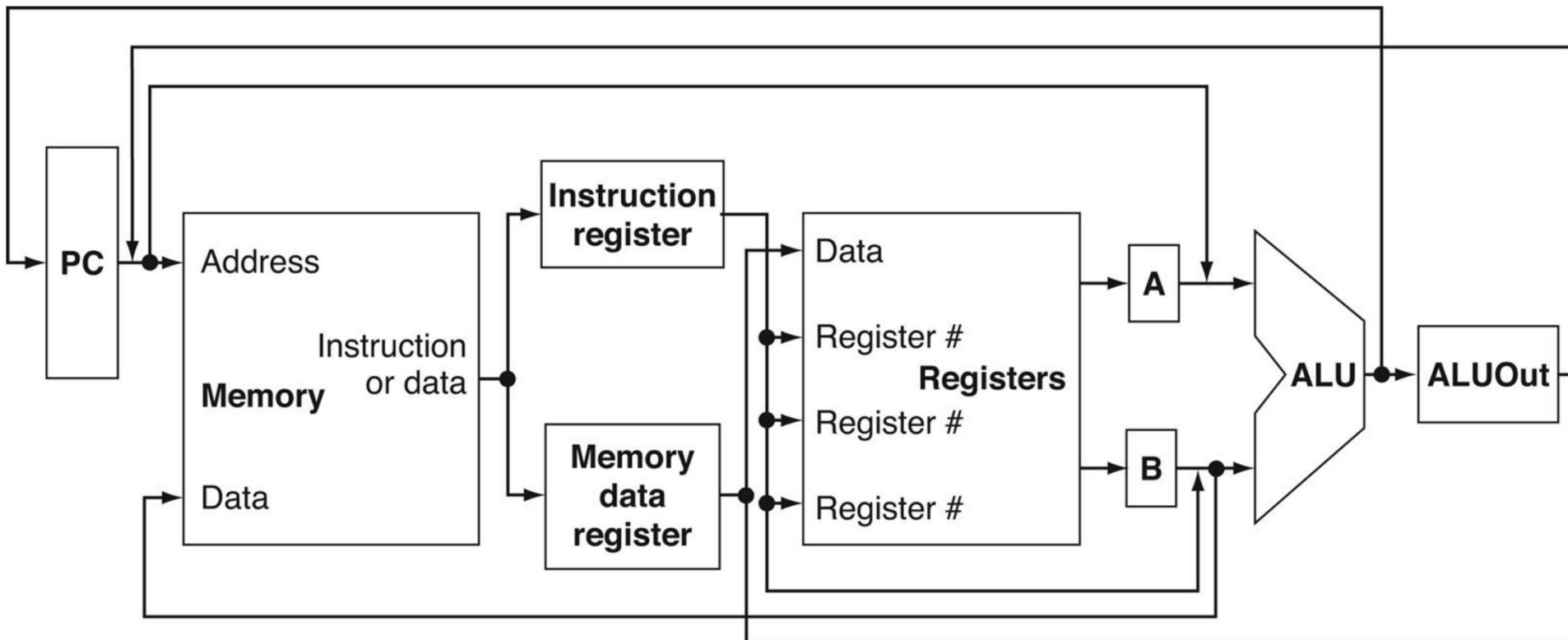
How it can be possible?
→ Introduce additional internal registers



Multicycle Implementation: Overview



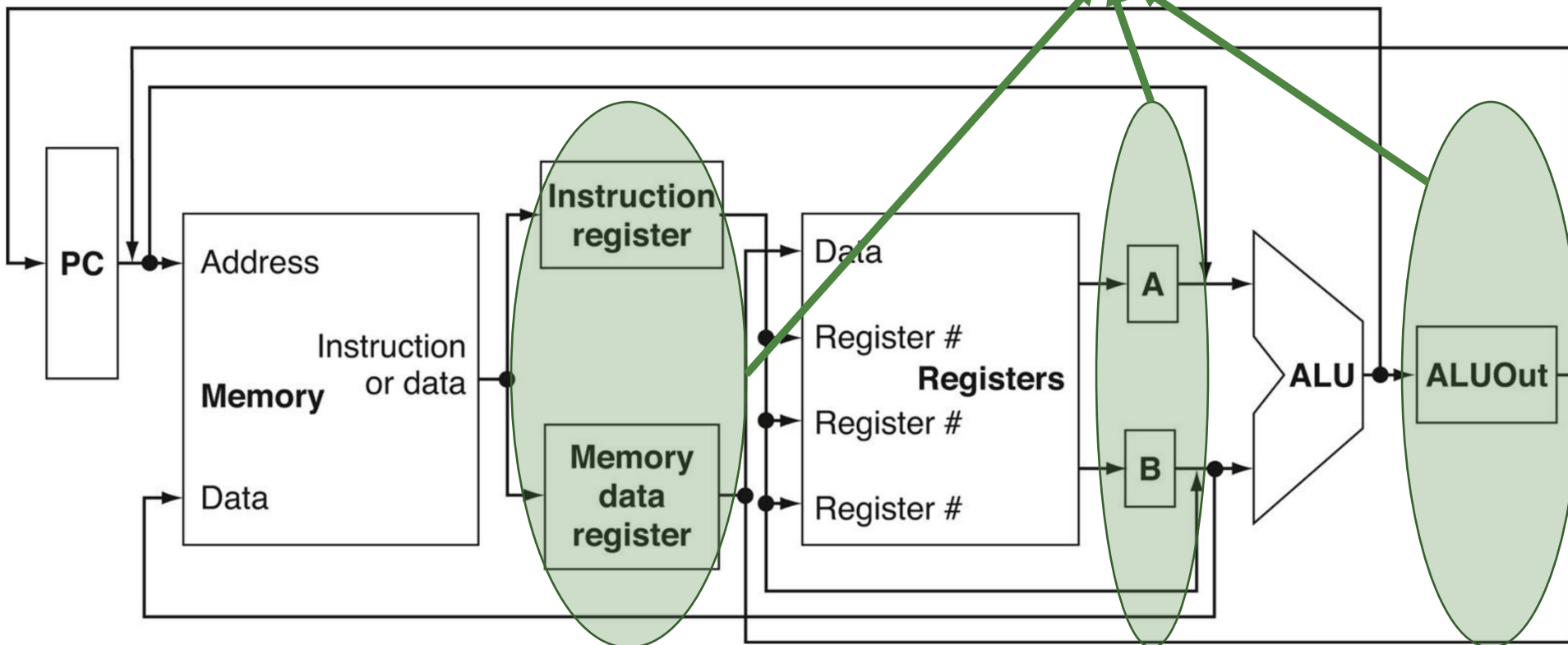
How it can be possible?
→ Introduce additional internal registers



Multicycle Implementation: Overview



31

lw
instruction

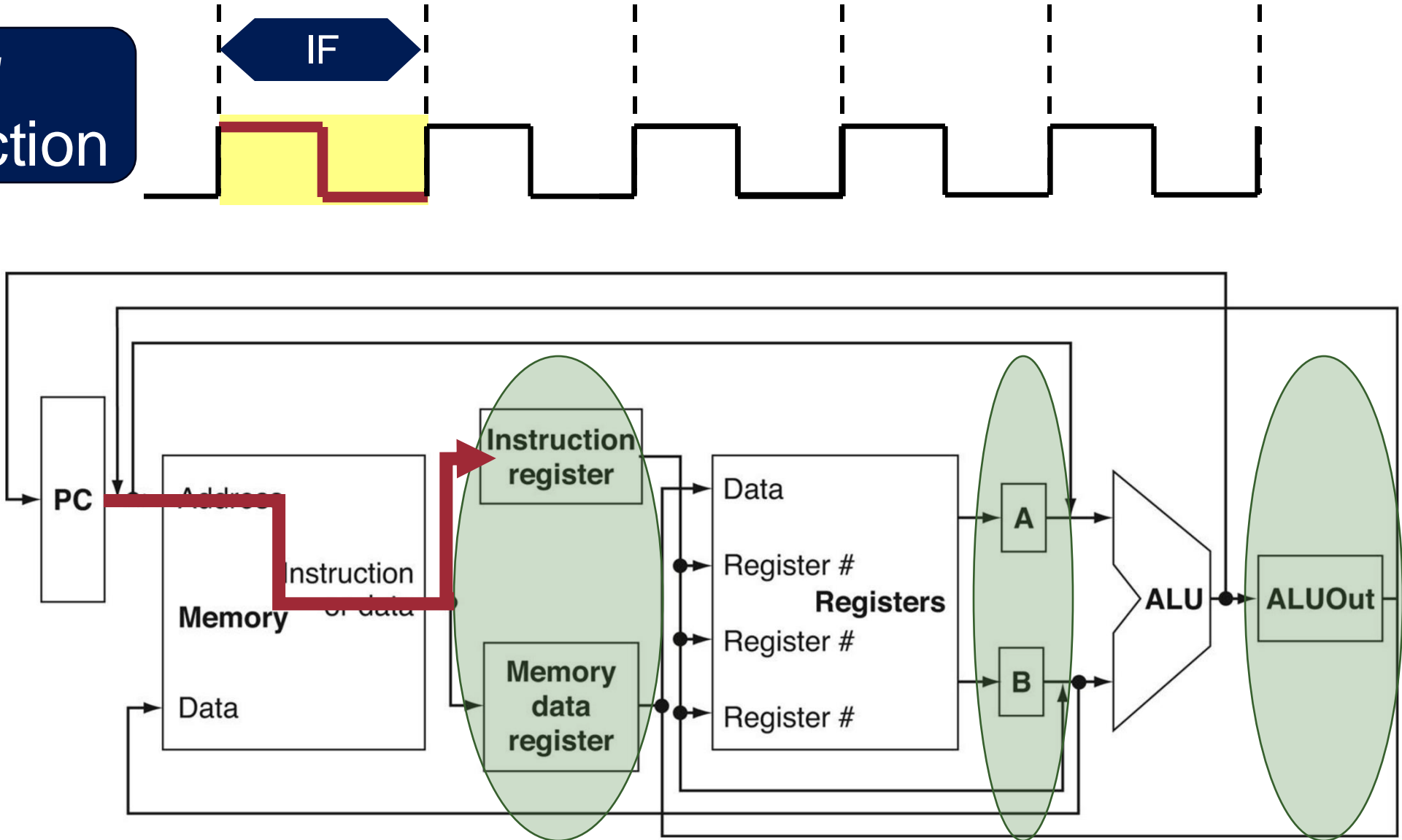



Multicycle Implementation: Overview

33

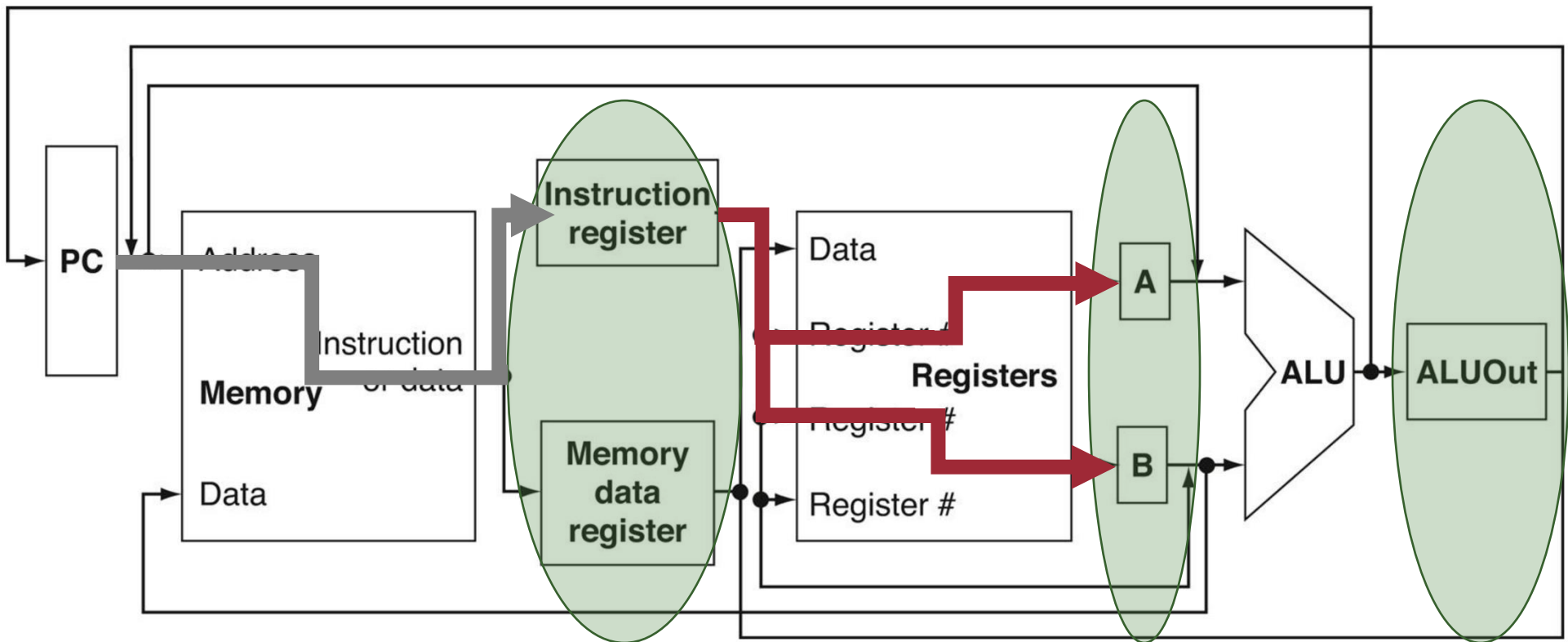 



Multicycle Implementation: Overview

34

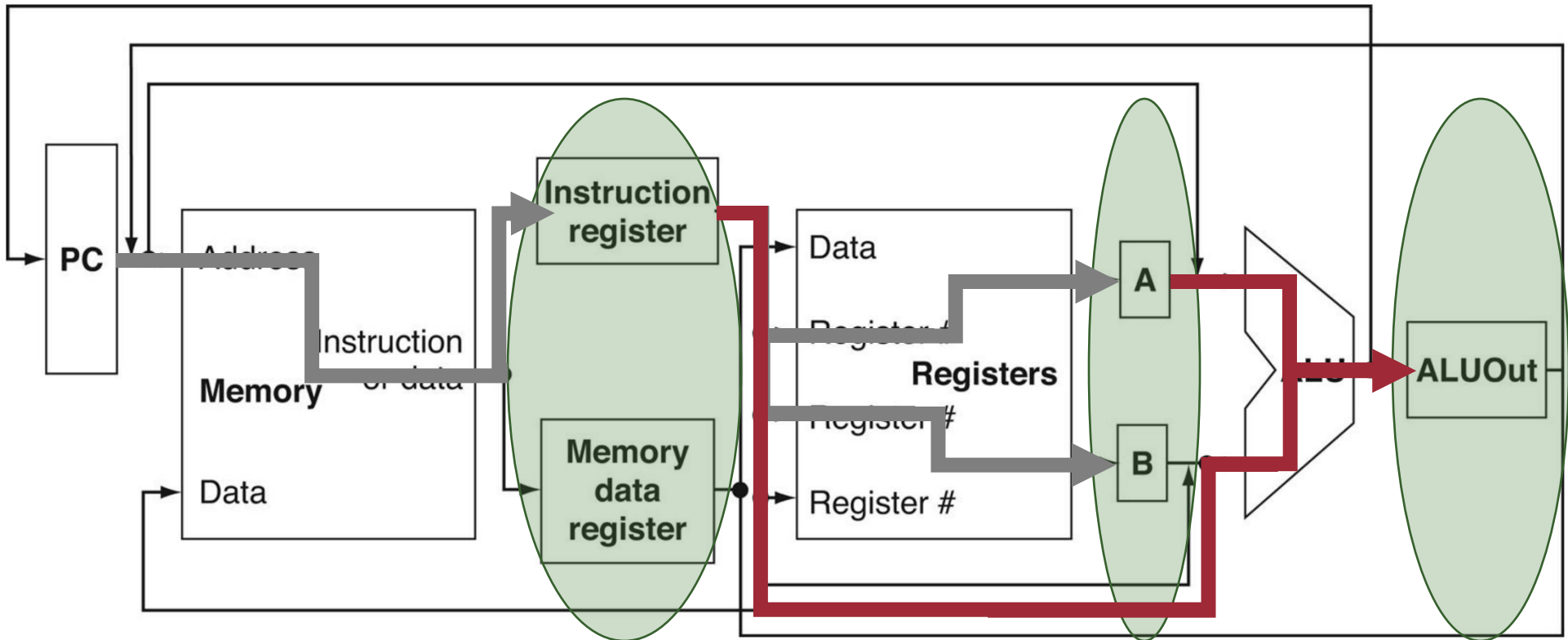 



Multicycle Implementation: Overview

36

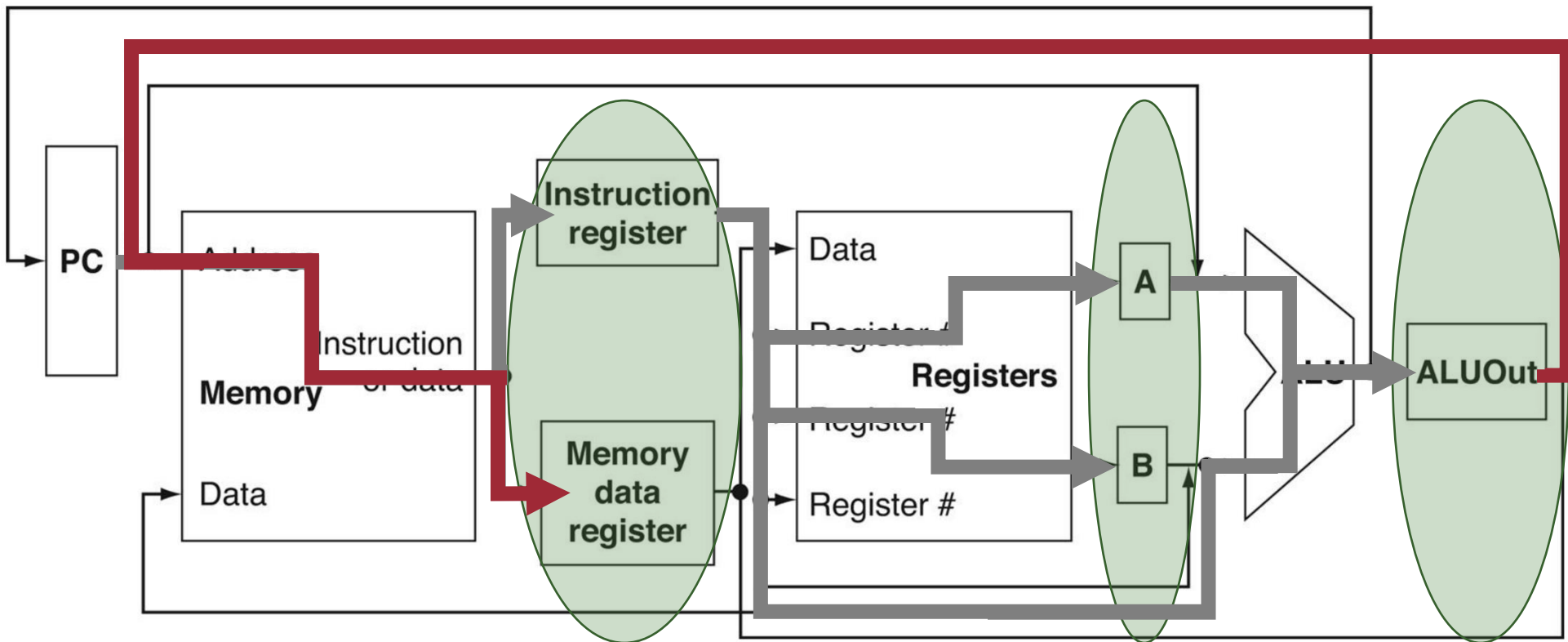 



Multicycle Implementation: Overview

37

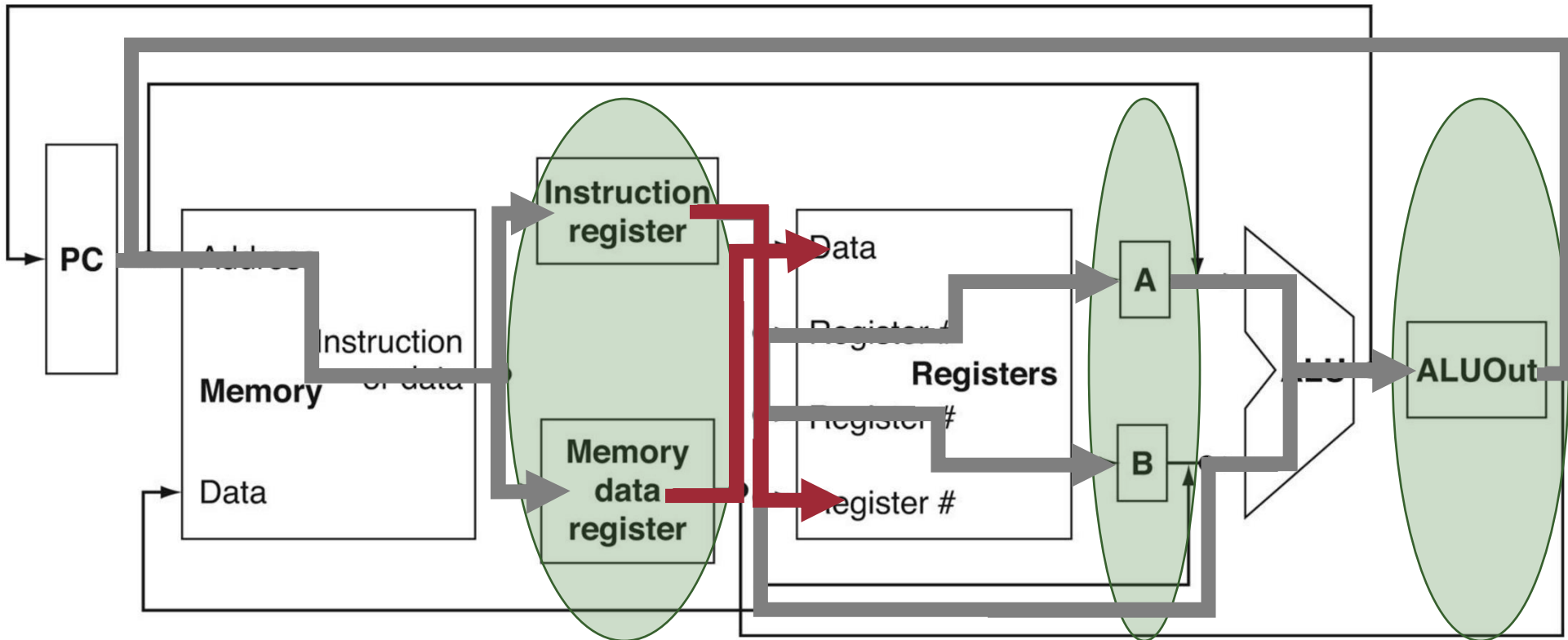 

Multicycle Implementation: Overview

38

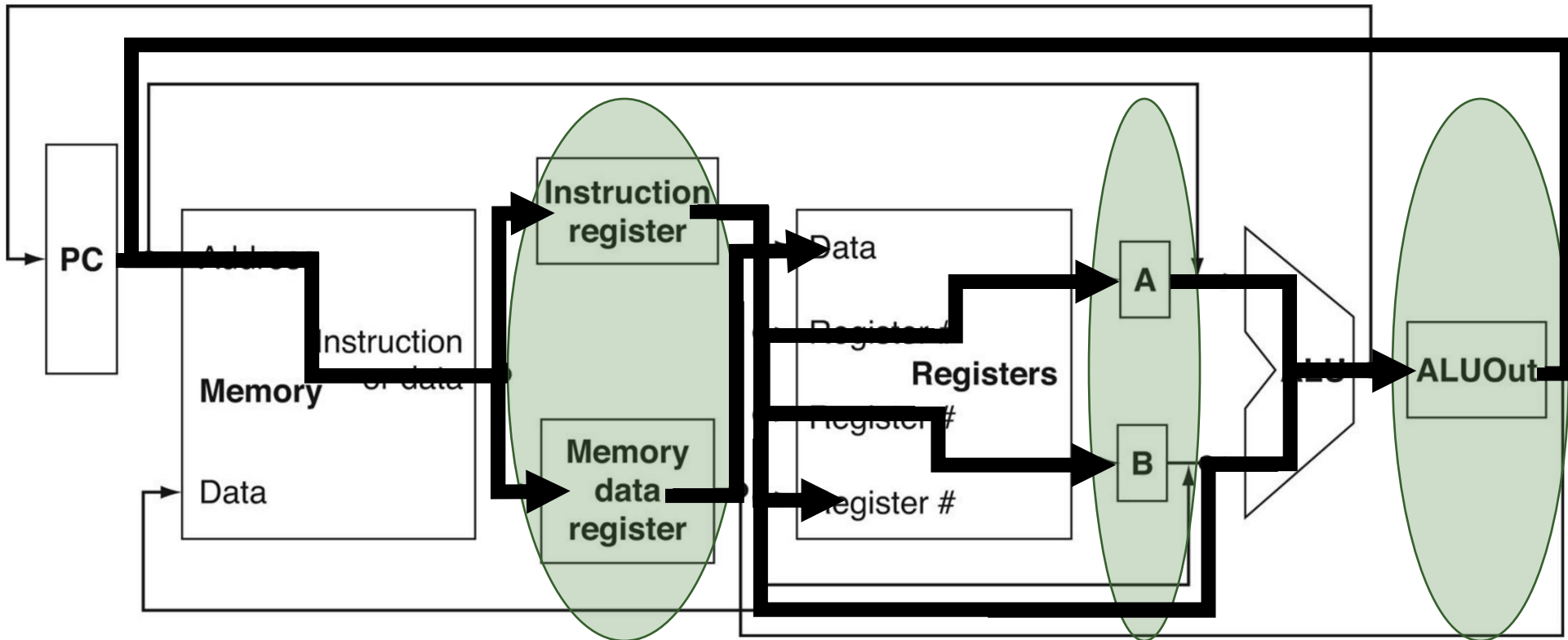 

Multicycle Implementation: Overview



- **An instruction is executed in multiple clock cycles**
 - Different instructions take different numbers of cycles
 - Make cycle time smaller
- **Break up the instructions into steps, each step takes a cycle**
 - Balance the amount of work to be done
 - Restrict each cycle to use only one major functional unit
- **At the end of a cycle**
 - (On rising-edge) store values for use in later cycles
 - Introduce additional internal registers

Multicycle Implementation: Advantages



40

Compared with single-cycle implementation, performance can be *increased* due to:

- Clock cycle period ↓
- Different instructions take different numbers of cycles
- Hardware sharing: single ALU and single memory
 - Reduce the circuit area
 - They can be used for **different purposes** in different clock cycle

Hardware Sharing: Single Memory





41

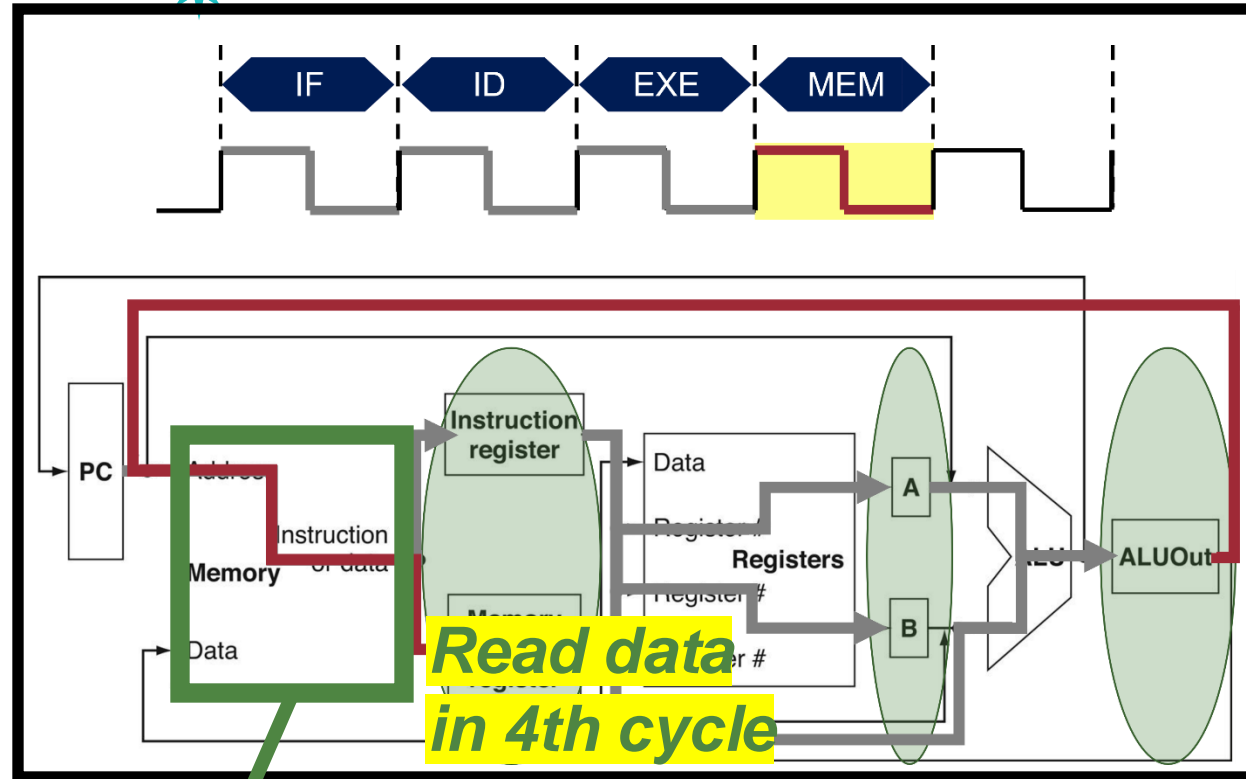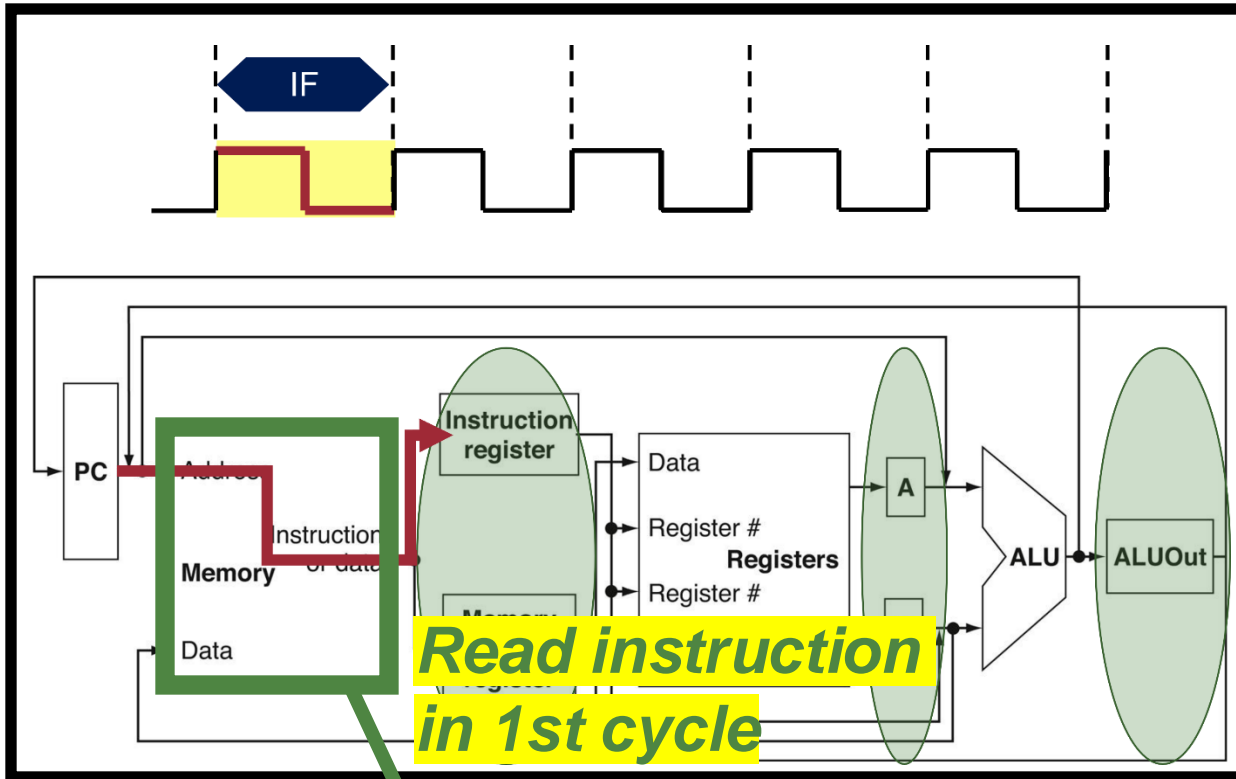



Memory can be shared because it is used
in different clock cycle

Hardware Sharing: Single ALU

42

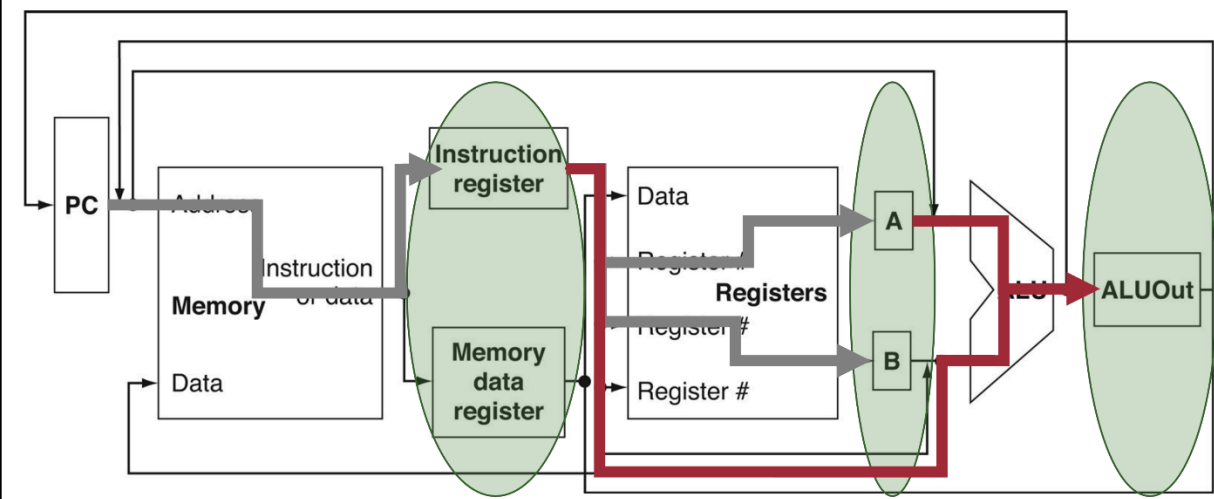 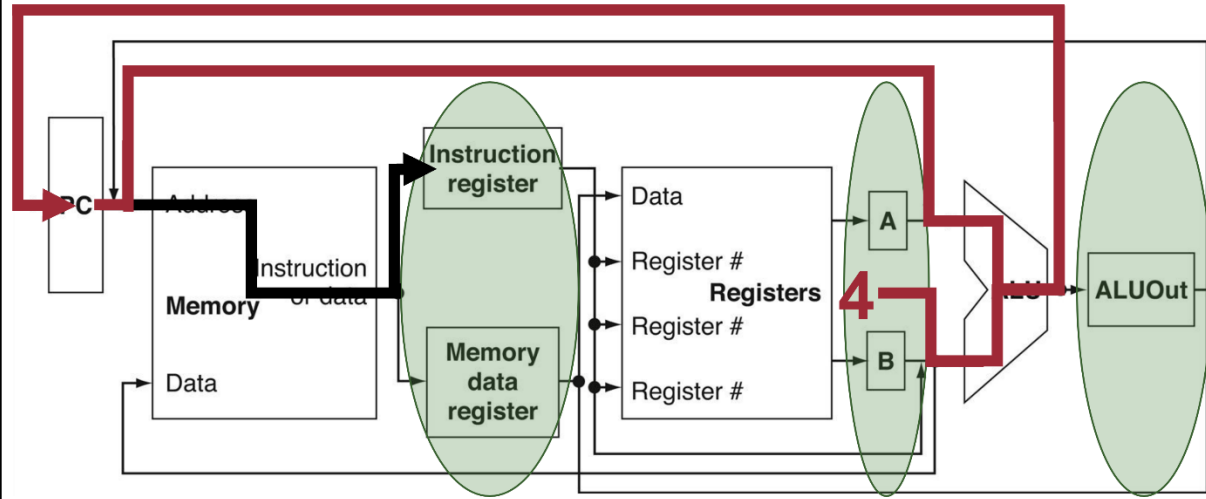 

Hardware Sharing: Single ALU

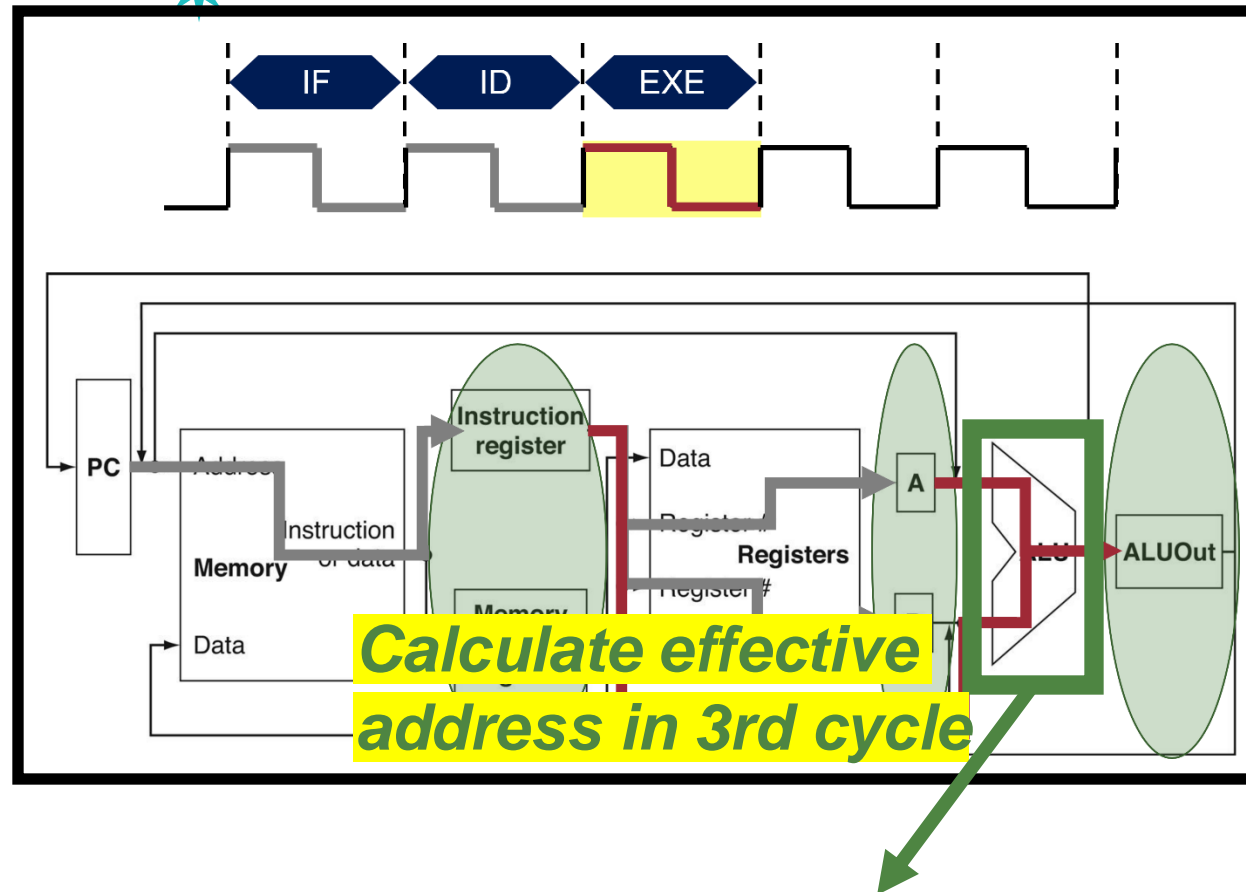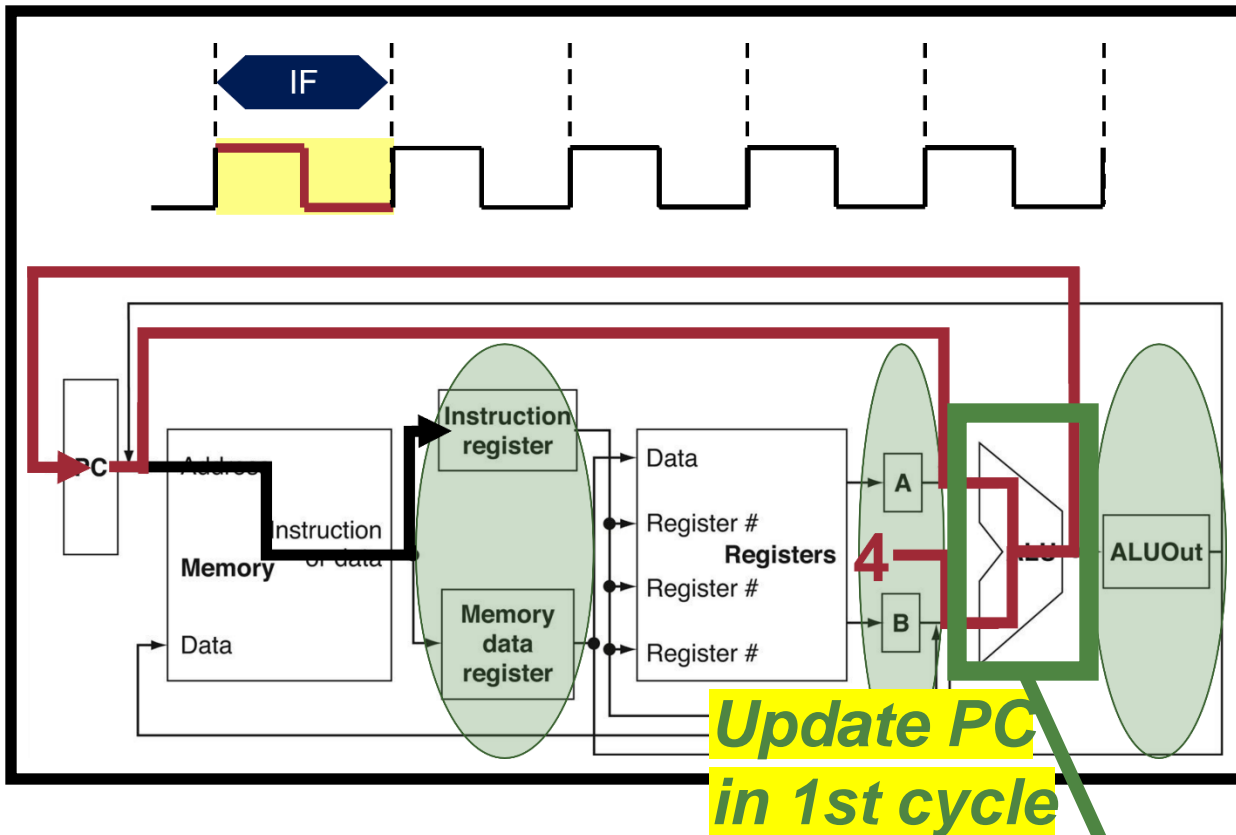

ALU can be shared because it is used
in different clock cycle

Multicycle Implementation: Advantages

44

Compared with single-cycle implementation, performance can be *increased* due to:

- Clock cycle period ↓
- Different instructions take different numbers of cycles
- Hardware sharing: single ALU and single memory
 - Reduce the circuit area
 - They can be used for **different purposes** in different clock cycle

Multicycle Implementation: Disadvantages



45

Compared with single-cycle implementation, performance can be **decreased** due to:

- Additional internal registers
- More multiplexors to shared functional units (We will cover about it)
- More complicated control to consider about *time* (We will cover about it)


Single-cycle vs multicycle: which one is better?

**There are trade-offs in terms of time,
design complexity, and hardware area**

**Now, let's look at the details
of the multicycle datapath!**


Multicycle Datapath for MIPS

48

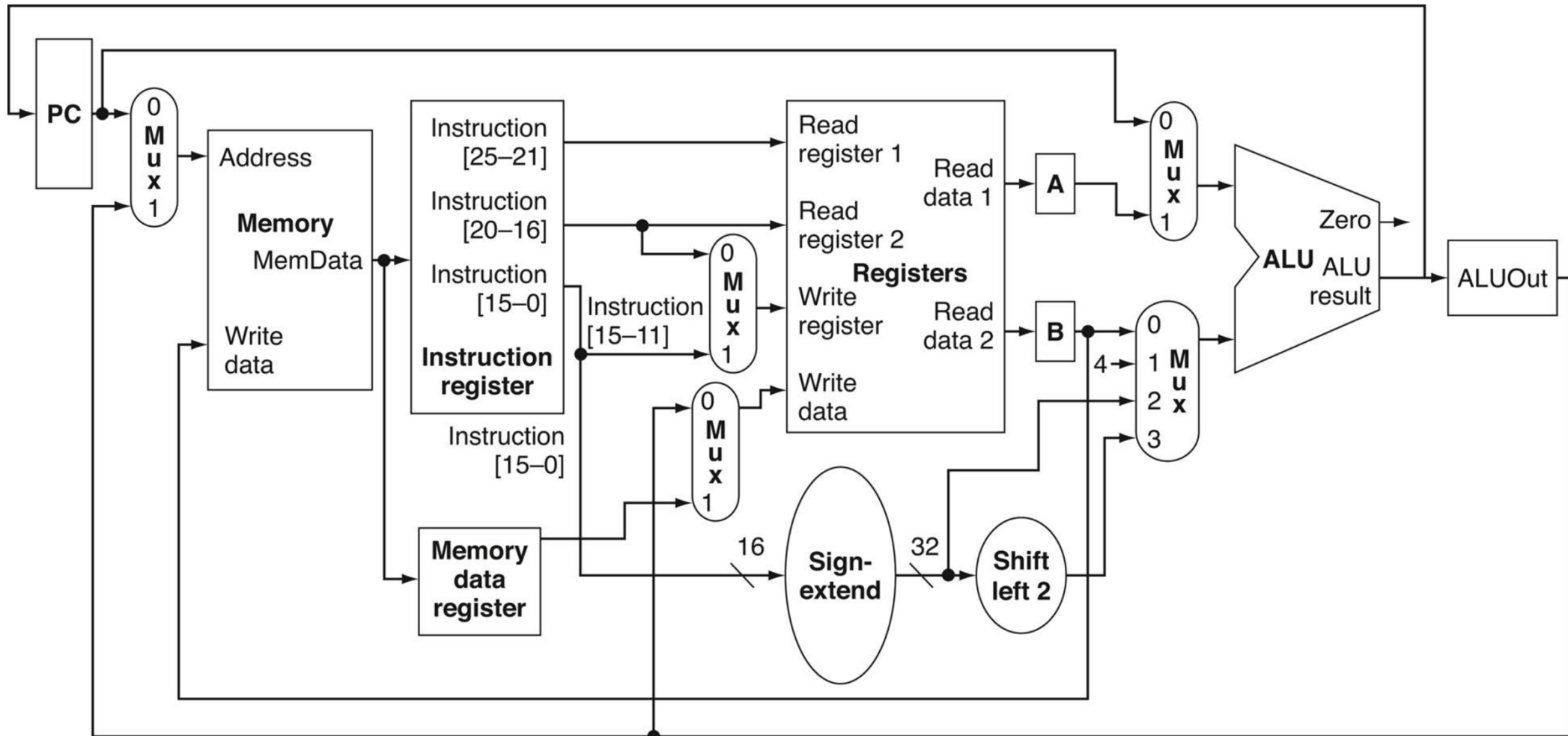


Multicycle Datapath for MIPS


49

 

(1) Instruction Fetch (IF) *

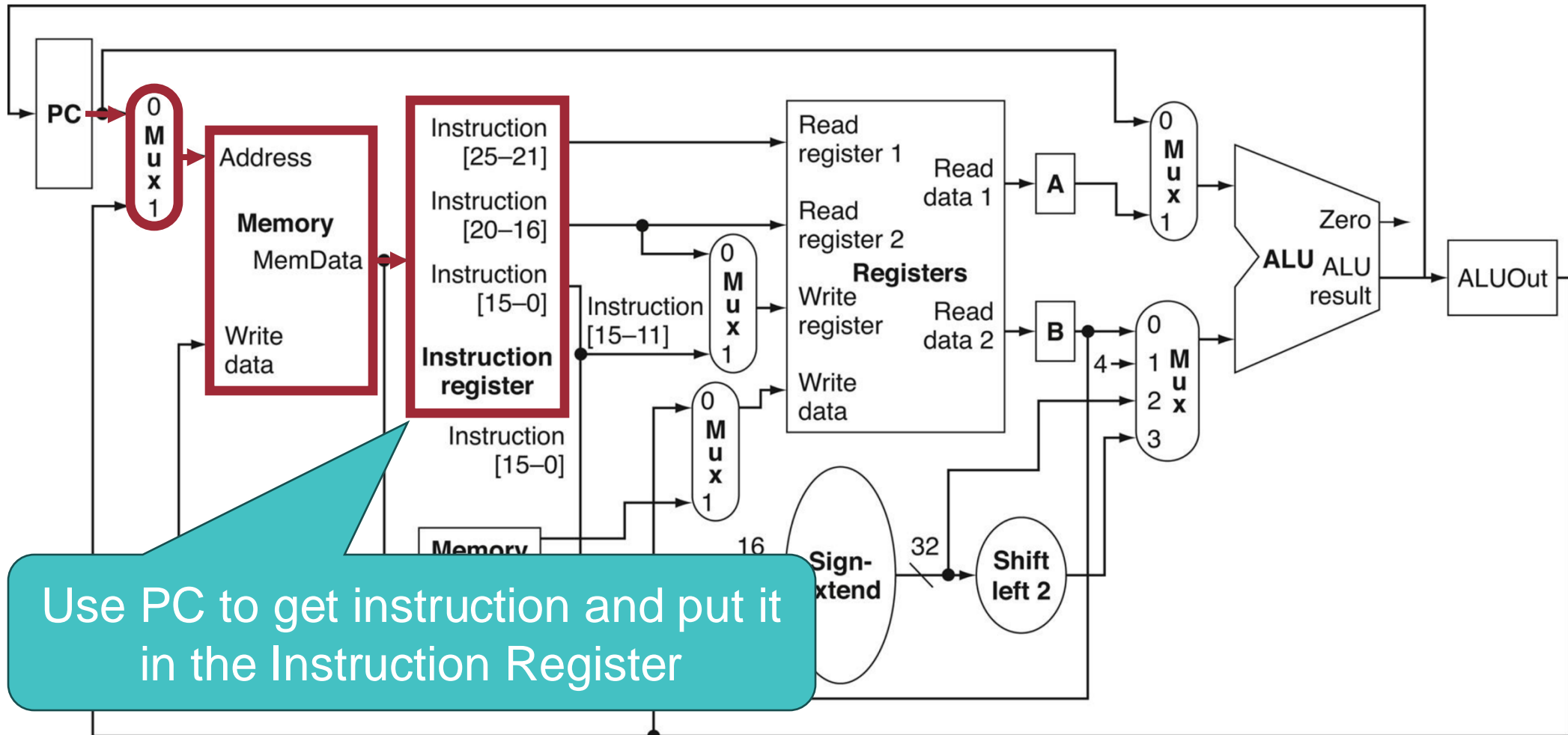


(1) Instruction Fetch (IF) ★

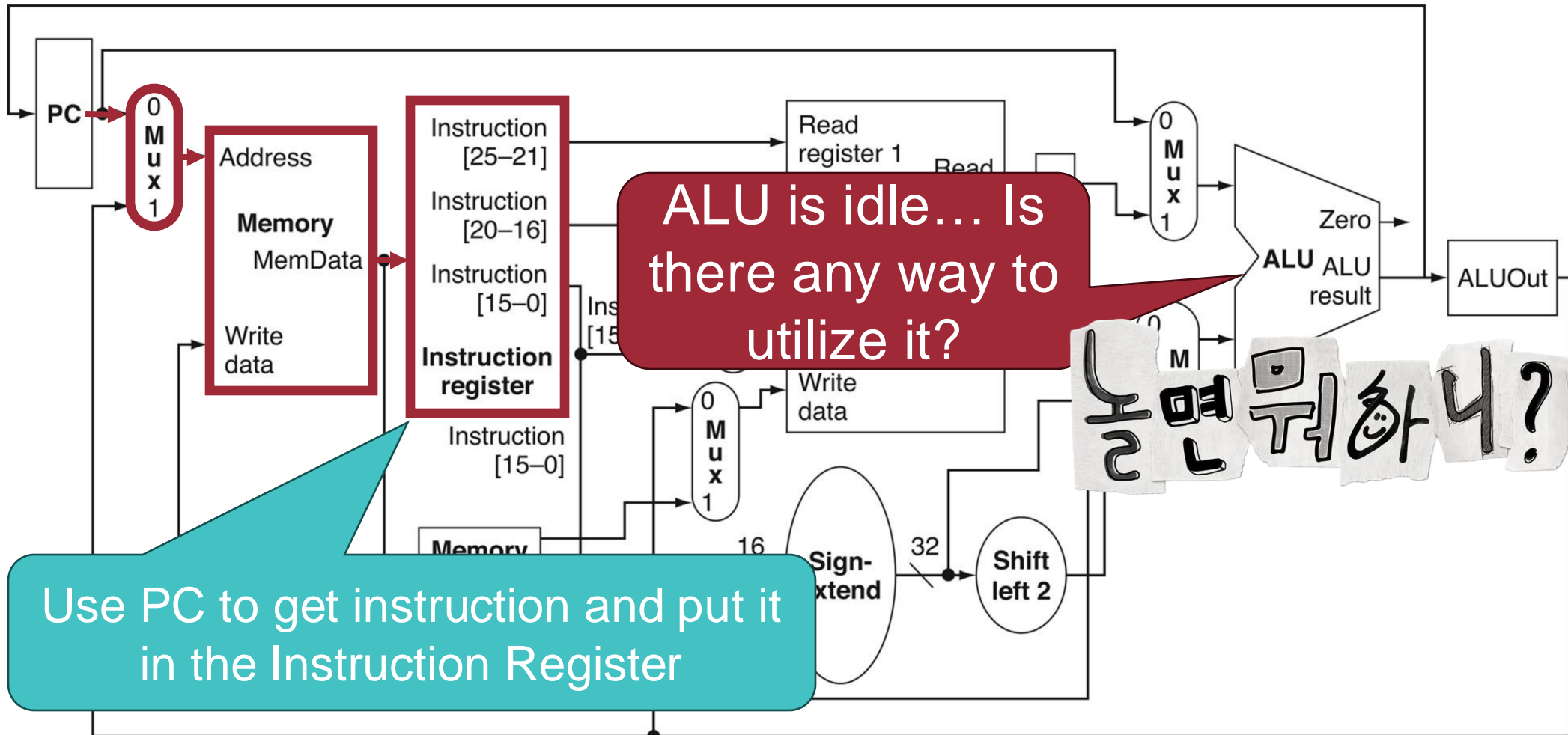

(1) Instruction Fetch (IF) *

PC = PC + 4

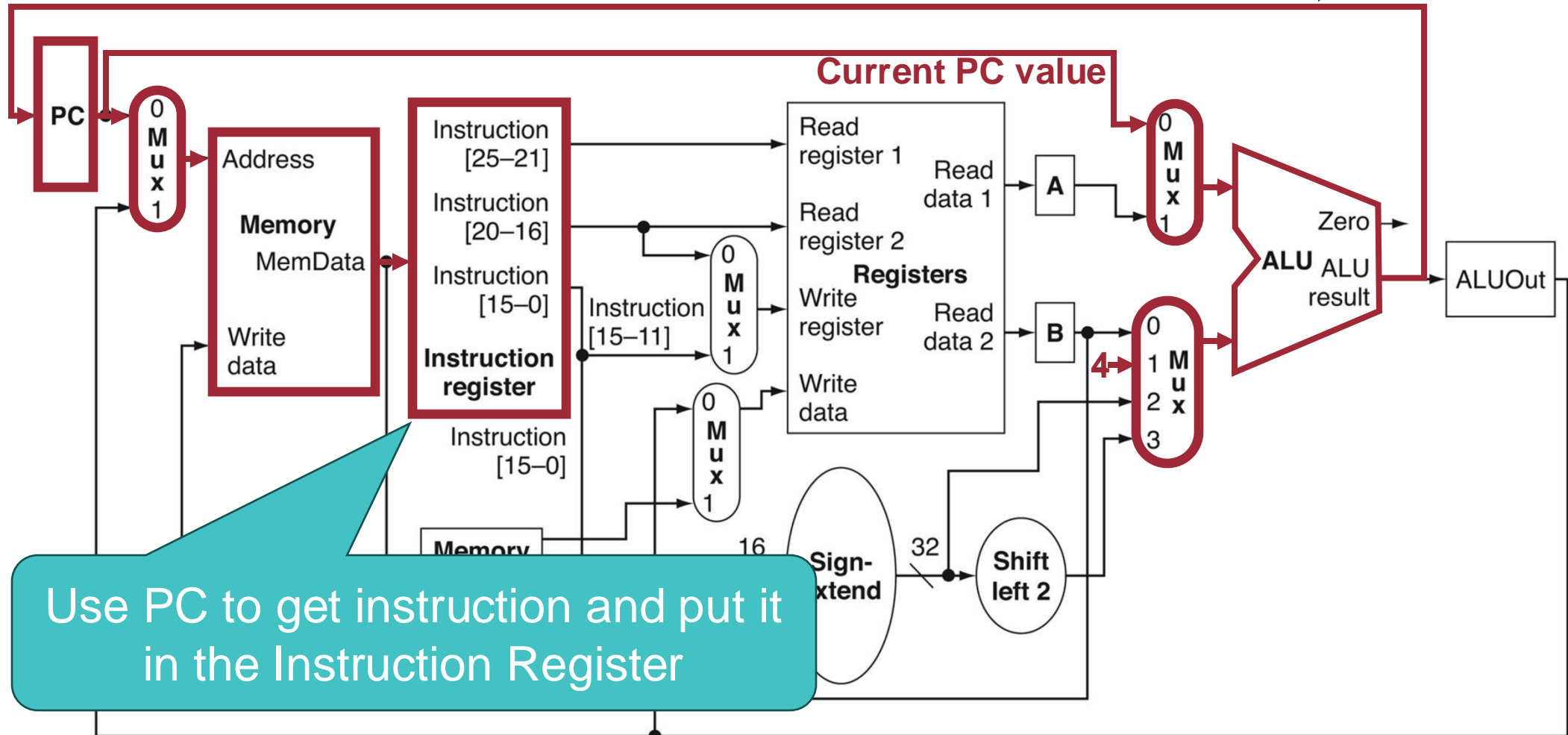


(1) Instruction Fetch (IF): Summary

- Use PC to get instruction and put it in the Instruction Register
- Increment the PC by 4 and put the result back in the PC


(2) Instruction Decode (ID)

54

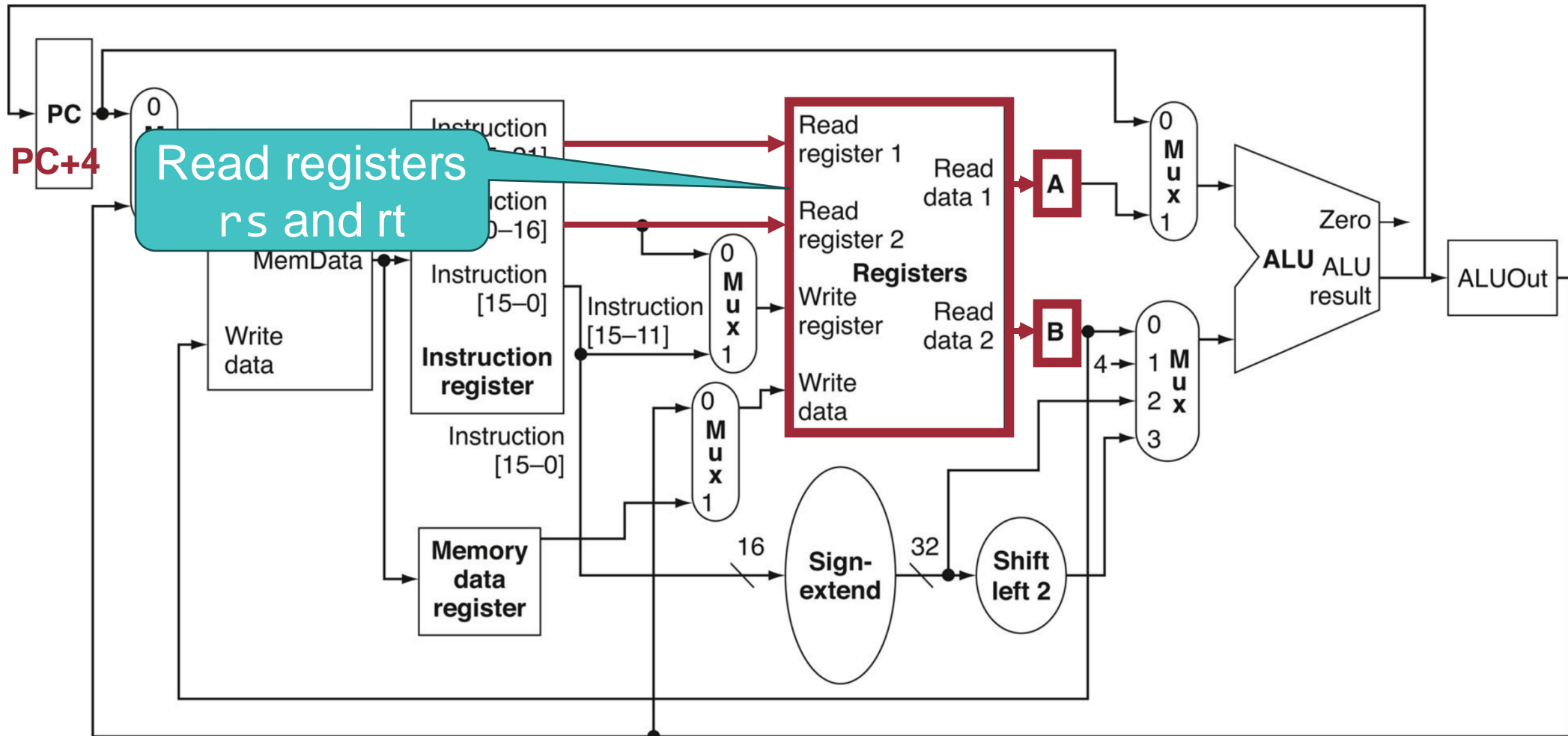


(2) Instruction Decode (ID)

55

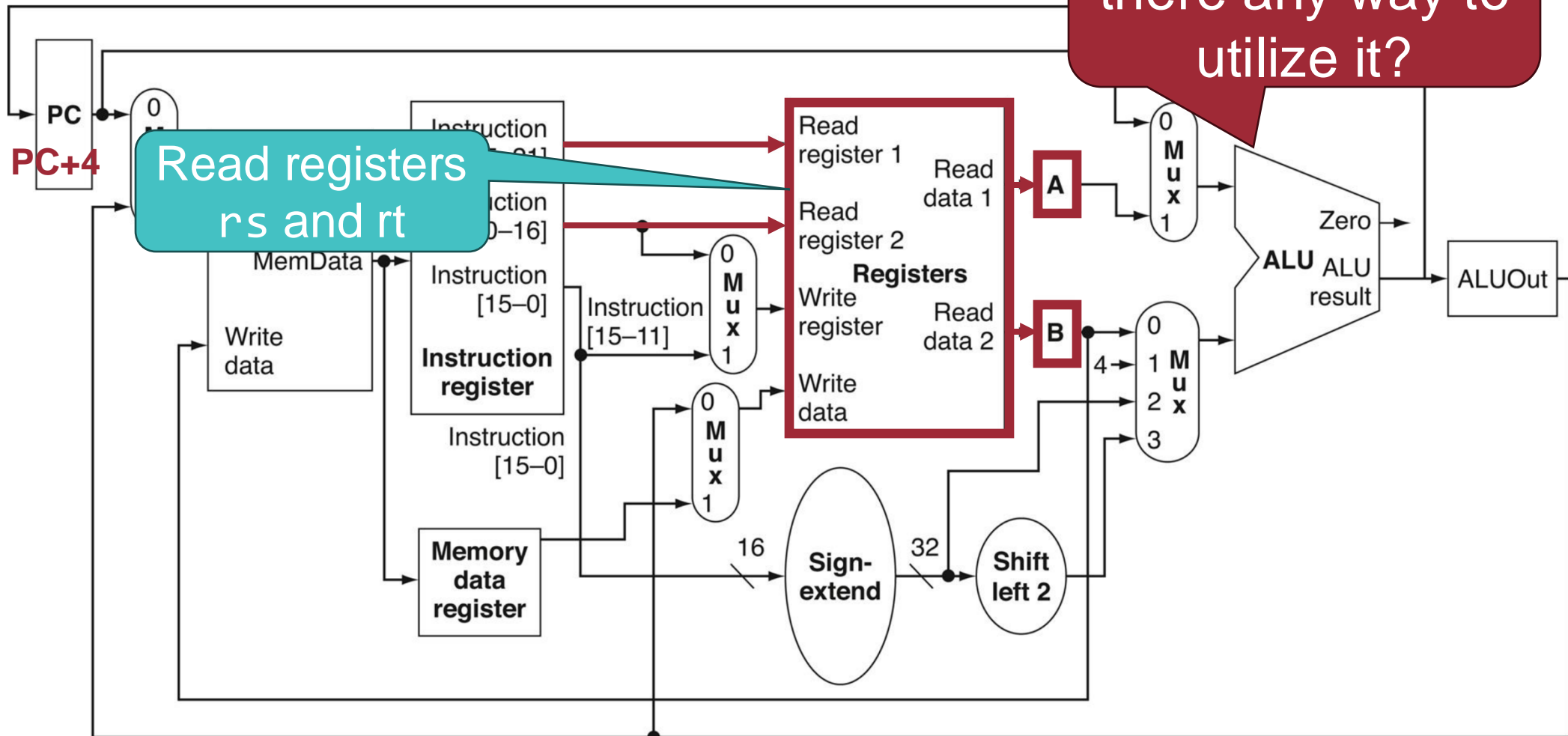

(2) Instruction Decode (ID)

56

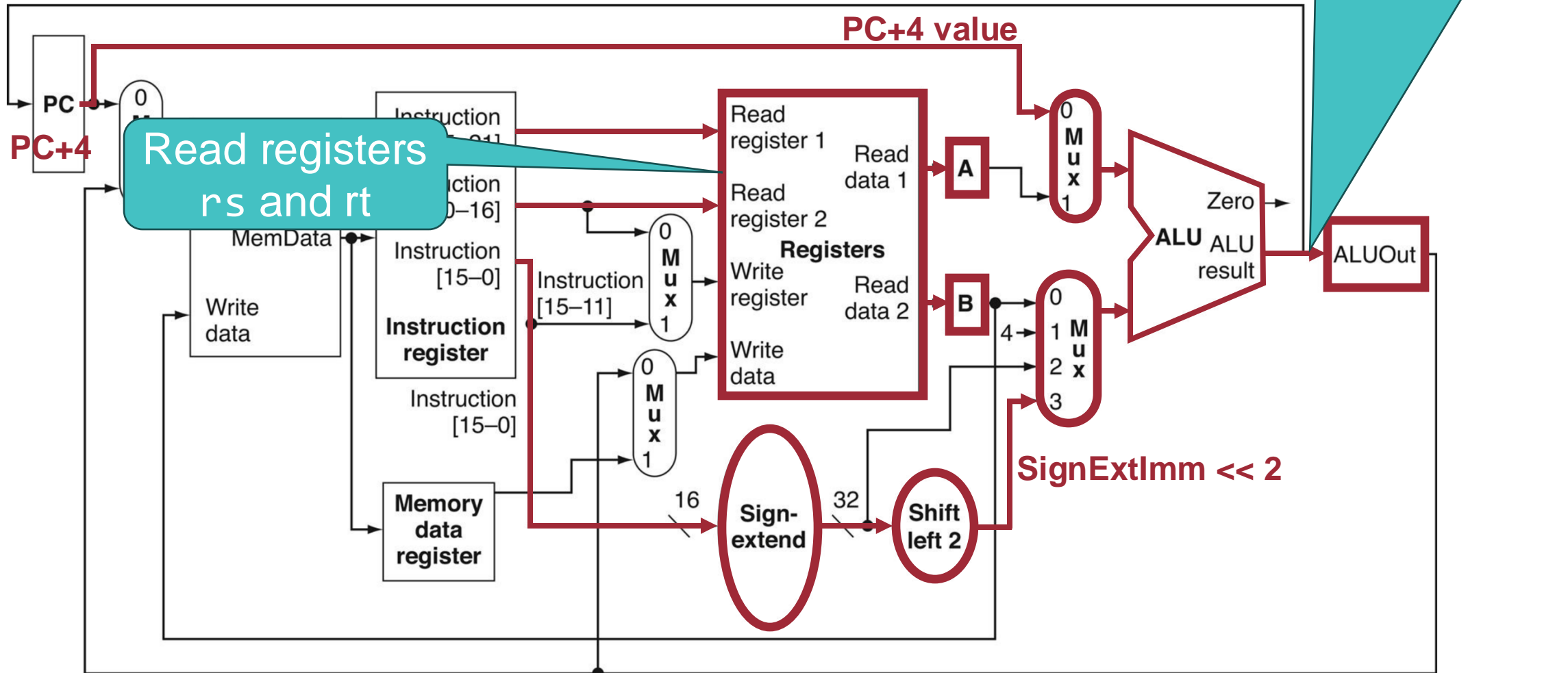

(2) Instruction Decode (ID): Summary



- Read registers `rs` and `rt`
- Compute the branch address in advance

IF and ID stages are common for all types of instructions

From the next stage, the actions vary depending on the type of instruction

Execution (EXE) Stage Summary



ALU is performing one of three functions, based on instruction type

Arithmetic / Logic
Instructions
(R-format)




$\text{ALUOut} \leftarrow A \text{ operation } B$

lw, sw
(I-format)

beq
(I-format)

R-formation – (3) Execution (EXE)

60

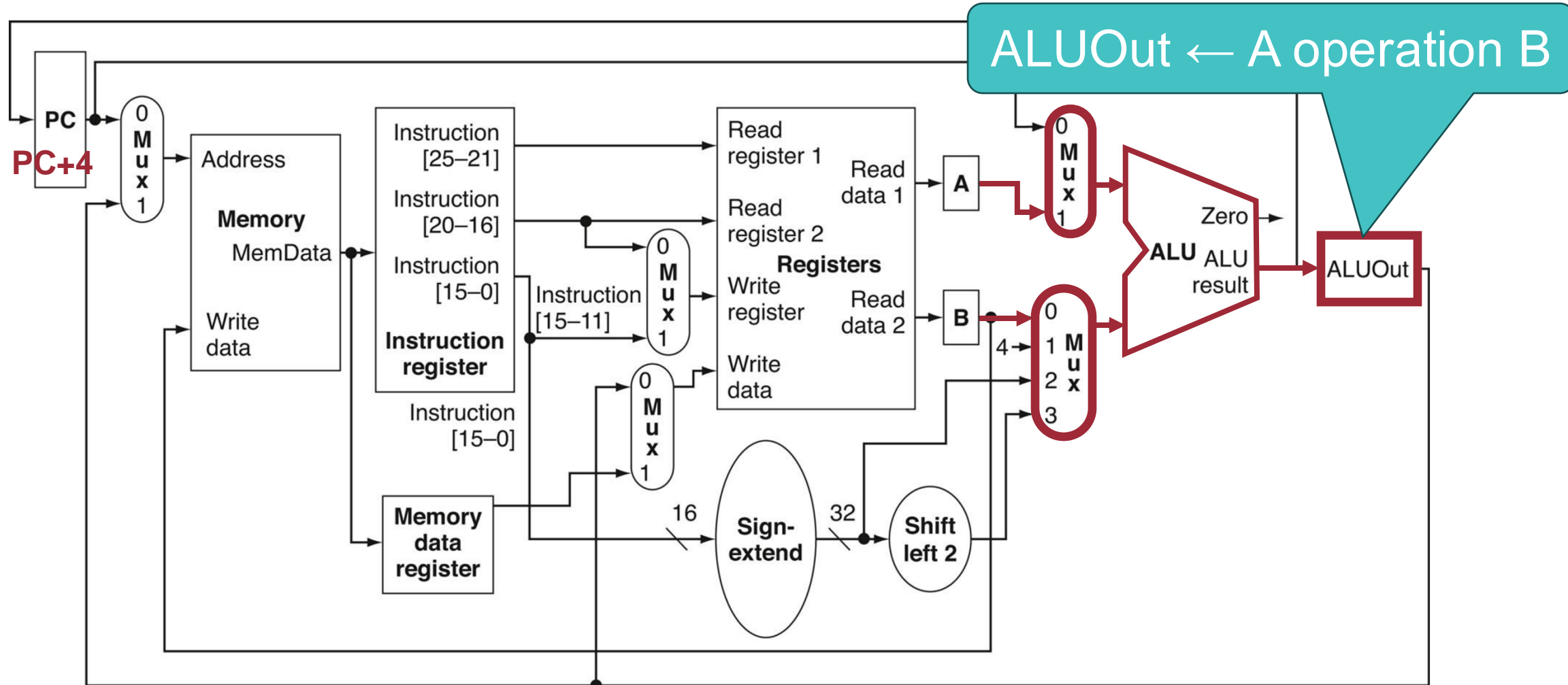

Execution (EXE) Stage Summary

ALU is performing one of three functions, based on instruction type

Arithmetic / Logic
Instructions
(R-format)



$\text{ALUOut} \leftarrow A \text{ operation } B$

lw, sw
(I-format)




$\text{ALUOut} \leftarrow A + \text{SignExtImm}$

beq
(I-format)

lw and sw – (3) Execution (EXE)


63

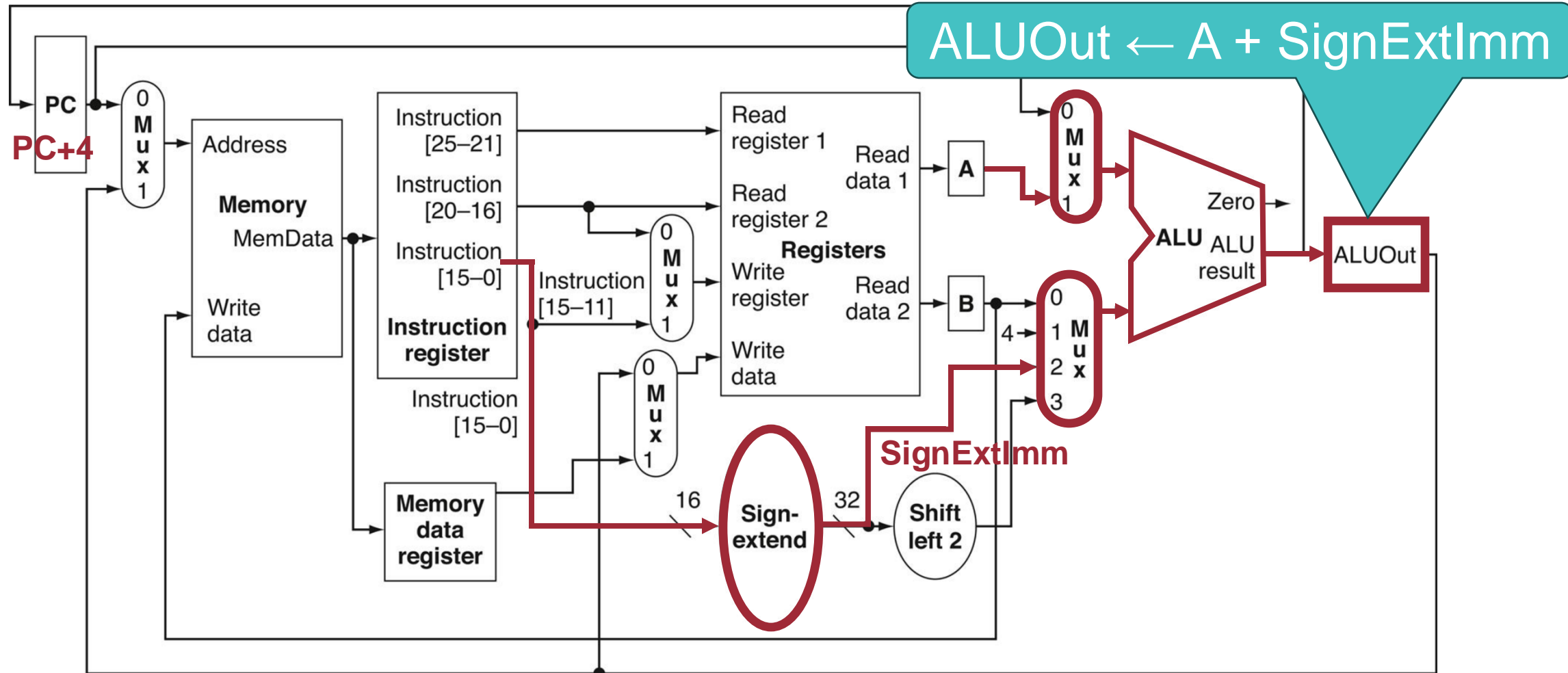

sw – (4) Memory Access (MEM)


64

Completion!

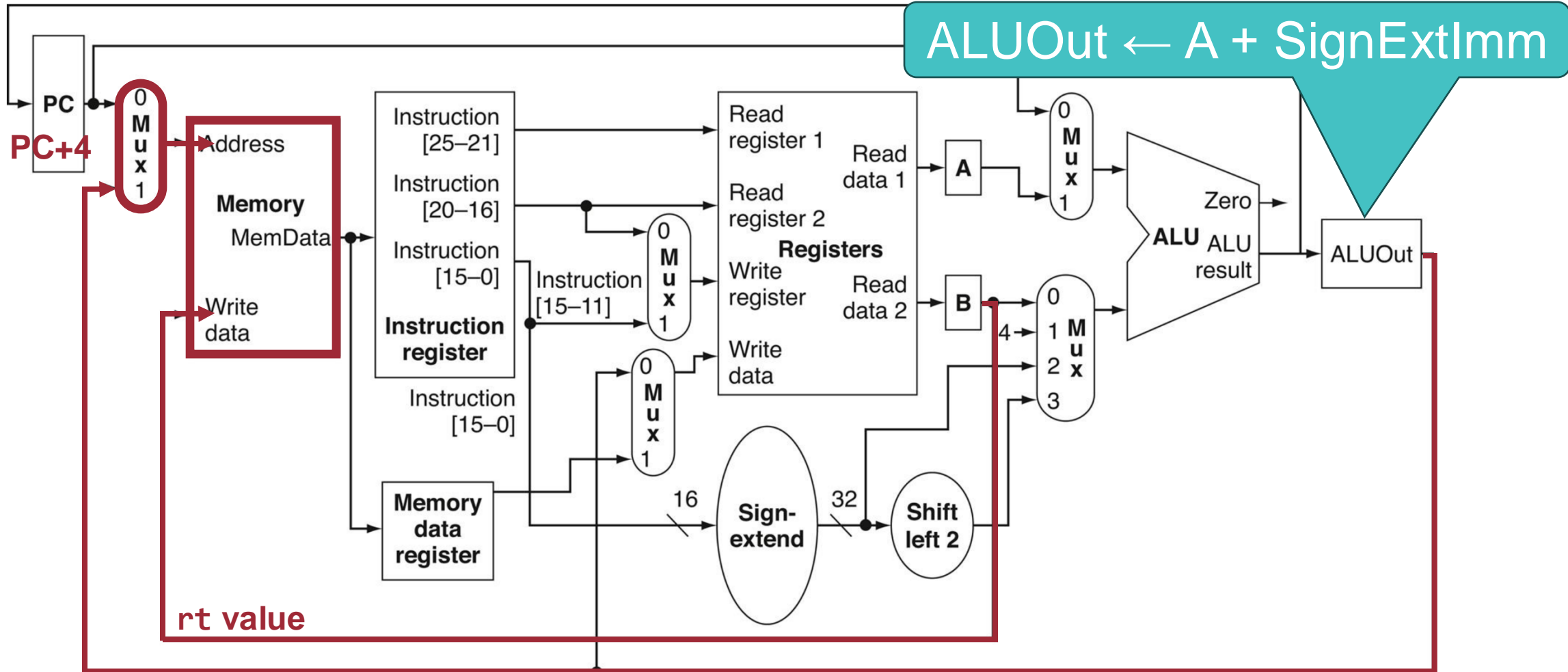

1w – (4) Memory Access (MEM)


65

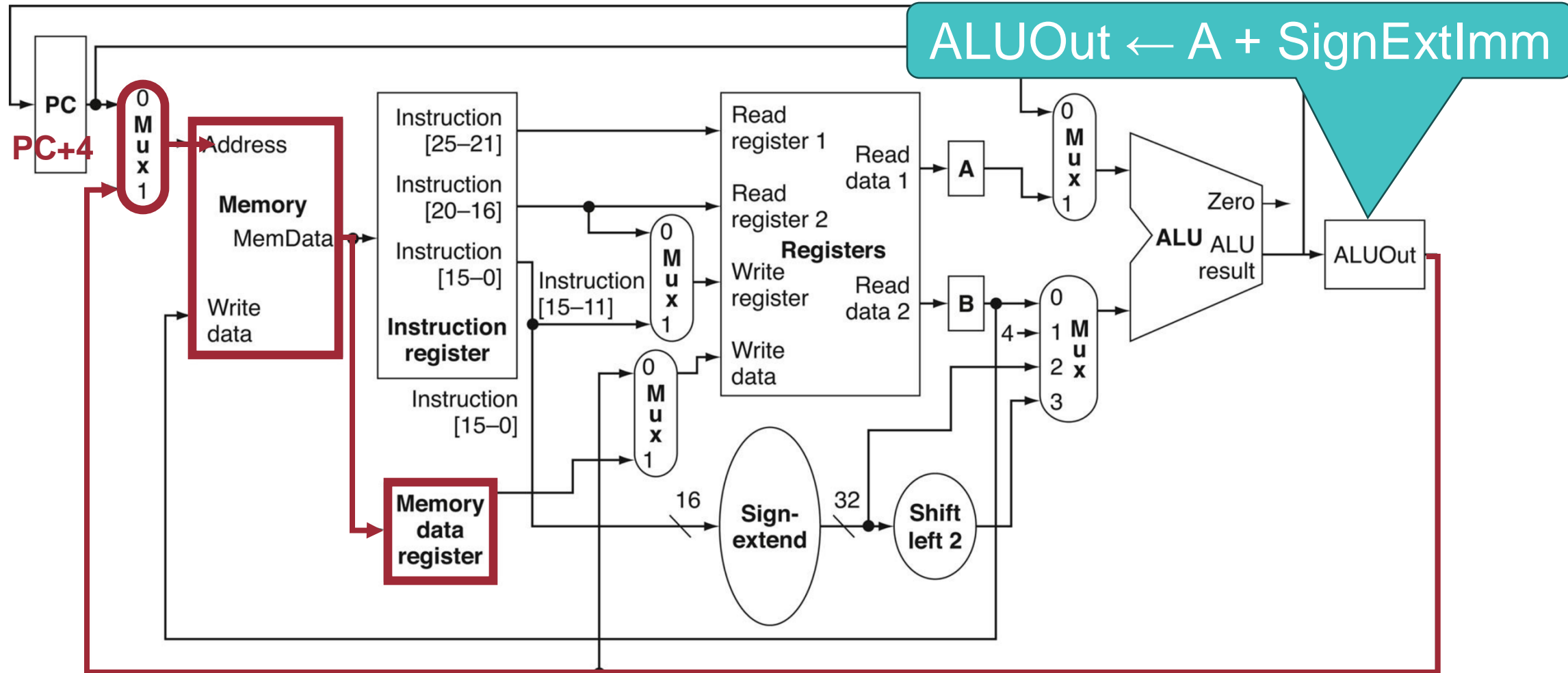

1w – (5) Register Write-back (WB)

66

Completion!

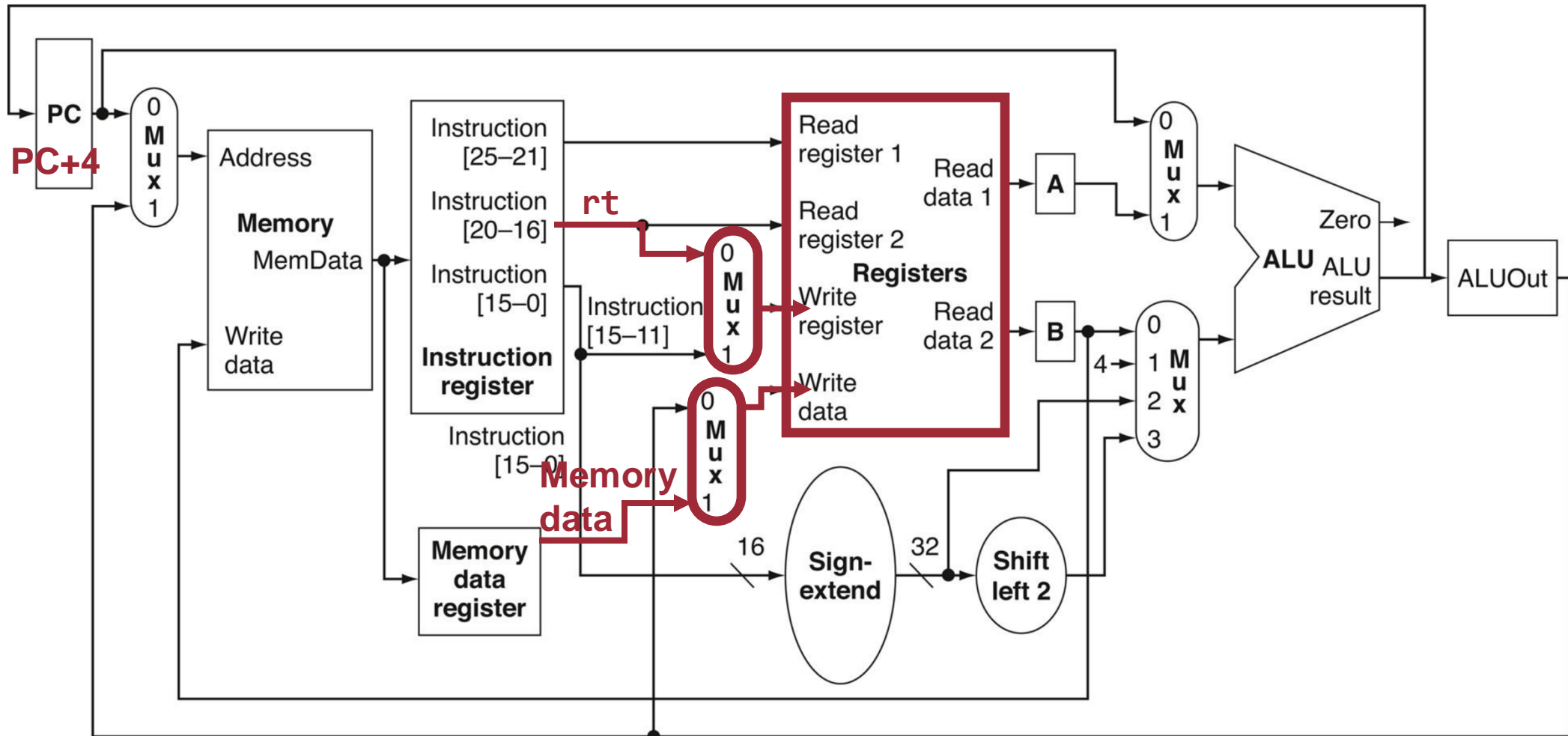

Execution (EXE) Stage Summary

ALU is performing one of three functions, based on instruction type

Arithmetic / Logic
Instructions
(R-format)



$\text{ALUOut} \leftarrow A \text{ operation } B$

lw, sw
(I-format)



$\text{ALUOut} \leftarrow A + \text{SignExtImm}$


beq
(I-format)



if (zero):
 $\text{PC} \leftarrow \text{ALUOut}$


beq – (3) Execution (EXE)

68

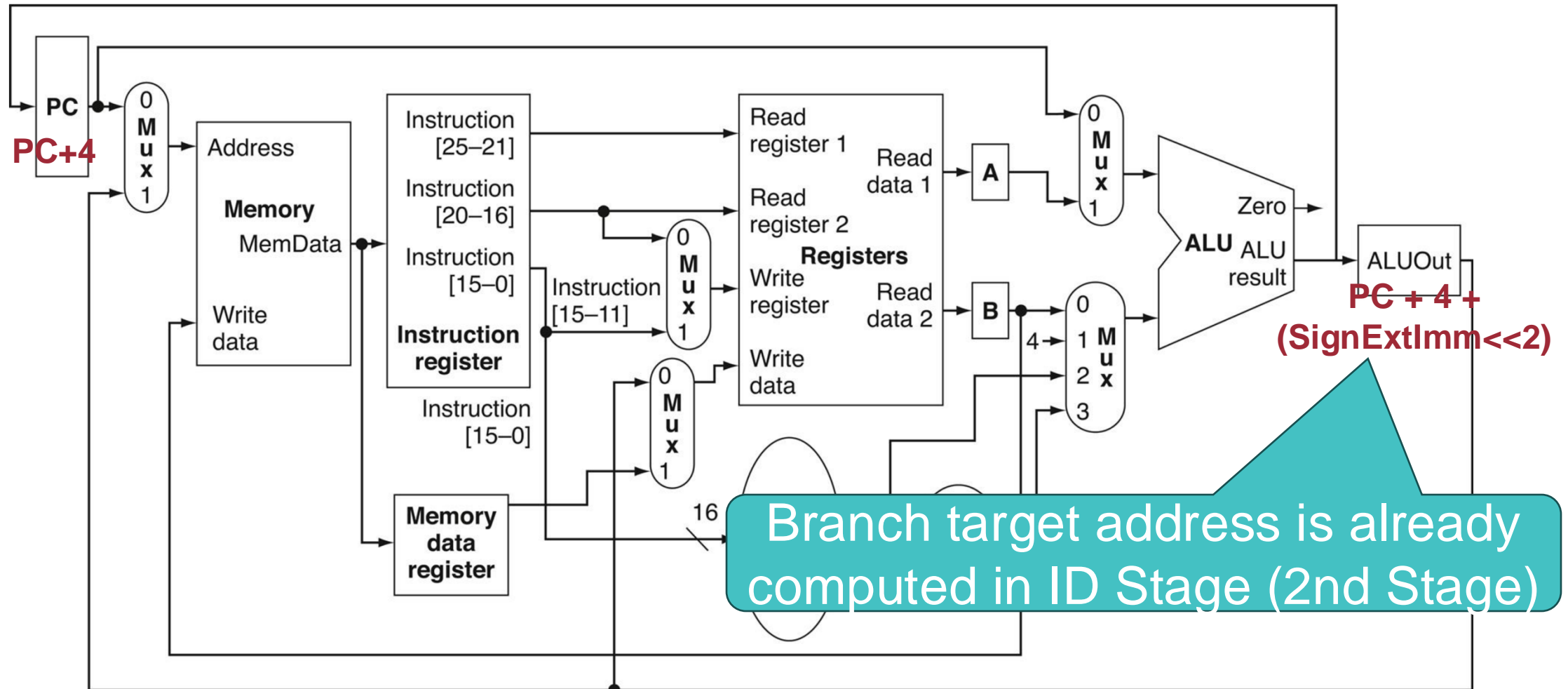


beq – (3) Execution (EXE)

Additional mux

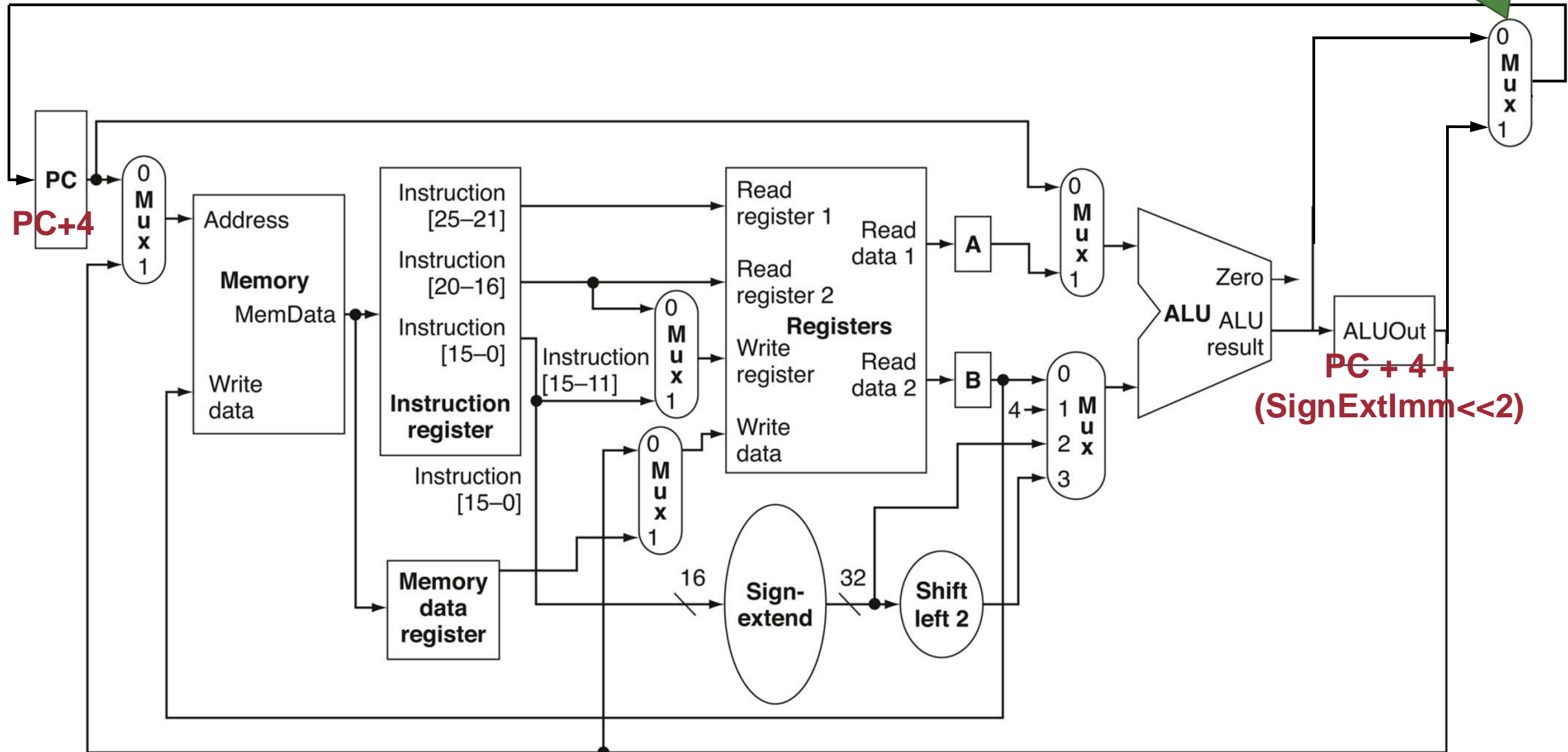


beq – (3) Execution (EXE)

70

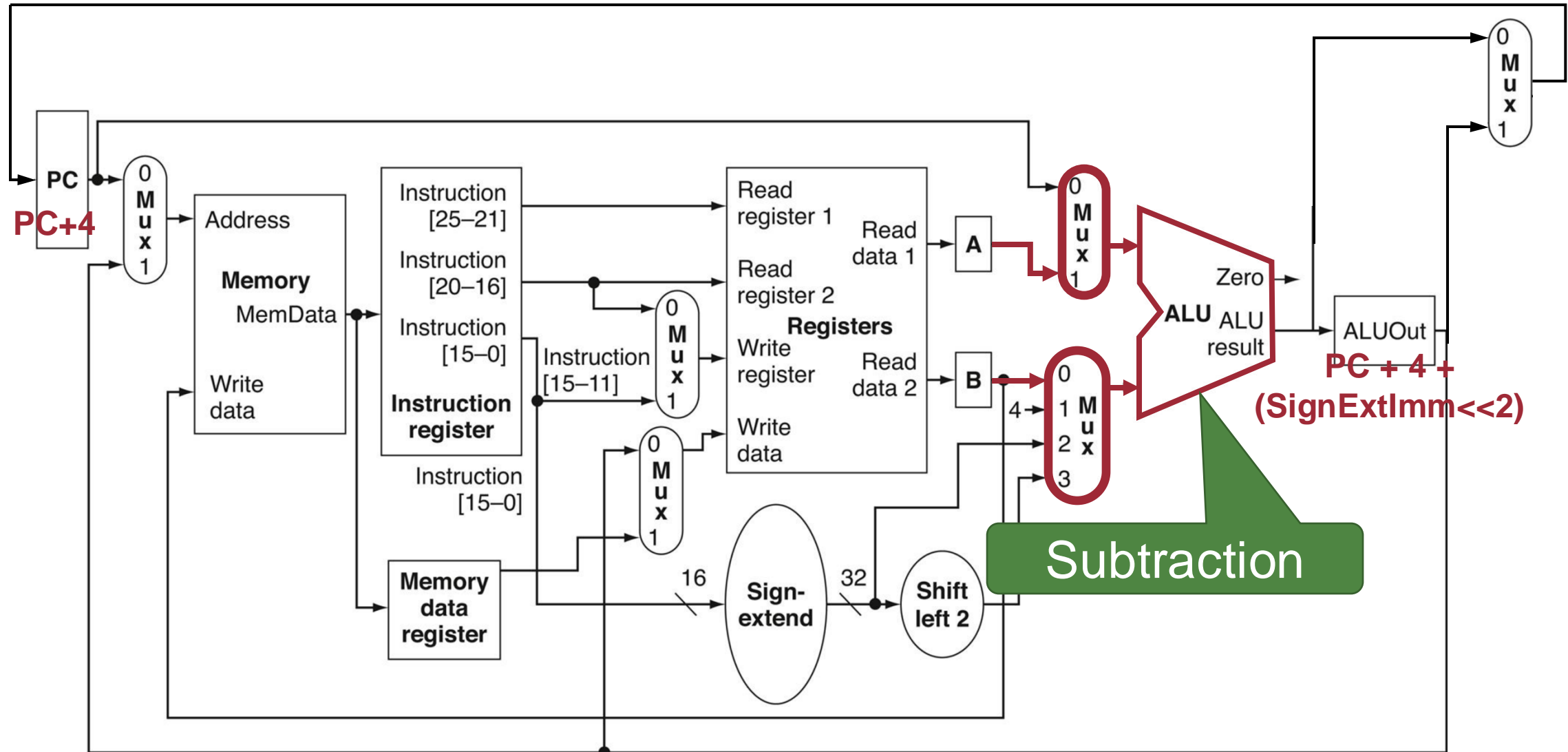


beq – (3) Execution (EXE)

71

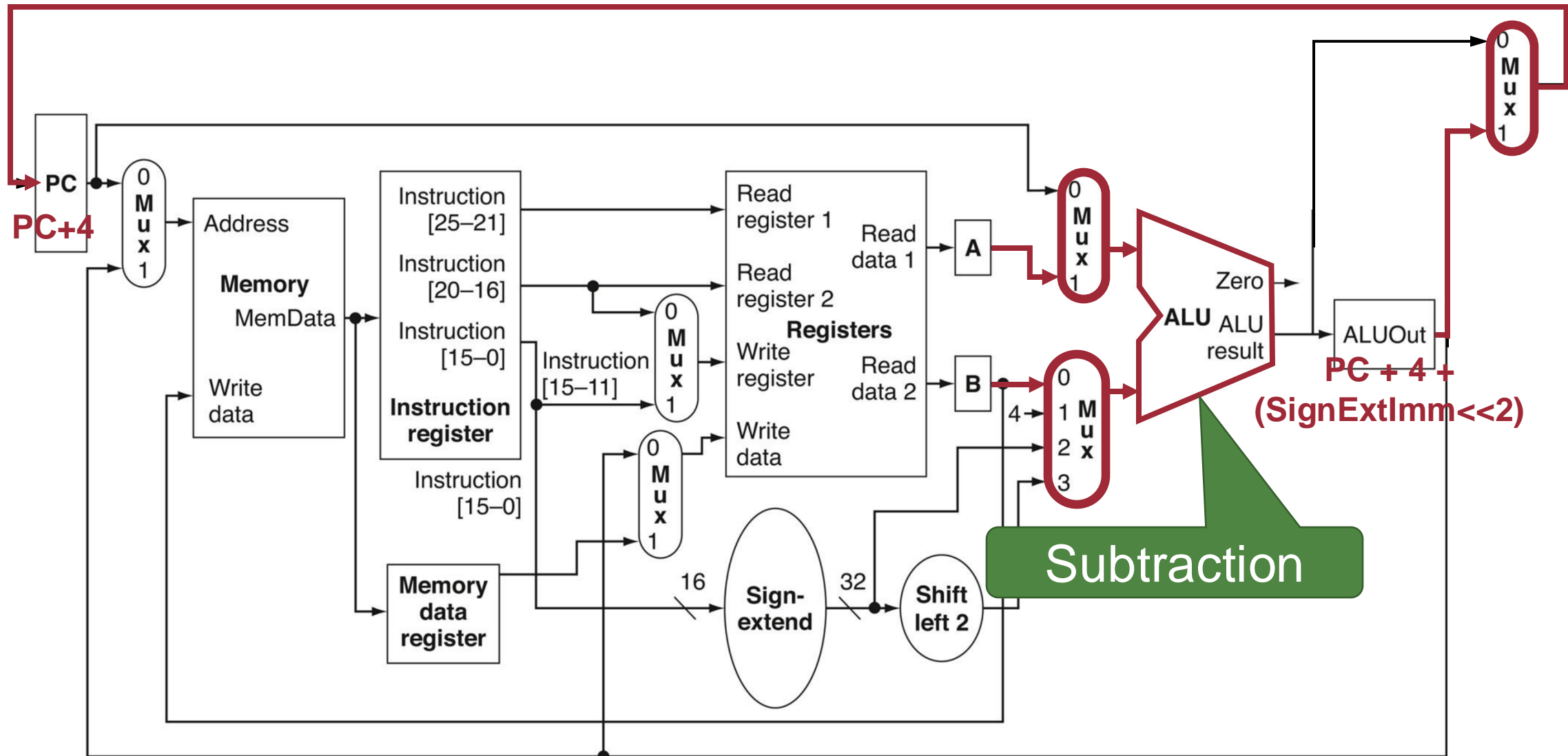


beq – (3) Execution (EXE)

Completion!

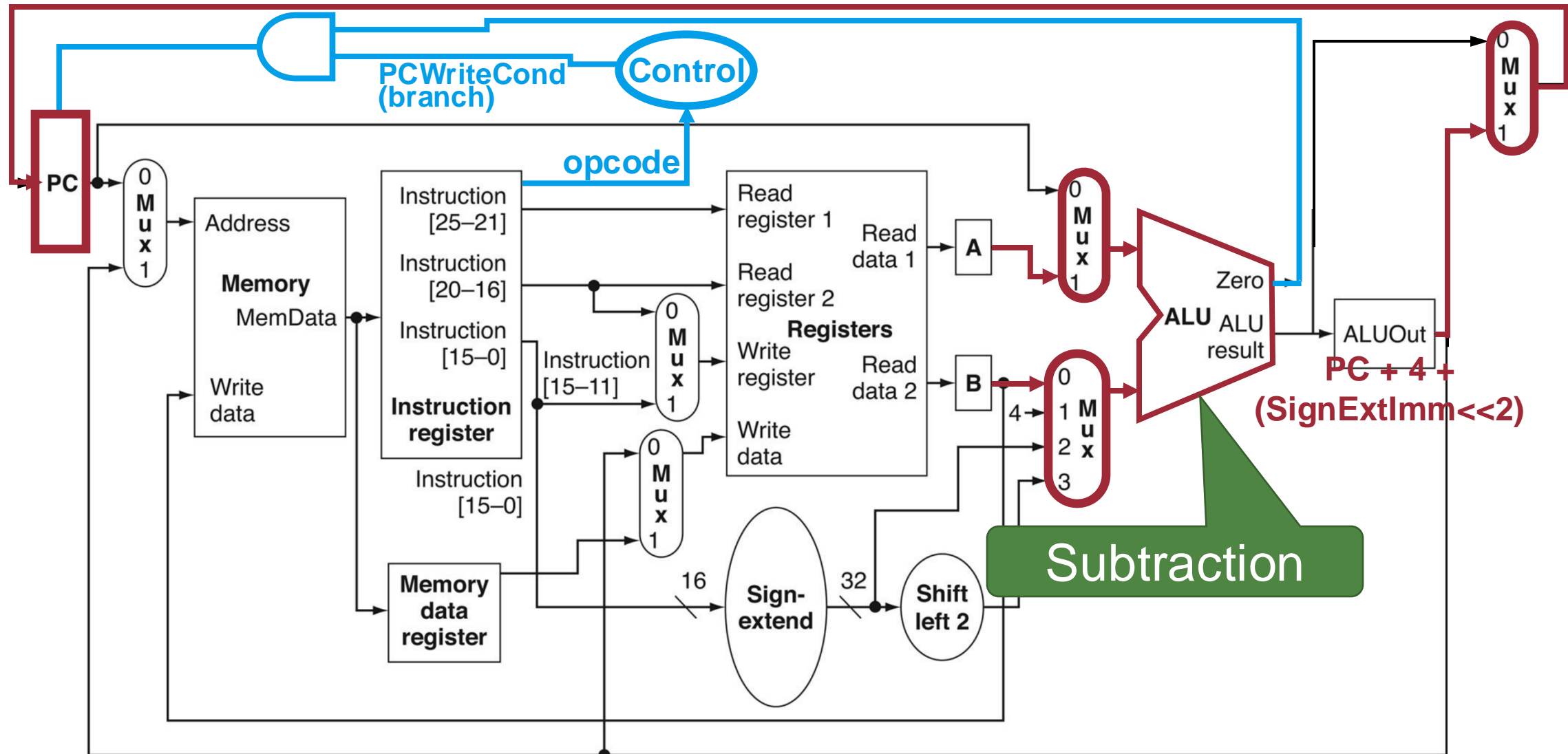


Multicycle Datapath: Complete View

73

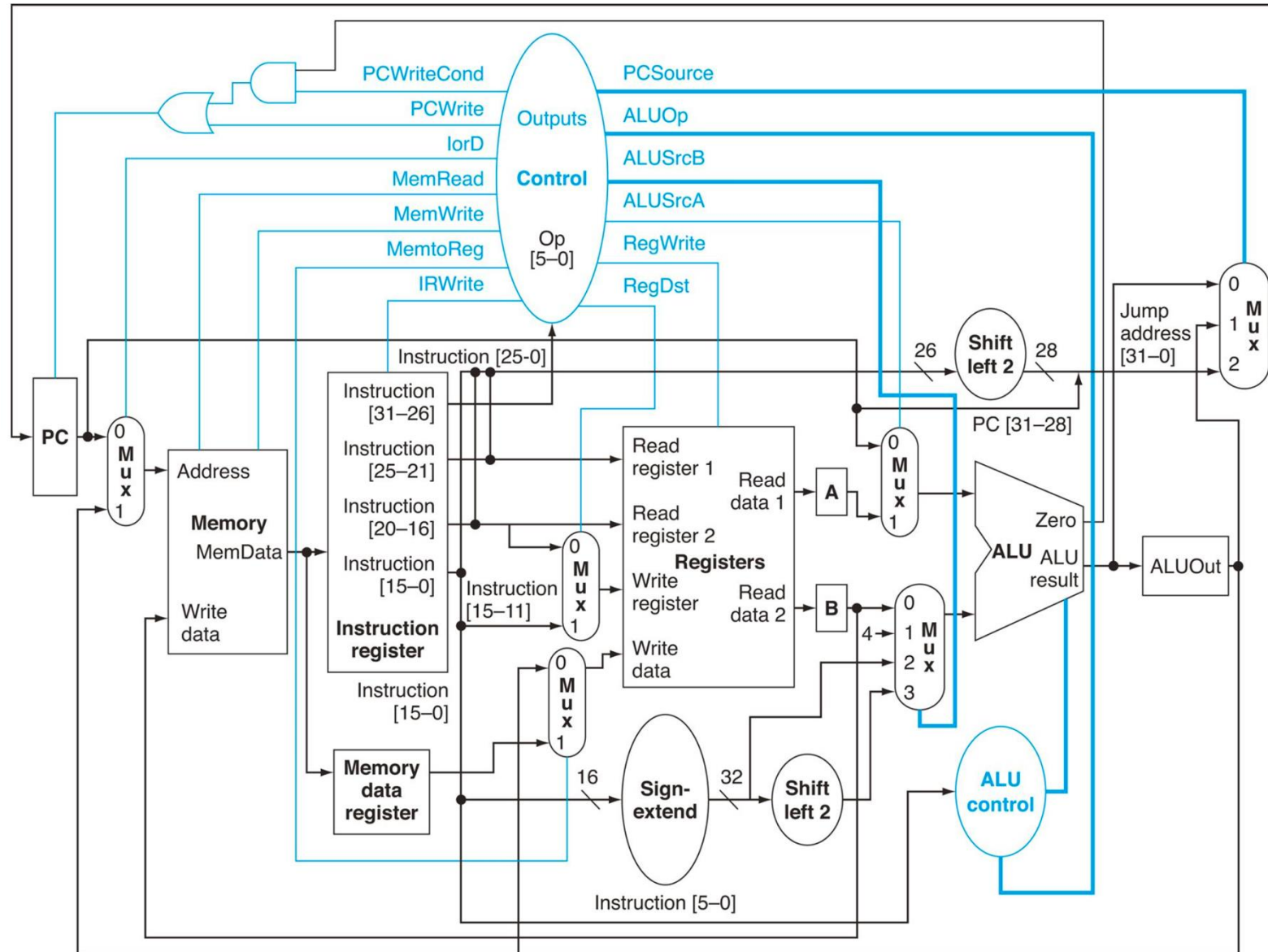

Multicycle Datapath: Jump Instruction

74

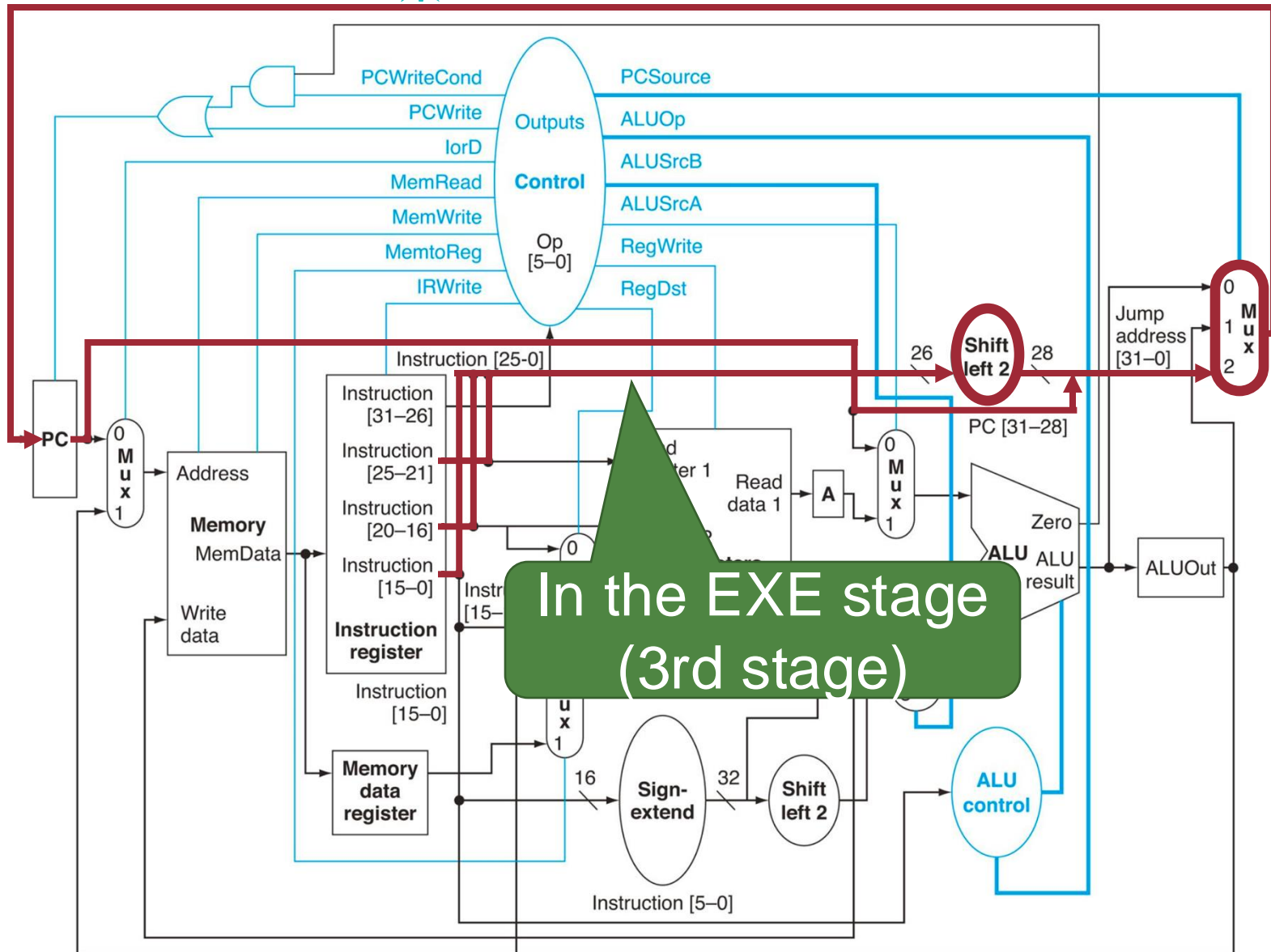

Multicycle Datapath: Summary



Step name	Action for R-type instructions	Action for memory reference instructions	Action for branches	Action for jumps
Instruction fetch	IR \leq Memory[PC] PC \leq PC + 4			

Multicycle Datapath: Summary



Step name	Action for R-type instructions	Action for memory reference instructions	Action for branches	Action for jumps
Instruction fetch	IR \leq Memory[PC] PC \leq PC + 4			
Instruction decode/register fetch	A \leq Reg [IR[25:21]] B \leq Reg [IR[20:16]] ALUOut \leq PC + (sign-extend (IR[15:0]) \ll 2)			

Multicycle Datapath: Summary



Step name	Action for R-type instructions	Action for memory reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR \leq \text{Memory}[PC]$ $PC \leq PC + 4$			
Instruction decode/register fetch	$A \leq \text{Reg}[IR[25:21]]$ $B \leq \text{Reg}[IR[20:16]]$ $ALUOut \leq PC + (\text{sign-extend}(IR[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut \leq A \text{ op } B$	$ALUOut \leq A + \text{sign-extend}(IR[15:0])$	if $(A == B)$ $PC \leq ALUOut$	$PC \leq \{PC[31:28], (IR[25:0]), 2'b00\}$

Multicycle Datapath: Summary



Step name	Action for R-type instructions	Action for memory reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR \leq \text{Memory}[PC]$ $PC \leq PC + 4$			
Instruction decode/register fetch	$A \leq \text{Reg}[IR[25:21]]$ $B \leq \text{Reg}[IR[20:16]]$ $ALUOut \leq PC + (\text{sign-extend}(IR[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut \leq A \text{ op } B$	$ALUOut \leq A + \text{sign-extend}(IR[15:0])$	if $(A == B)$ $PC \leq ALUOut$	$PC \leq \{PC[31:28], (IR[25:0]), 2'b00\}$
Memory access or R-type completion	$\text{Reg}[IR[15:11]] \leq ALUOut$	Load: $MDR \leq \text{Memory}[ALUOut]$ or Store: $\text{Memory}[ALUOut] \leq B$		


Multicycle Datapath: Summary



Step name	Action for R-type instructions	Action for memory reference instructions	Action for branches	Action for jumps
Instruction fetch	$IR \leq \text{Memory}[PC]$ $PC \leq PC + 4$			
Instruction decode/register fetch	$A \leq \text{Reg}[IR[25:21]]$ $B \leq \text{Reg}[IR[20:16]]$ $ALUOut \leq PC + (\text{sign-extend}(IR[15:0]) \ll 2)$			
Execution, address computation, branch/jump completion	$ALUOut \leq A \text{ op } B$	$ALUOut \leq A + \text{sign-extend}(IR[15:0])$	if $(A == B)$ $PC \leq ALUOut$	$PC \leq \{PC[31:28], (IR[25:0]), 2'b00\}$
Memory access or R-type completion	$\text{Reg}[IR[15:11]] \leq ALUOut$	Load: $MDR \leq \text{Memory}[ALUOut]$ or Store: $\text{Memory}[ALUOut] \leq B$		
Memory read completion		Load: $\text{Reg}[IR[20:16]] \leq MDR$		

Multicycle Implementation: Control Signals

Introduced by the newly added mux

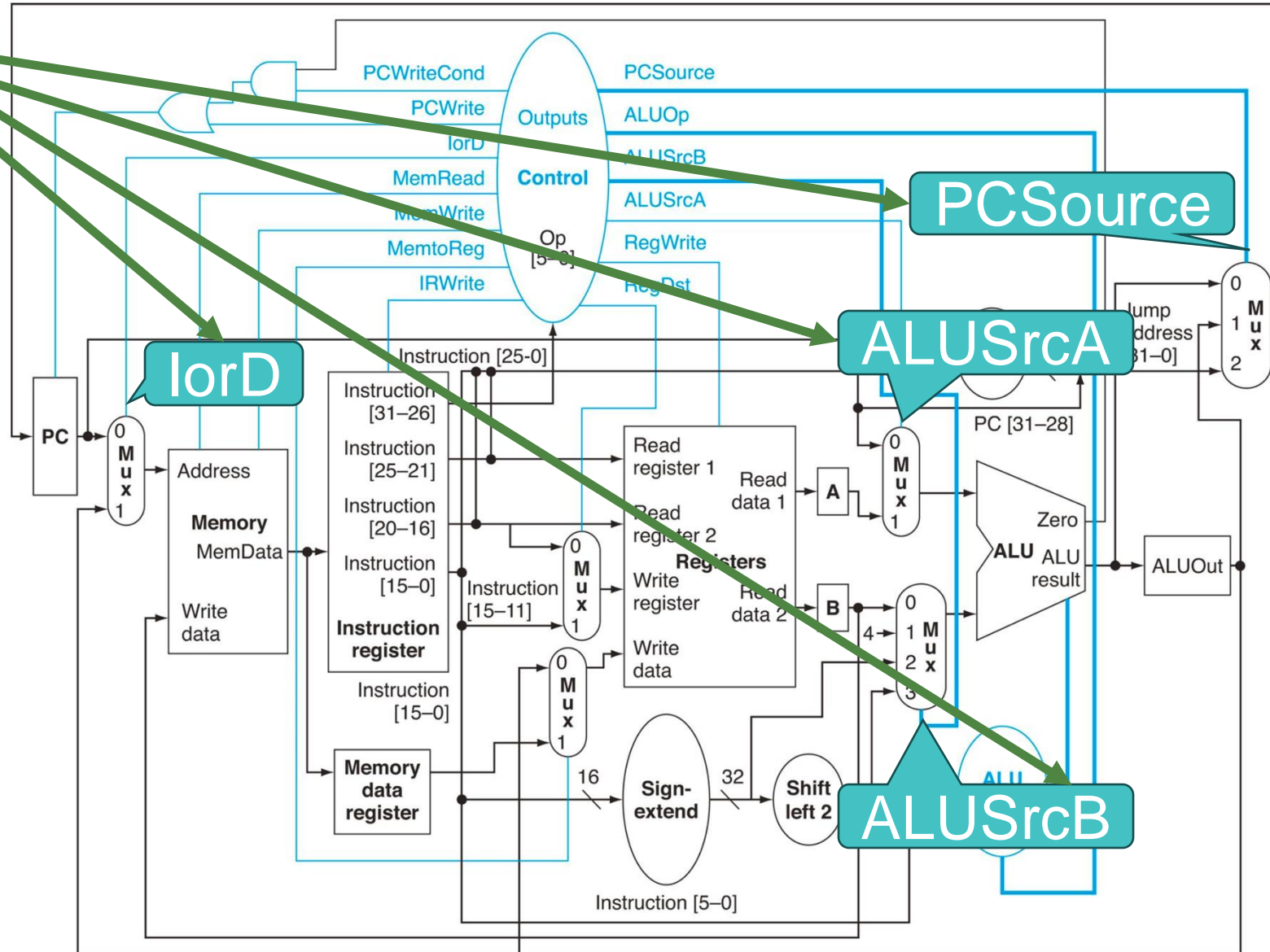


Multicycle Implementation: Control Signals


31

PCWrite

 Single-cycle implementation:
we don't need a PC write signal because
it is updated on every clock cycle




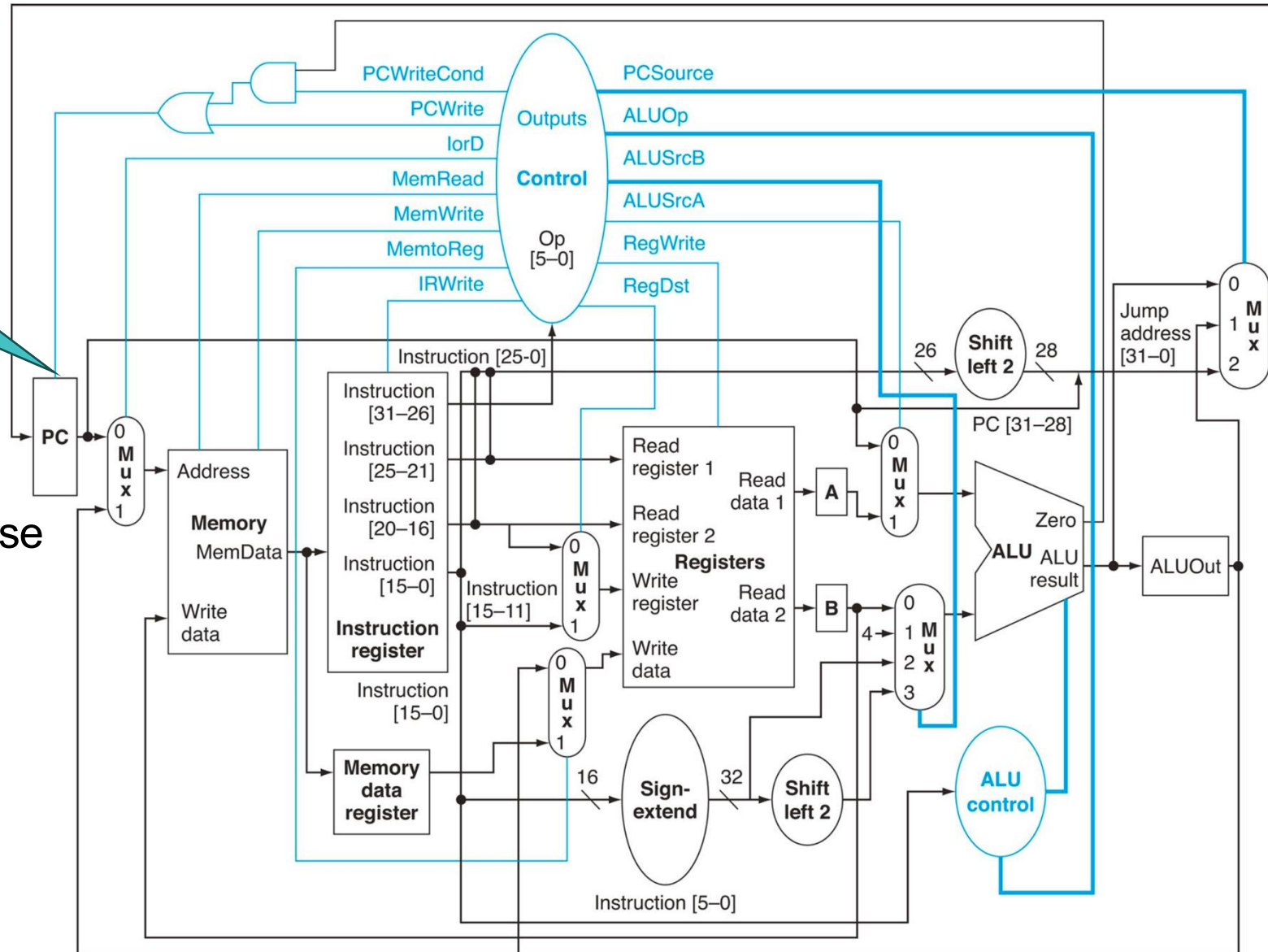Multi-cycle implementation:
The PC should be updated *only in a specific cycle* → Introduce a PC write signal



Multicycle Implementation: Control Signals

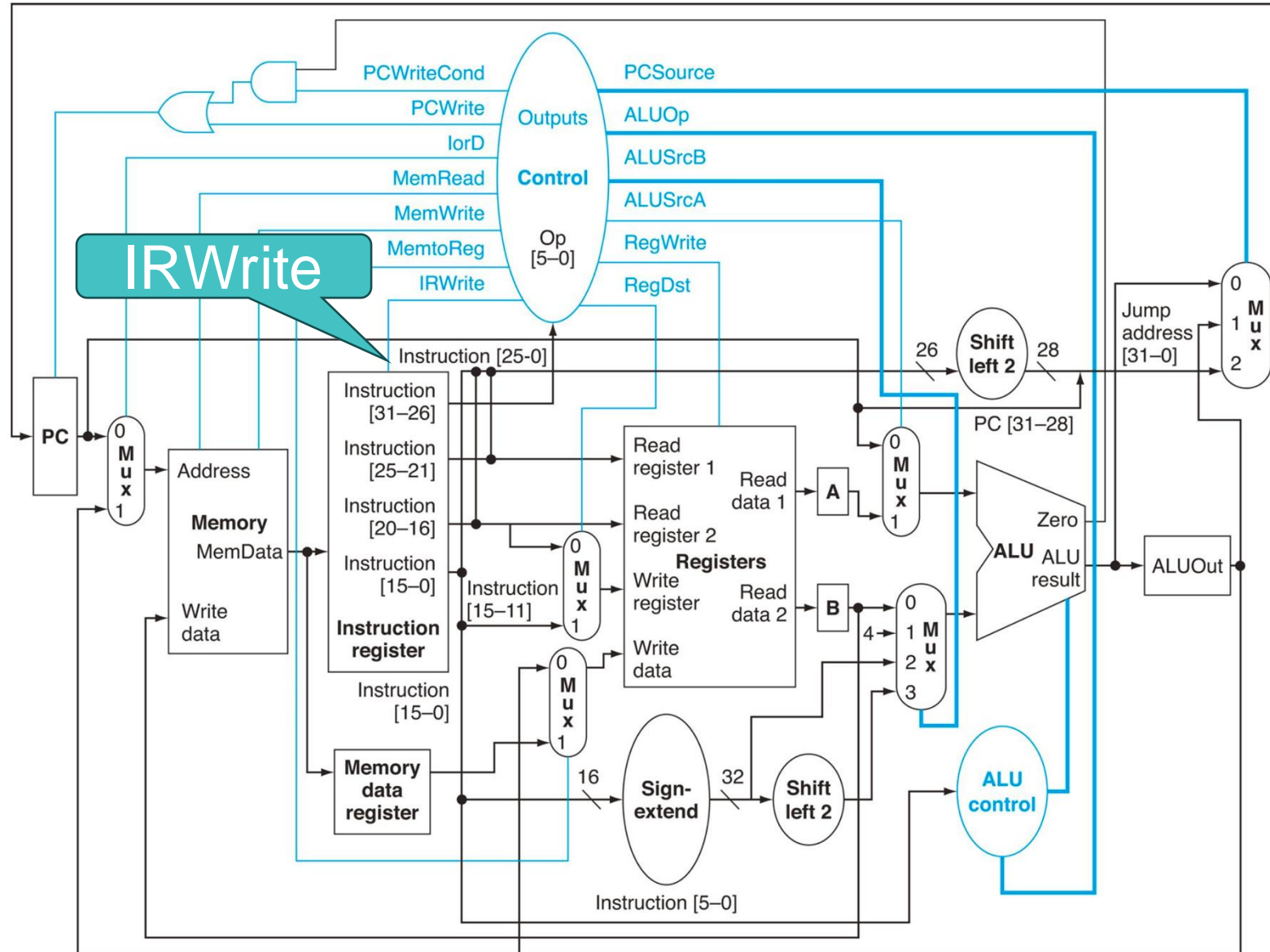The instruction register should be updated only in the IF stage →
Introduce a IR write signal



1-bit Control Signals



Signal name	Effect when deasserted	Effect when asserted
RegDst	The register file destination number for the Write register comes from the rt field.	The register file destination number for the Write register comes from the rd field.
RegWrite	None.	The general-purpose register selected by the Write register number is written with the value of the Write data input.
ALUSrcA	The first ALU operand is the PC.	The first ALU operand comes from the A register.
MemRead	None.	Content of memory at the location specified by the Address input is put on Memory data output.
MemWrite	None.	Memory contents at the location specified by the Address input is replaced by the value on the Write data input.
MemtoReg	The value fed to the register file Write data input comes from ALUOut.	The value fed to the register file Write data input comes from the MDR.
IorD	The PC is used to supply the address to the memory unit.	ALUOut is used to supply the address to the memory unit.
IRWrite	None.	The output of the memory is written into the IR.
PCWrite	None.	The PC is written; the source is controlled by PCSource.
PCWriteCond	None.	The PC is written if the Zero output from the ALU is also active.

2-bit Control Signals




Signal name	Value (binary)	Effect
ALUOp	00	The ALU performs an add operation.
	01	The ALU performs a subtract operation.
	10	The funct field of the instruction determines the ALU operation.
ALUSrcB	00	The second input to the ALU comes from the B register.
	01	The second input to the ALU is the constant 4.
	10	The second input to the ALU is the sign-extended, lower 16 bits of the IR.
	11	The second input to the ALU is the sign-extended, lower 16 bits of the IR shifted left 2 bits.
PCSource	00	Output of the ALU ($PC + 4$) is sent to the PC for writing.
	01	The contents of ALUOut (the branch target address) are sent to the PC for writing.
	10	The jump target address ($IR[25:0]$ shifted left 2 bits and concatenated with $PC + 4[31:28]$) is sent to the PC for writing.

Multicycle Implementation: Control


85

Let's look at the Control!

 Single-cycle implementation:
The control unit is a combinational circuit







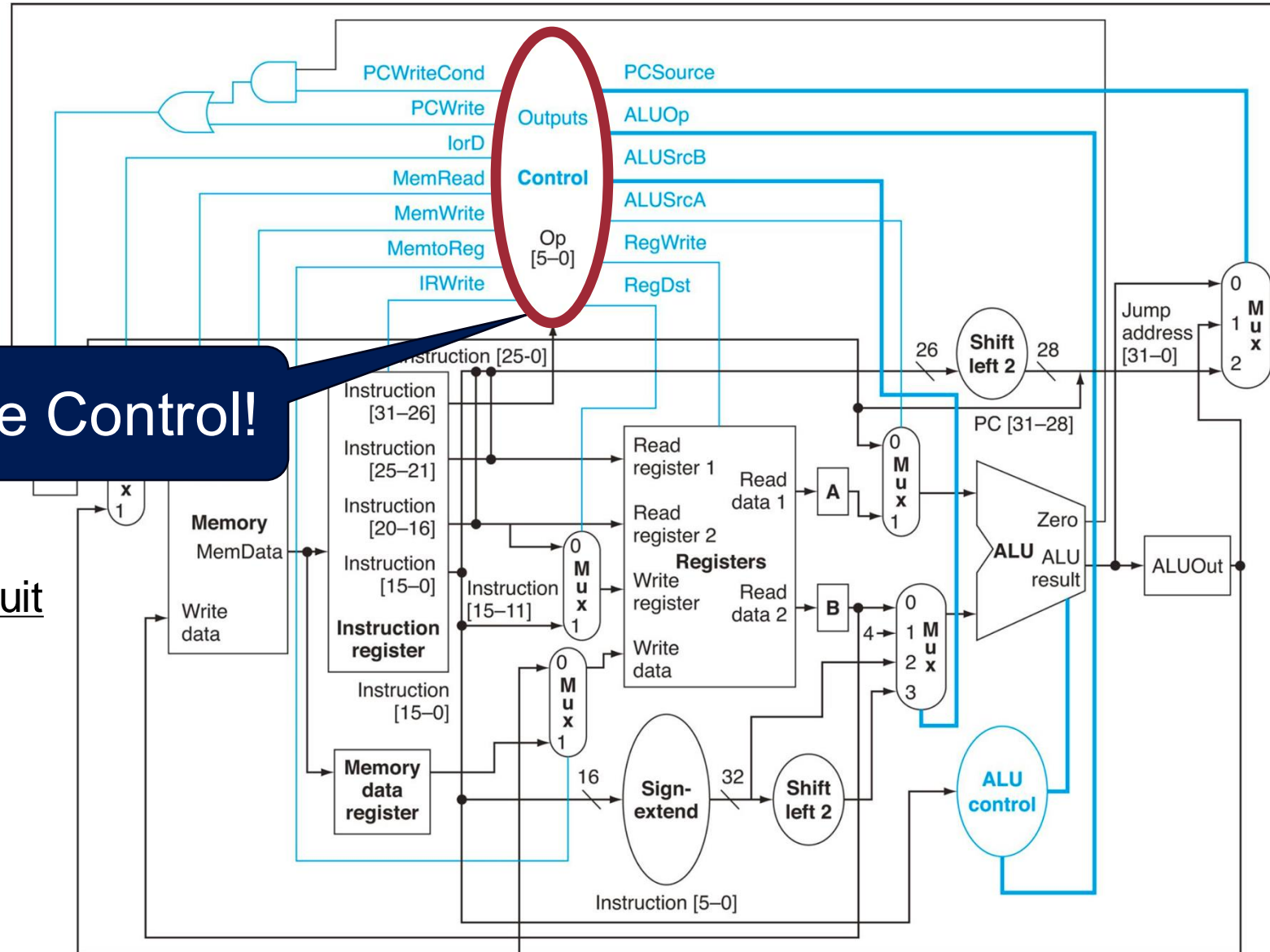Multi-cycle implementation:
The control unit is a sequential circuit




Motivation: Multicycle Control Unit

86

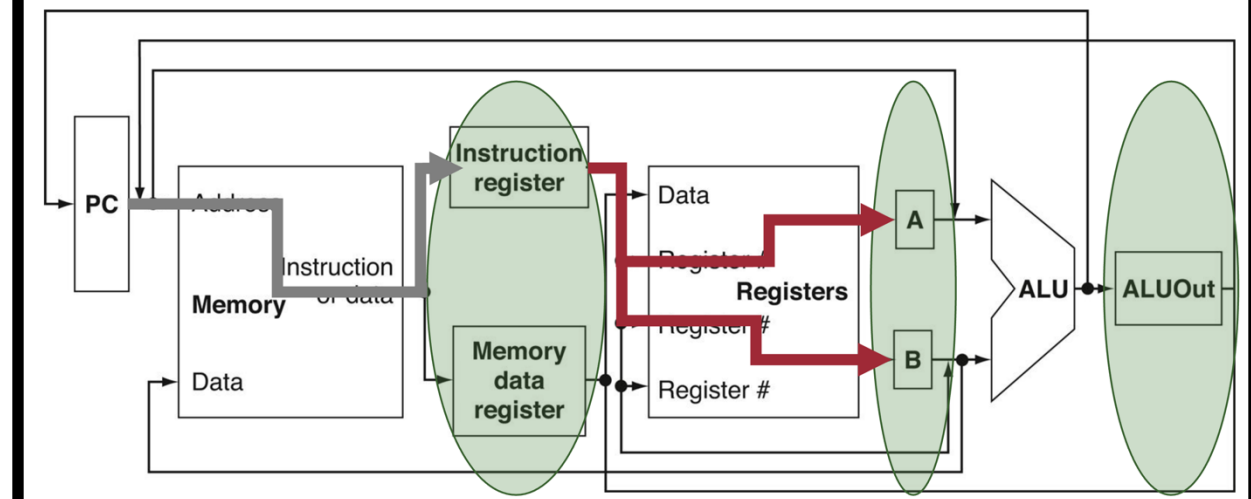 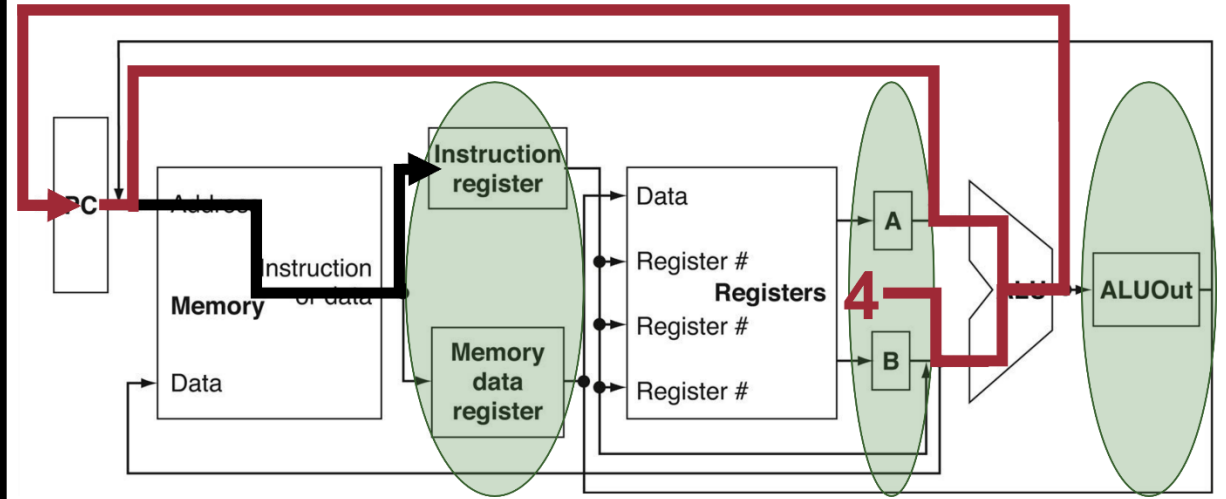 

Motivation: Multicycle Control Unit

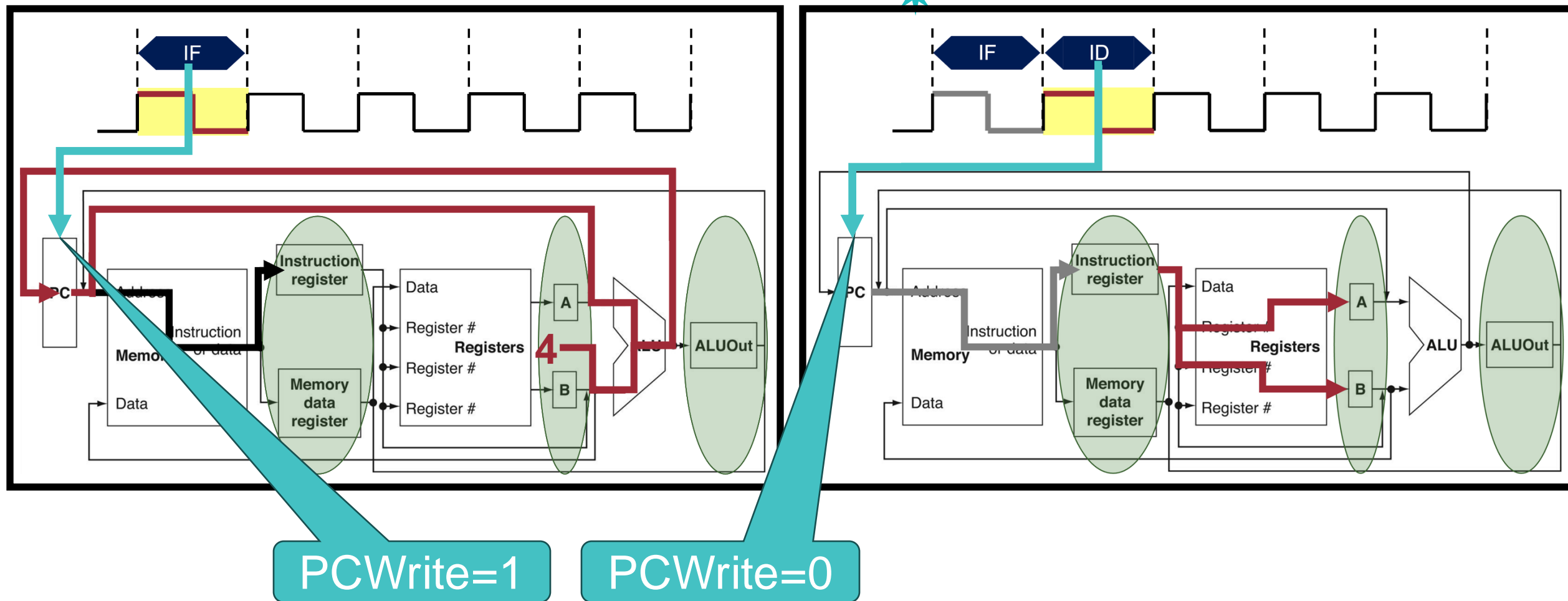

Even for the same instruction, the required control signals vary depending on the cycle


Idea: maintain states (signals) for each cycle

Multicycle Control Unit: Use Finite State Machine




Multicycle Control Unit: Use Finite State Machine

39

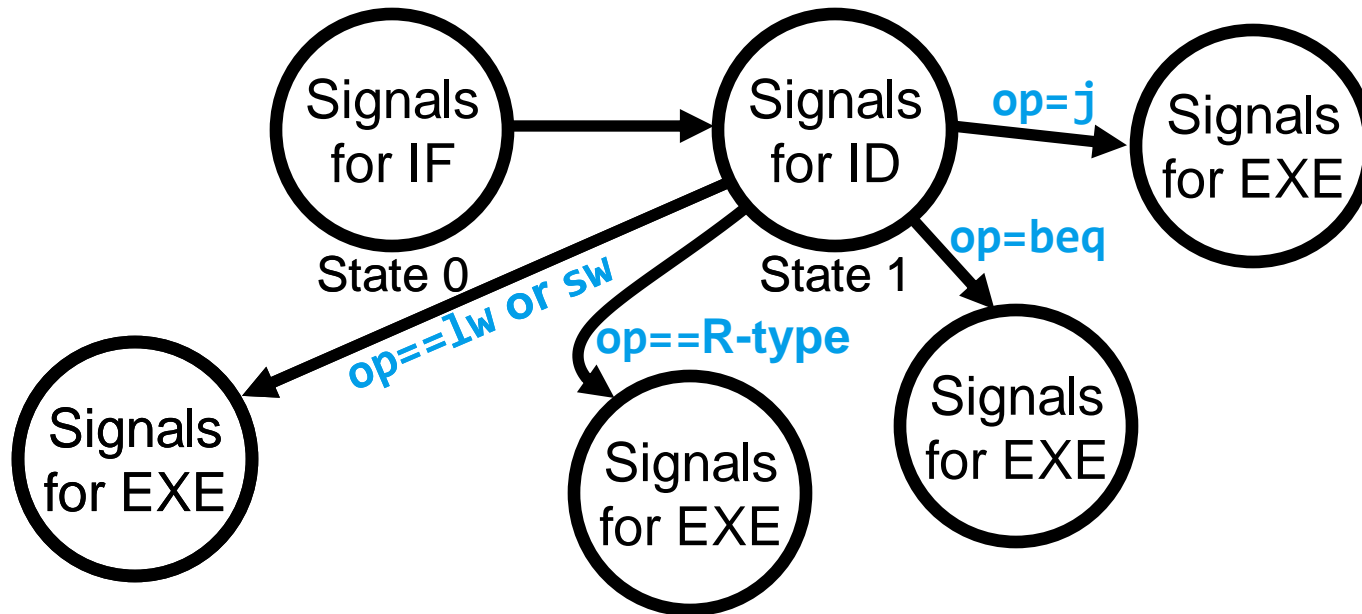


Multicycle Control Unit: Use Finite State Machine

20

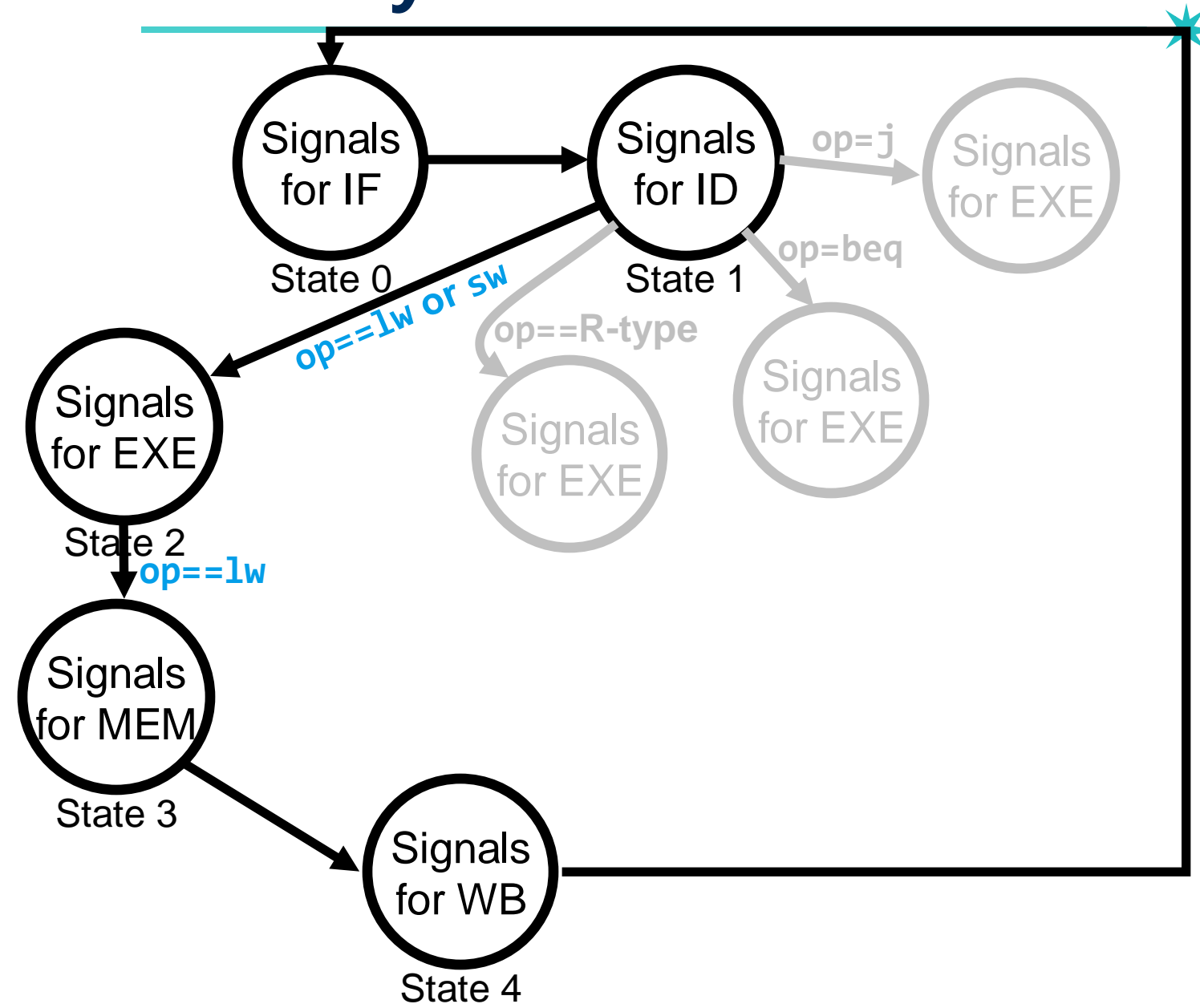


Multicycle Control Unit: Use Finite State Machine

91

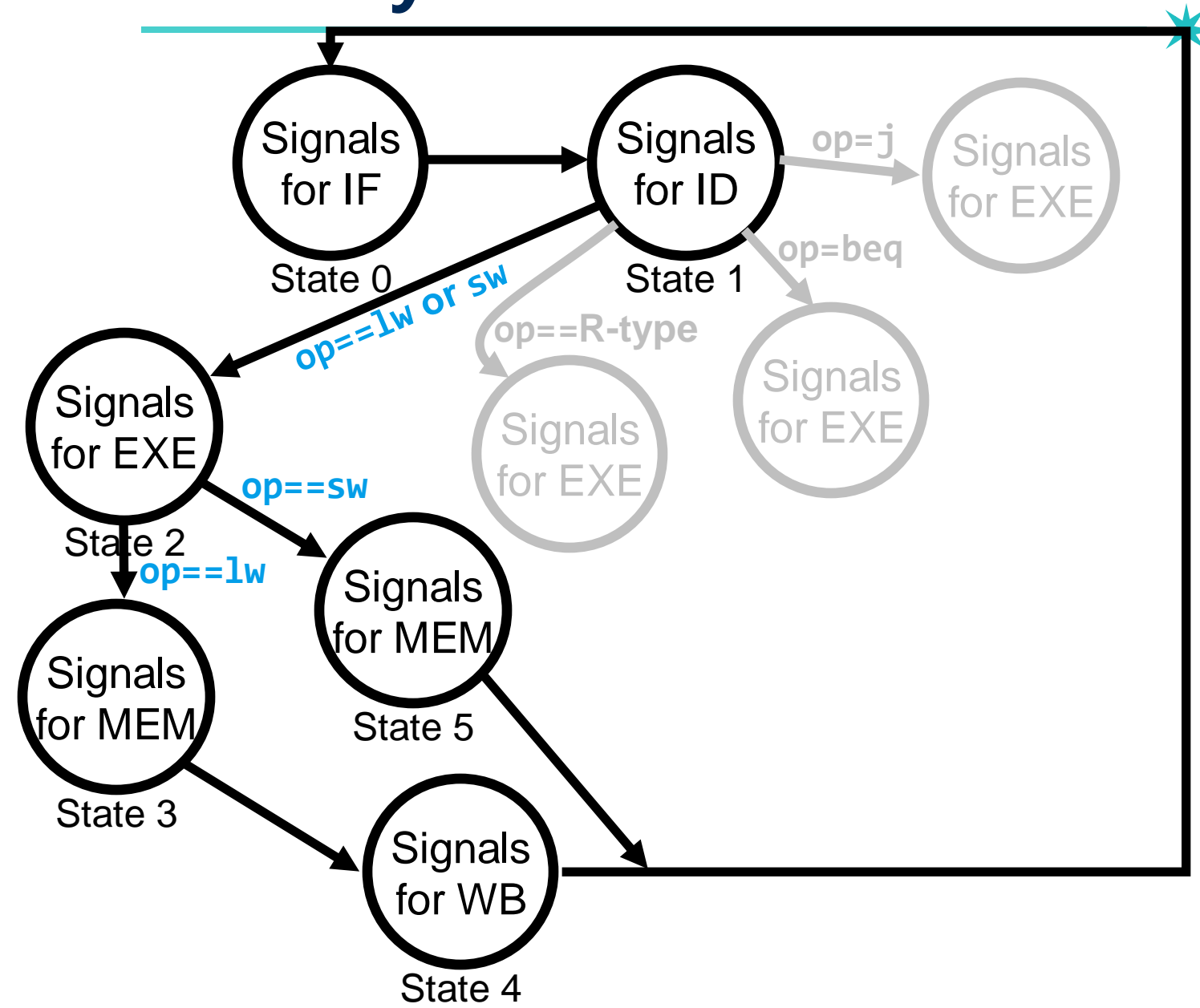


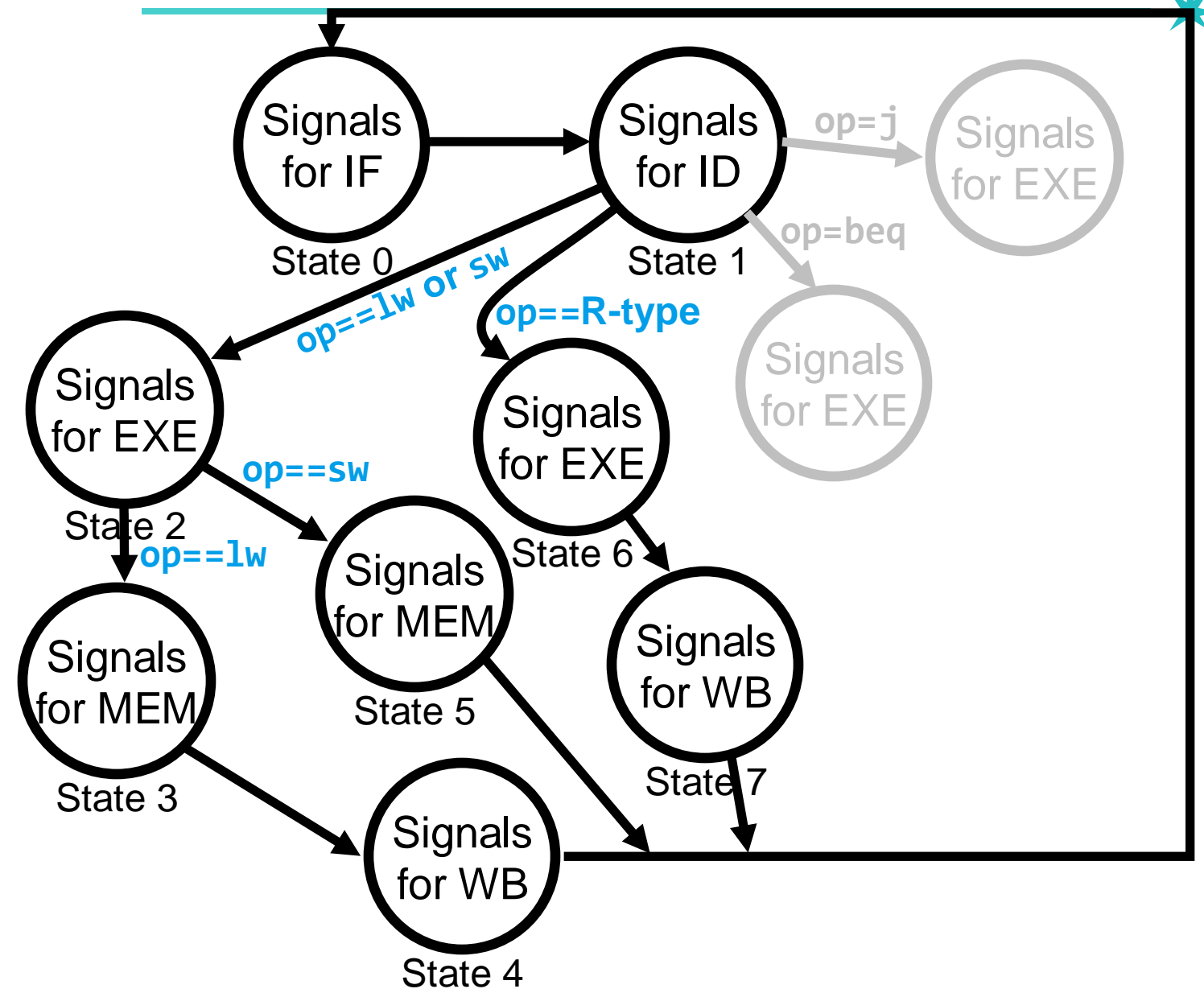Multicycle Control Unit: Use Finite State Machine




Multicycle Control Unit: Use Finite State Machine

23


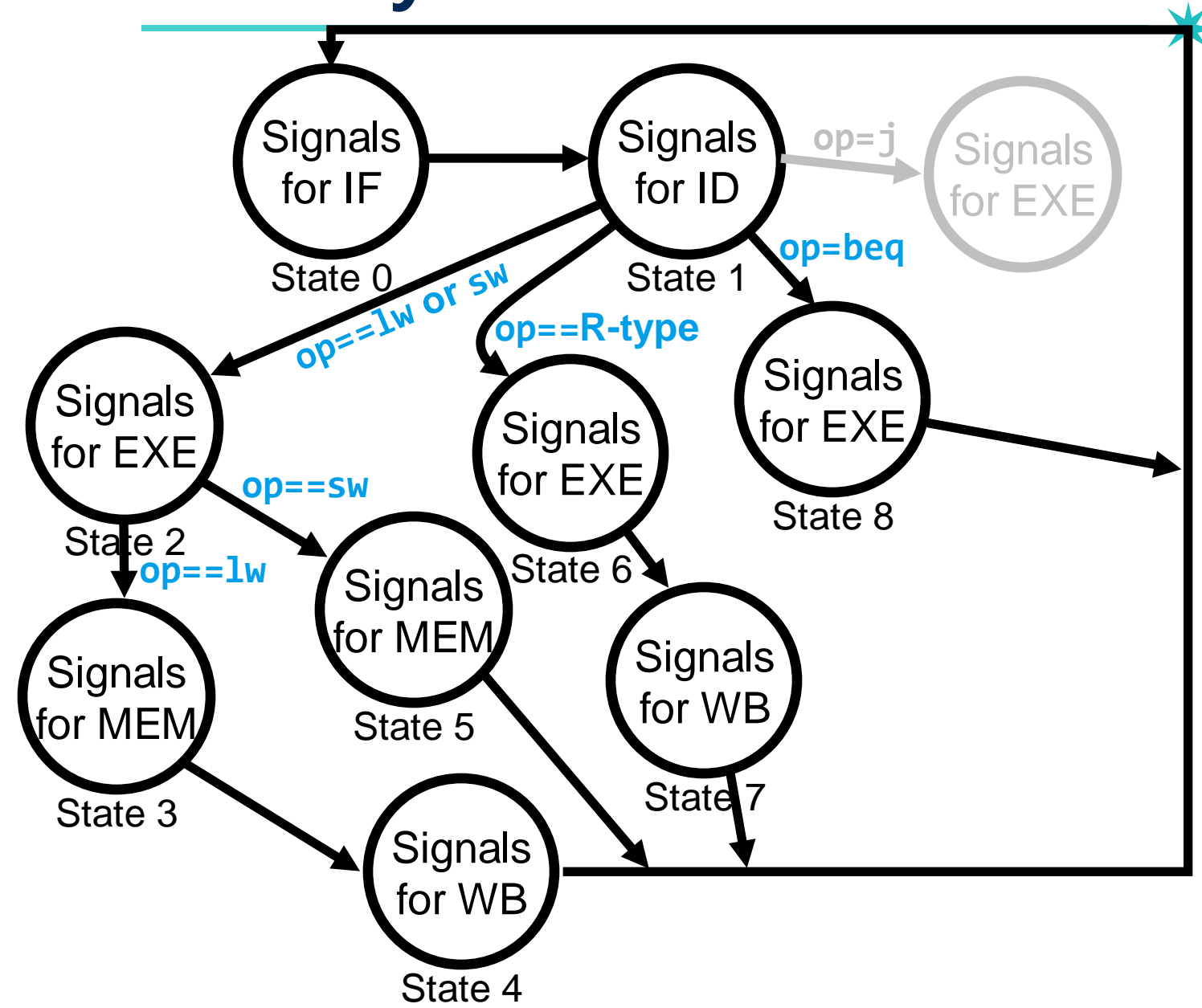


Multicycle Control Unit: Use Finite State Machine

94


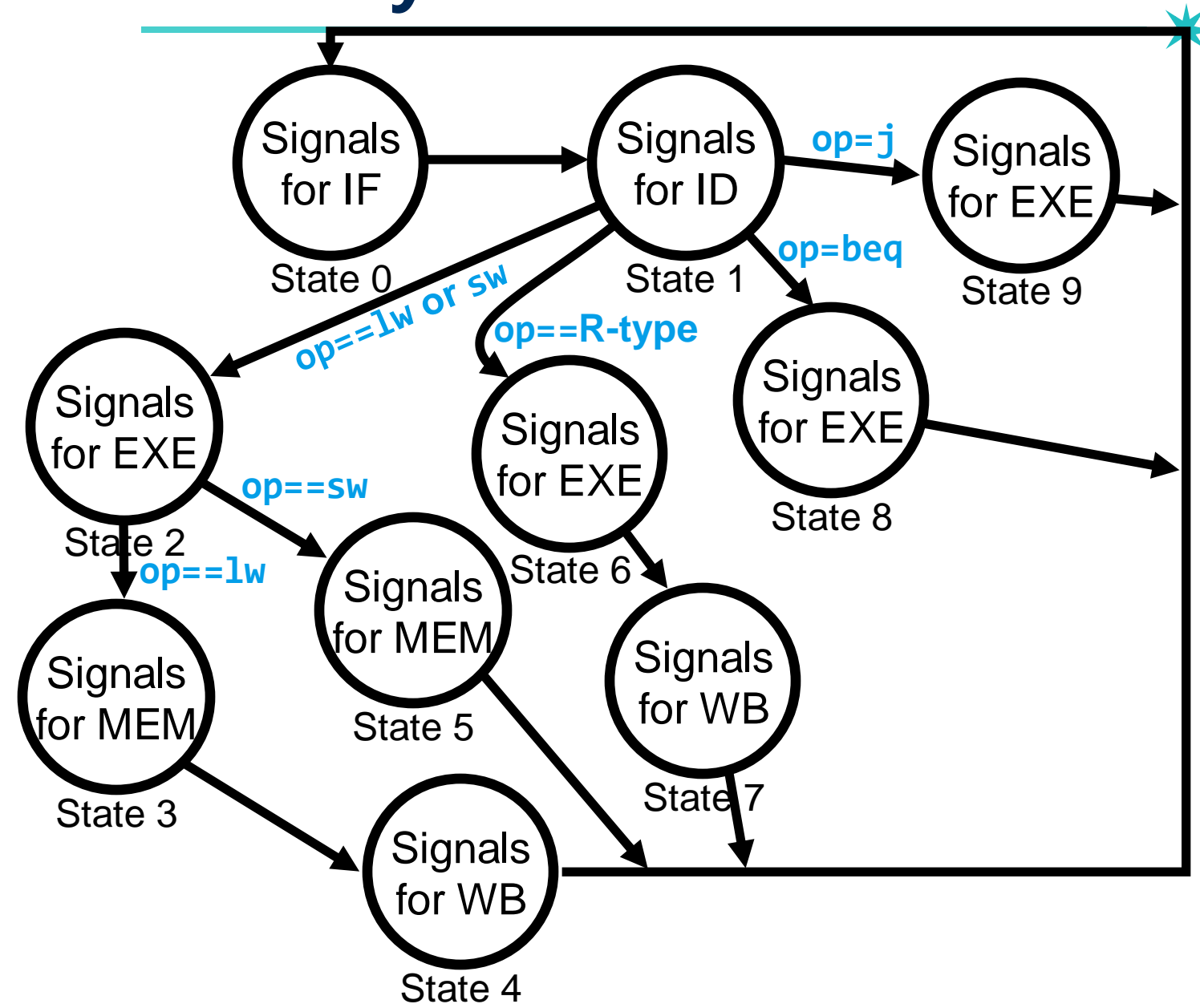


Control Unit Details

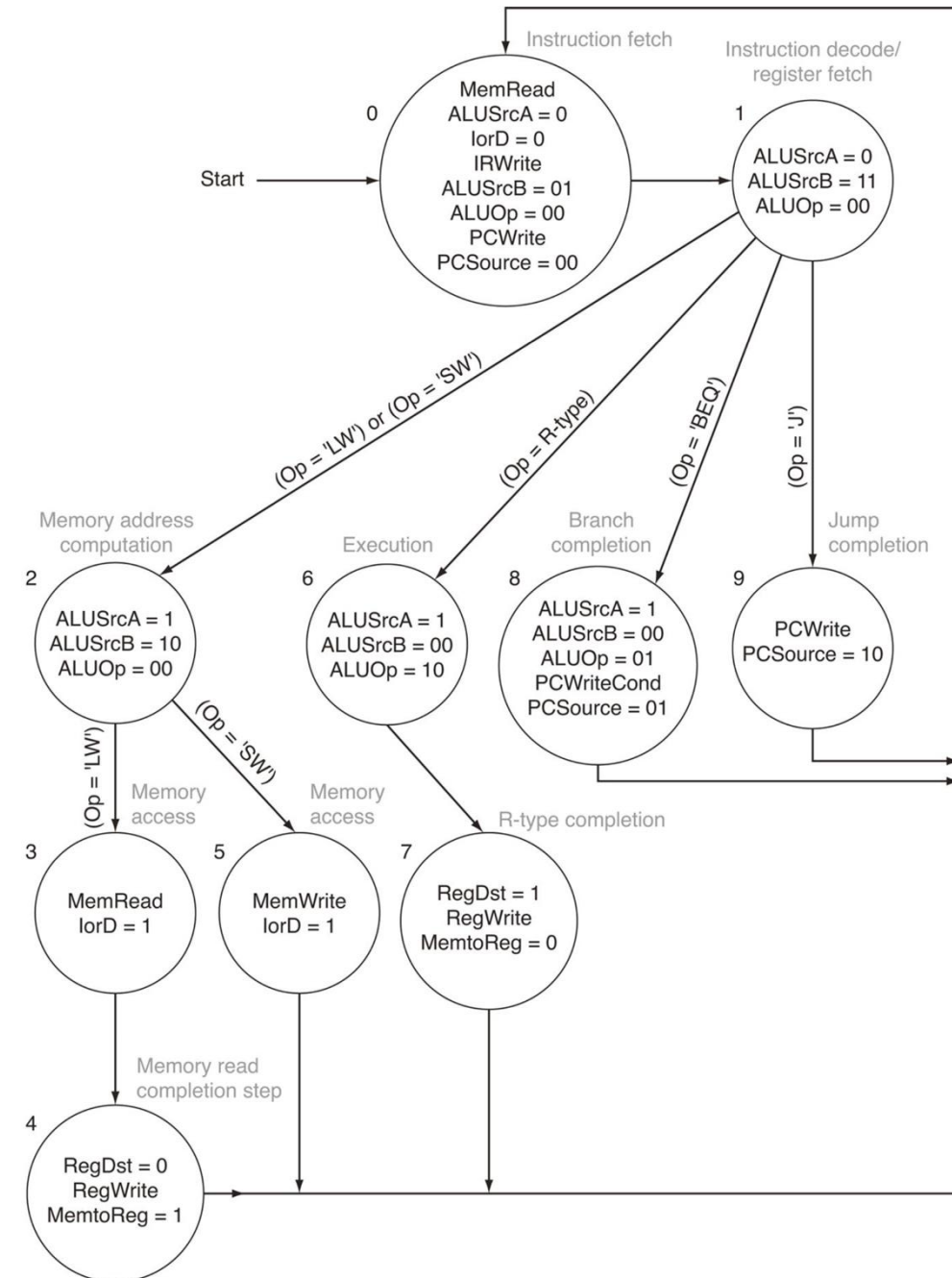
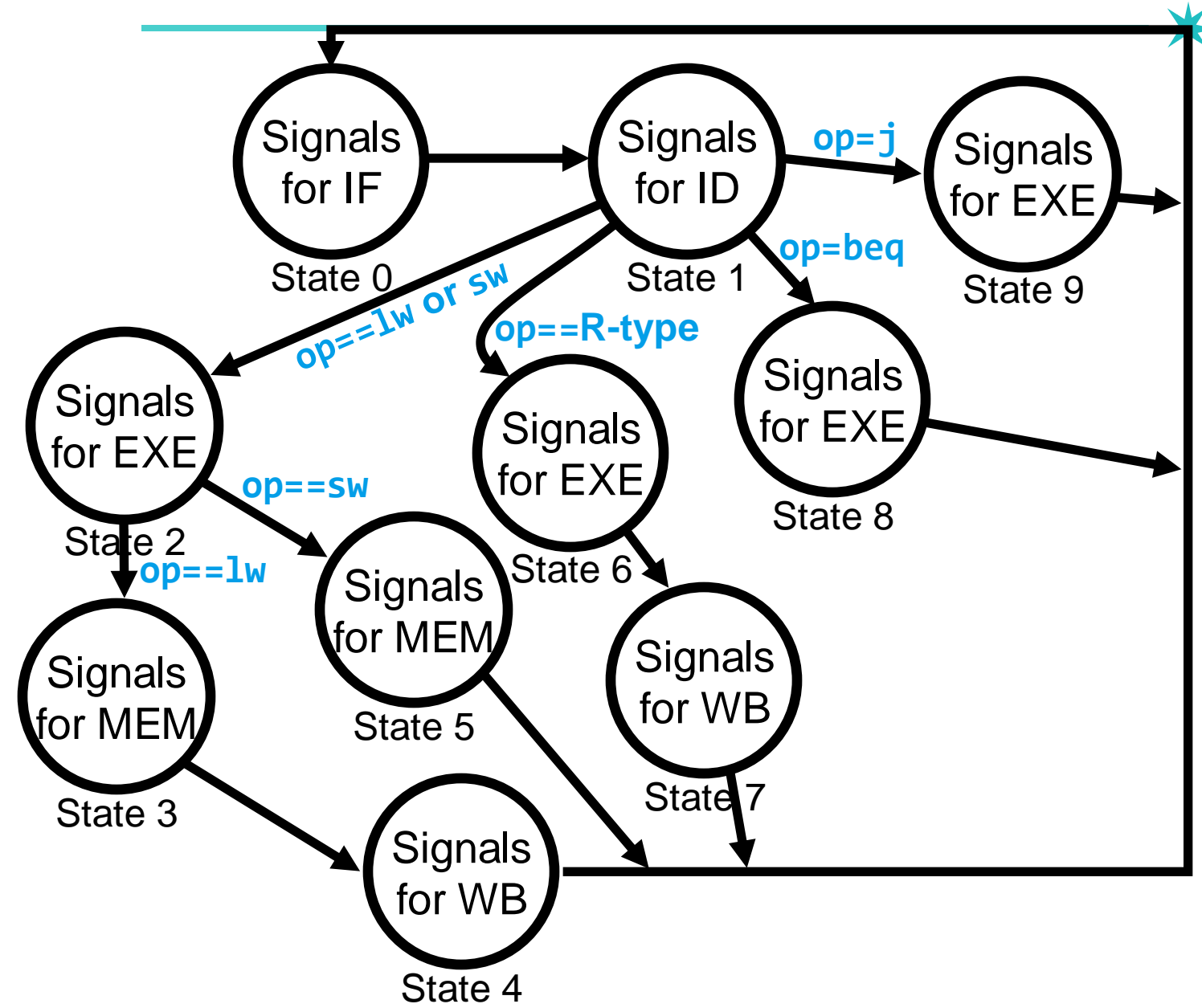


Control Example



96

 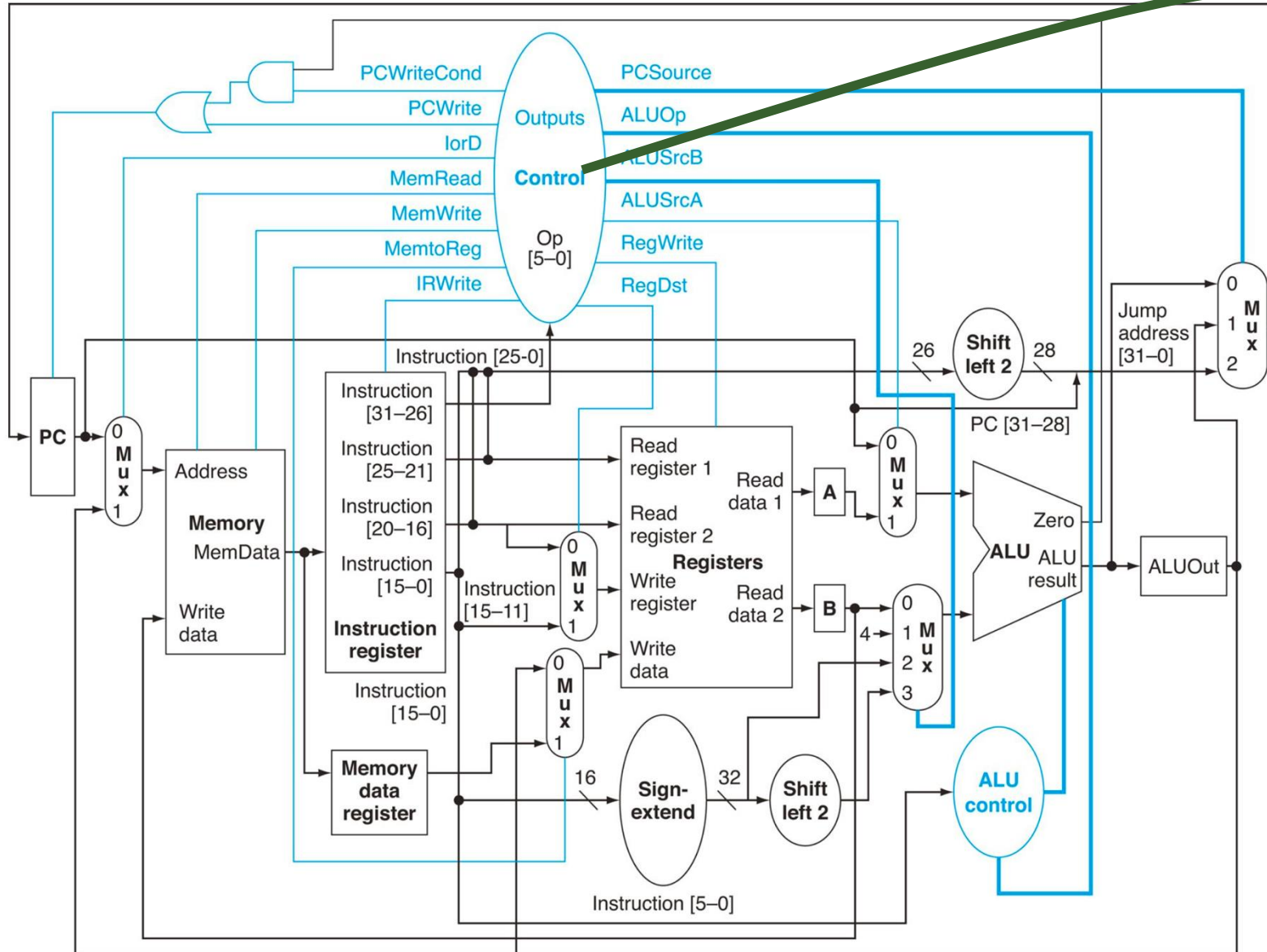



Example: 1st Cycle (Instruction Fetch)

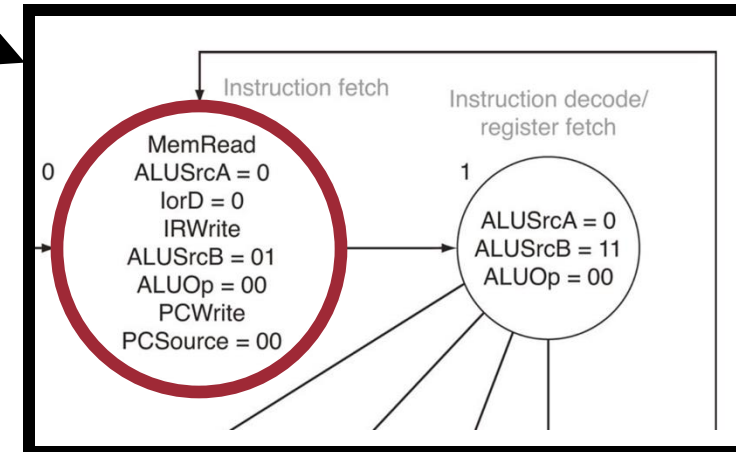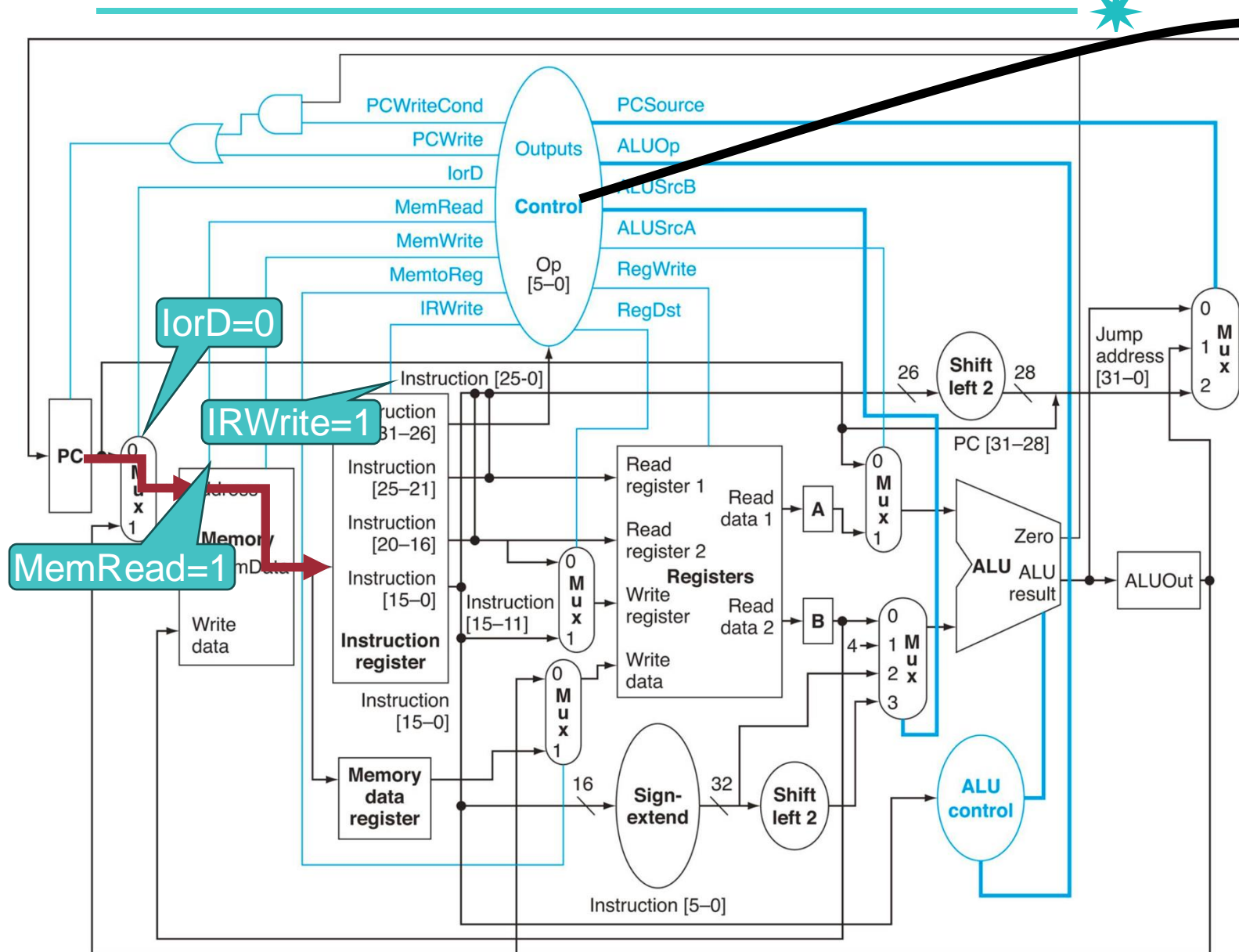

Example: 1st Cycle (Instruction Fetch)

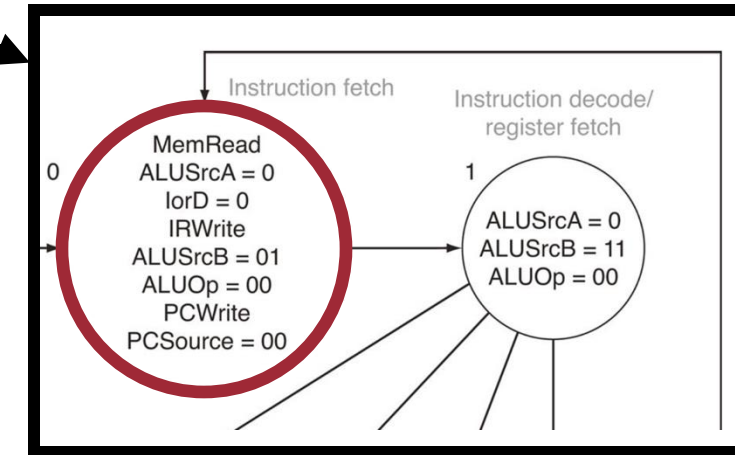
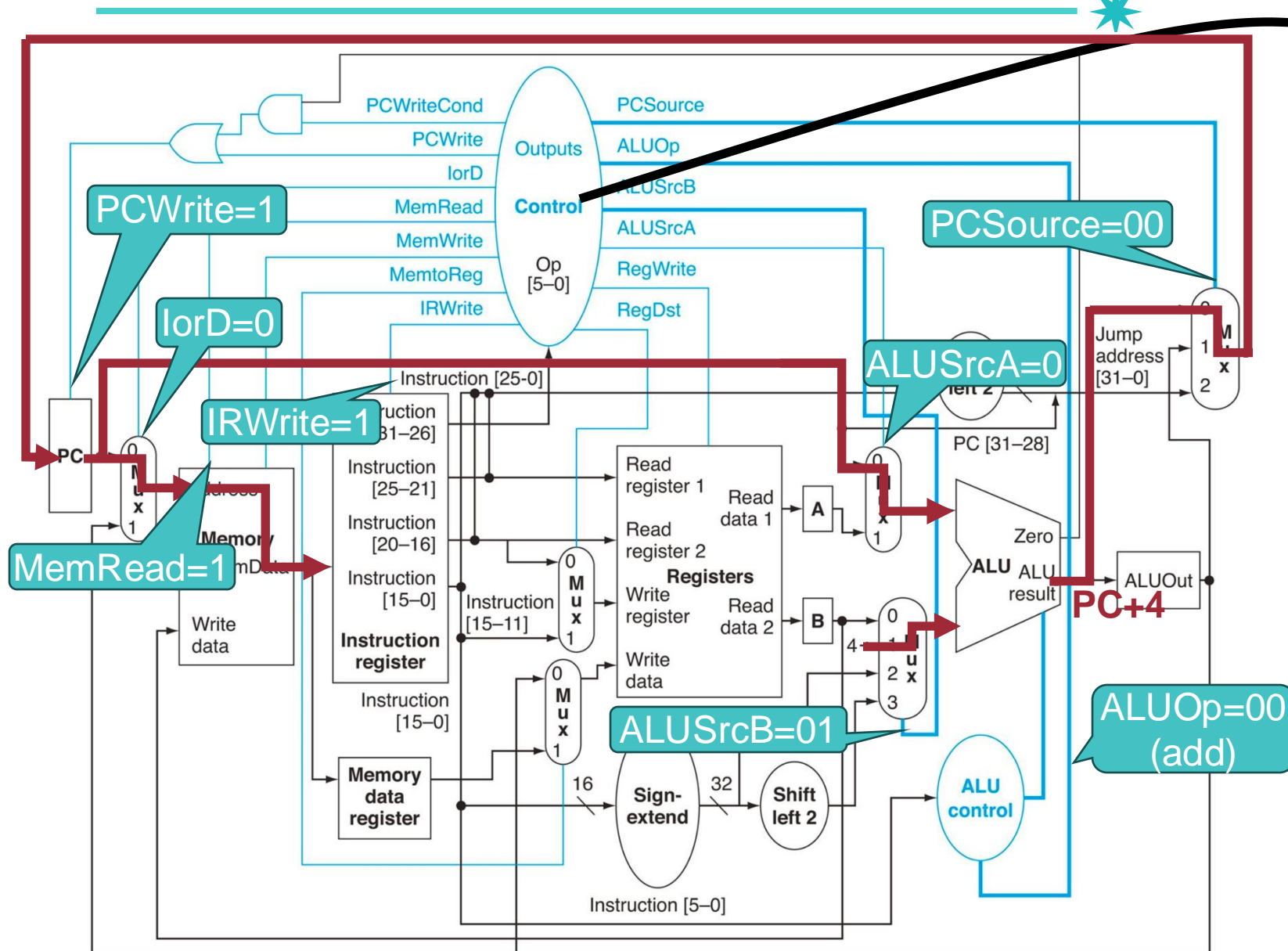


Example: 1st Cycle (Instruction Fetch)

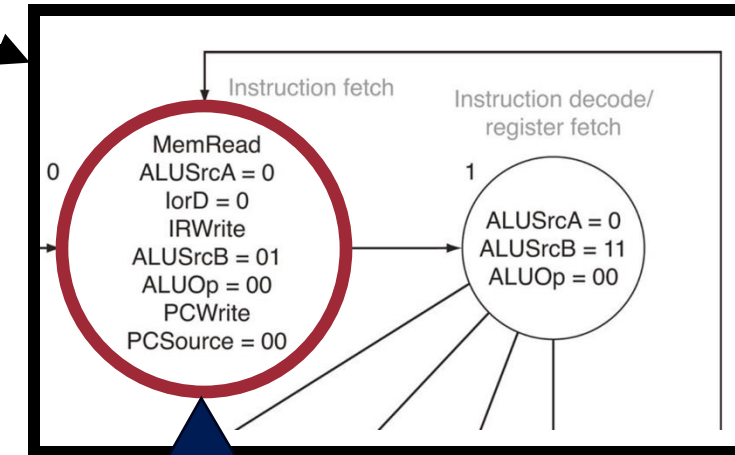 

Signals that are not specified as 0 (deasserted)

Example: 2nd Cycle (Instruction Decode)

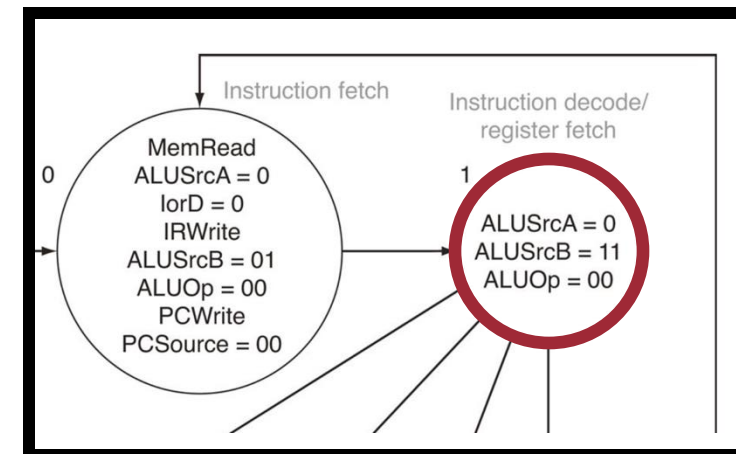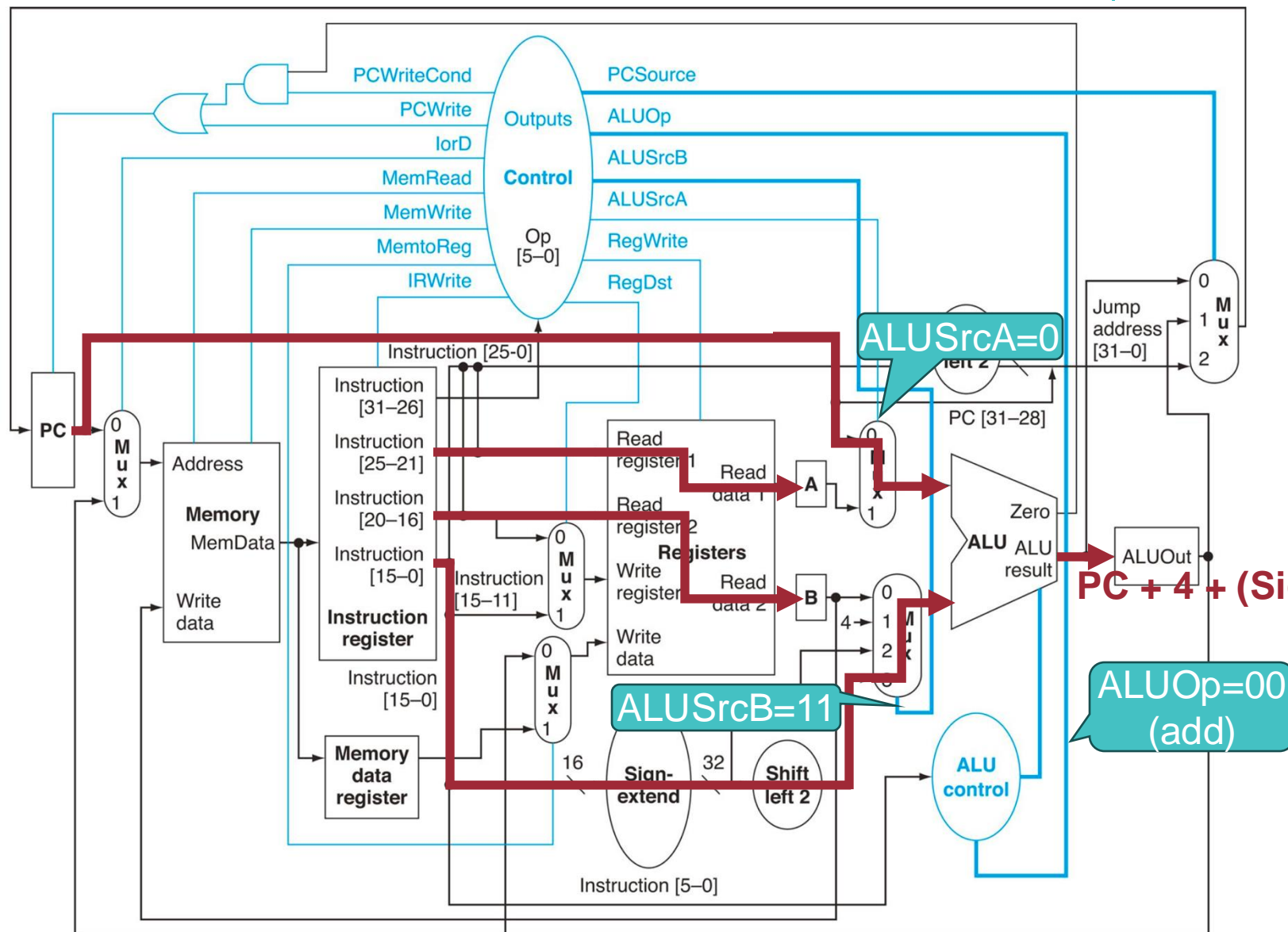

Multicycle Implementation: Advantages

102

Compared with single-cycle implementation, performance can be **increased** due to:

- Clock cycle period ↓
- Different instructions take different numbers of cycles
- Hardware sharing: single ALU and single memory
 - Reduce the circuit area
 - They can be used for **different purposes** in different clock cycle

Multicycle Implementation: Disadvantages

Compared with single-cycle implementation, performance can be **decreased** due to:

- Additional internal registers
- More multiplexors to shared functional units
- More complicated control to consider about *time*

Question?