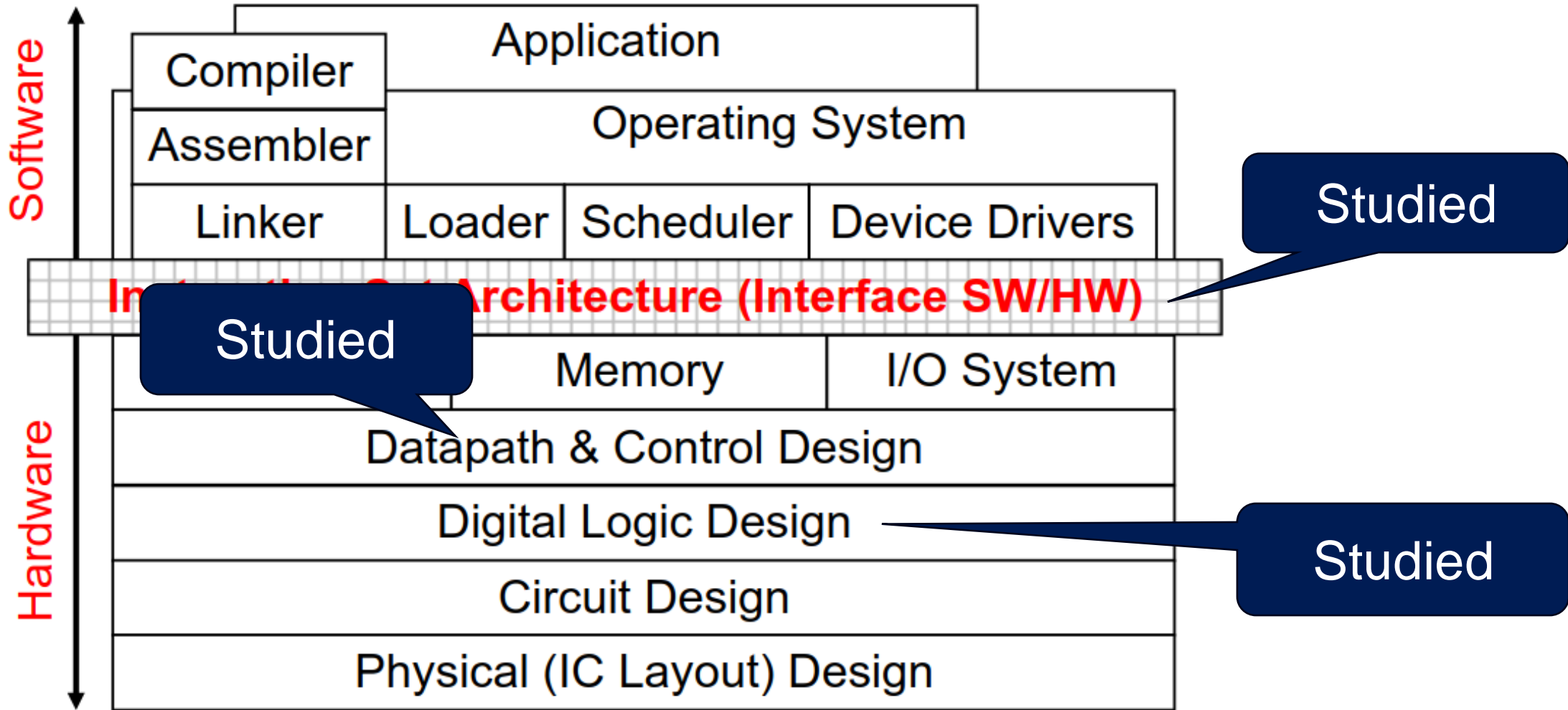


# CSE261: Computer Architecture


## 10. Processor (2)

Seongil Wi


# Where Are We?



# Today's Topic

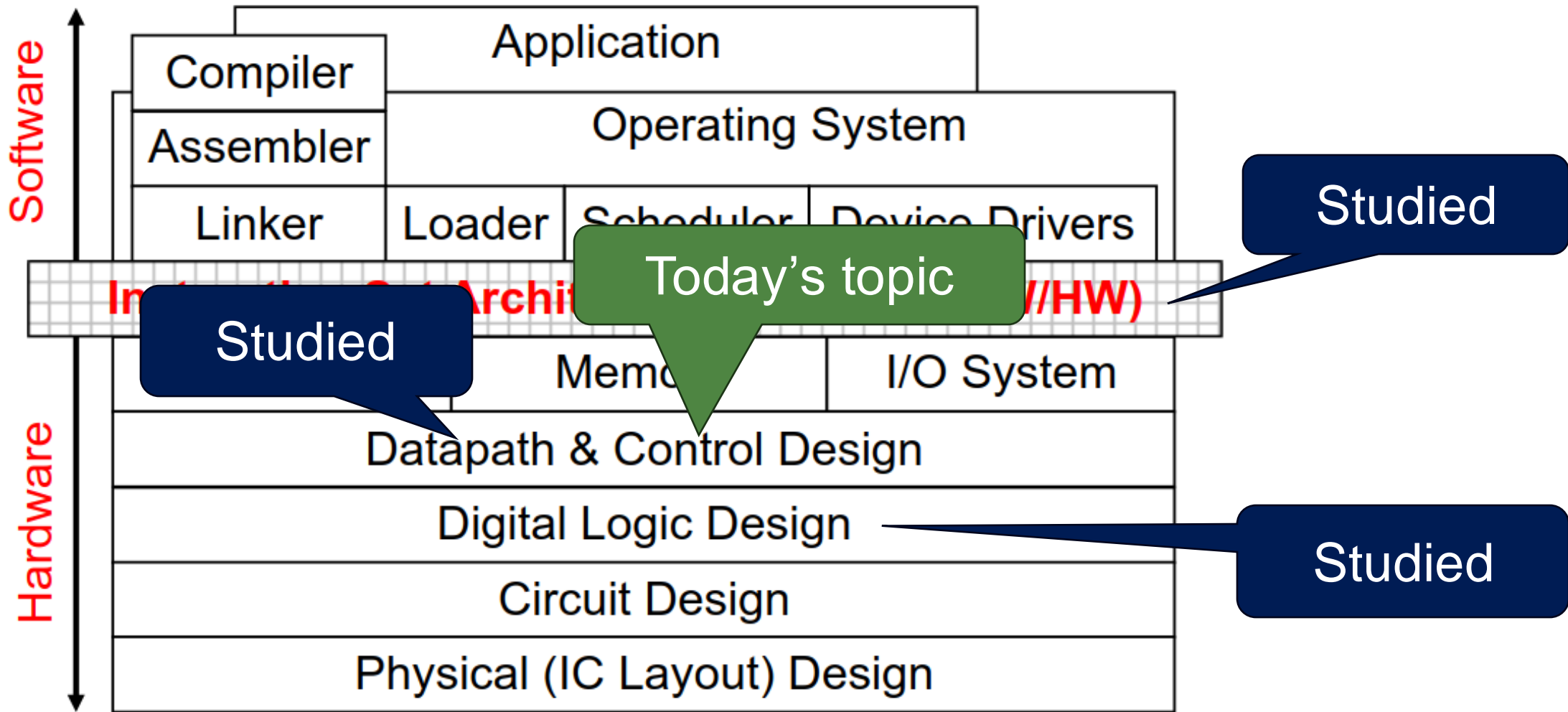


# Today's Topic

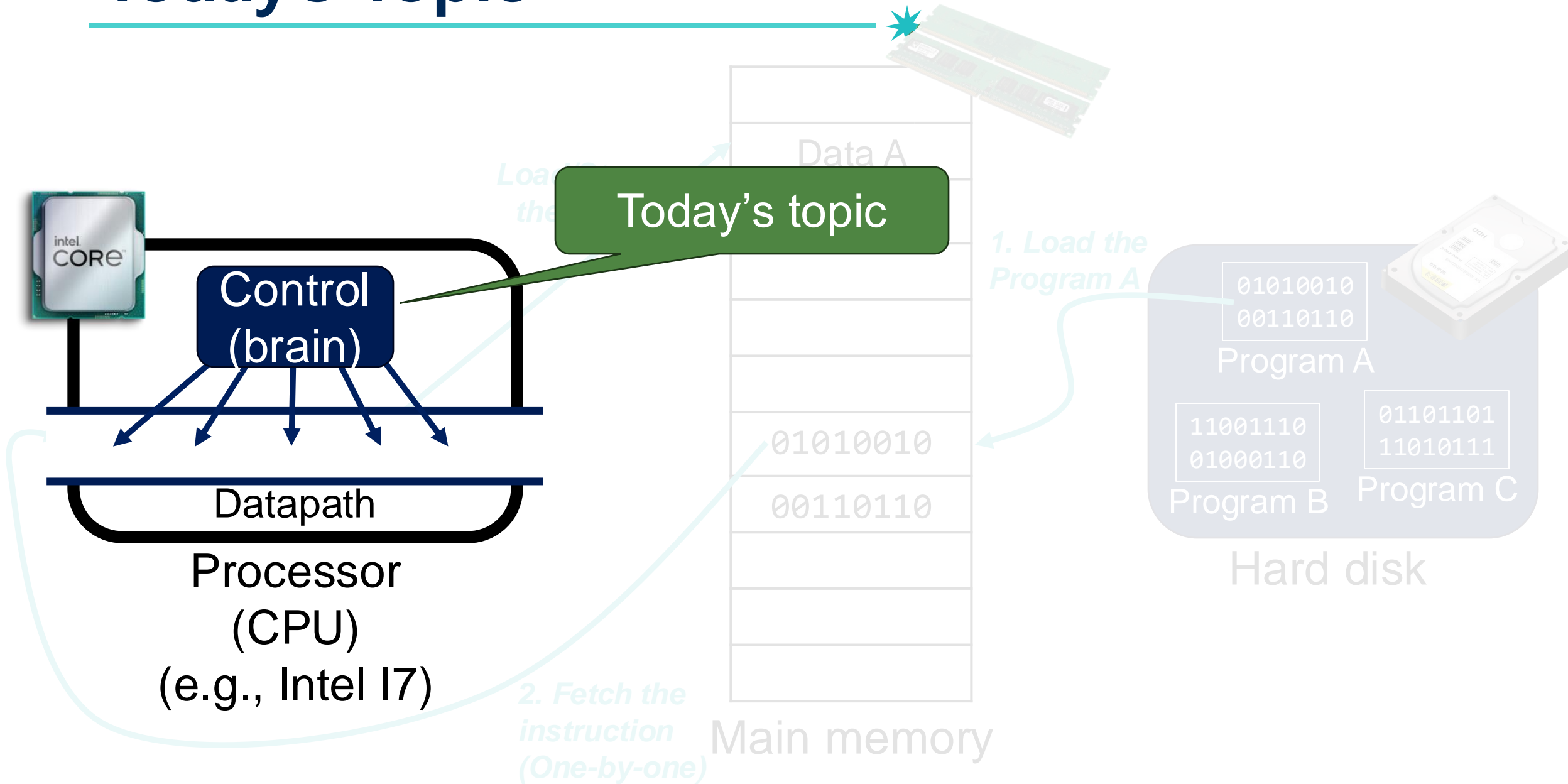

# Building a Control Unit

# Introduction to Control

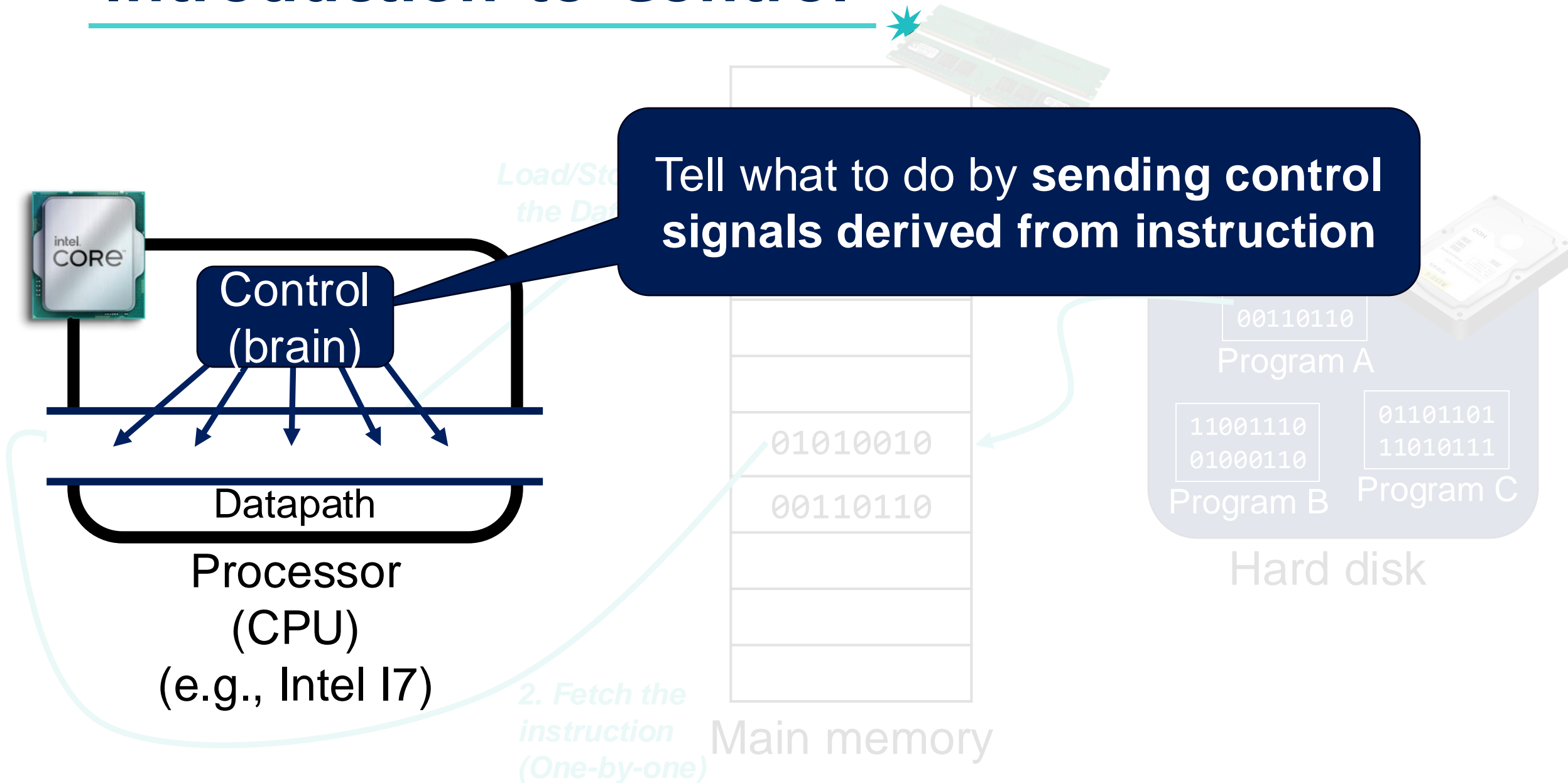


# Introduction to Control

7

add instruction

R-type:

op	rs	rt	rd	shamt	funct
31:26	25:21	20:16	15:11	10:6	5:0

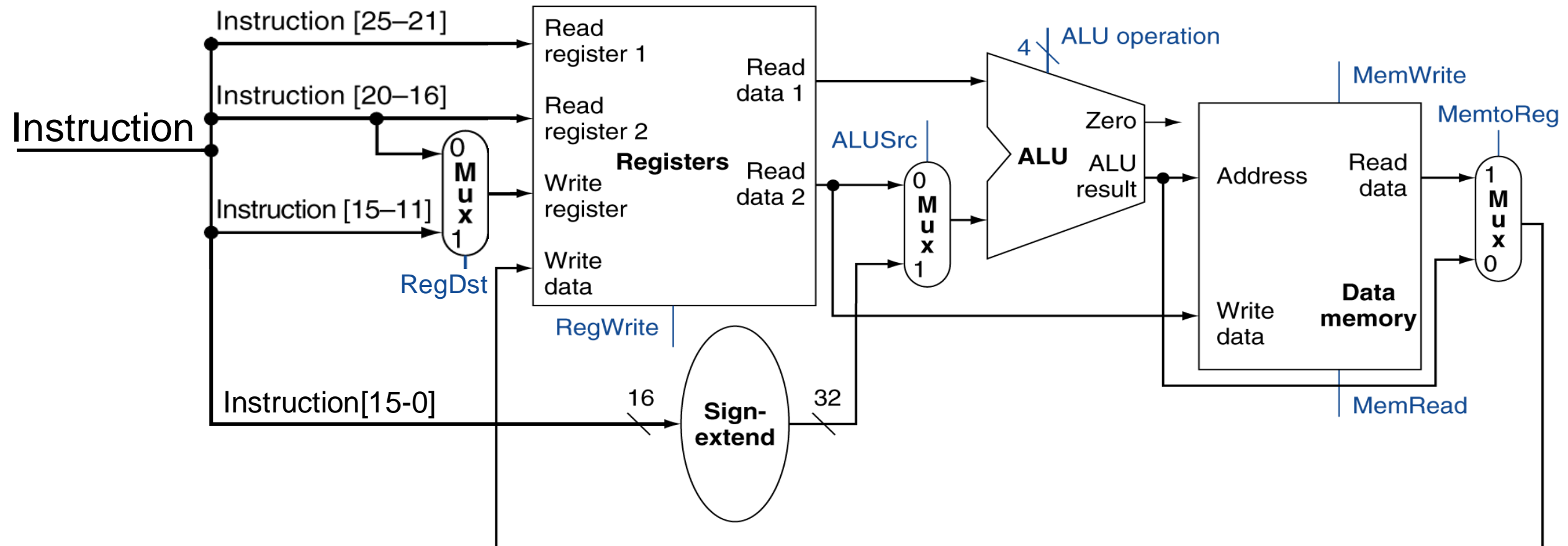


# Introduction to Control

8

add instruction


R-type:

 

Control

Send signals

Instruction

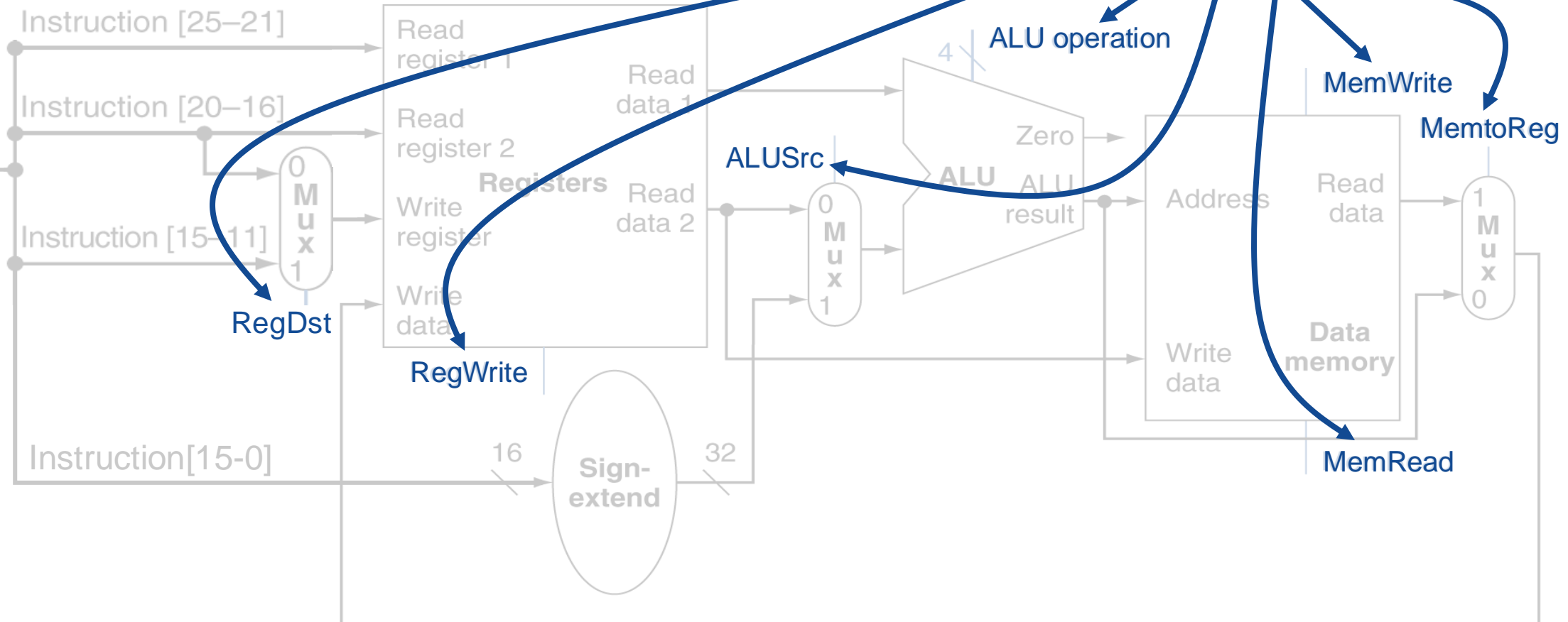




**Let's add the `Control` to  
complete the implementation**


# Datapath with Control

10

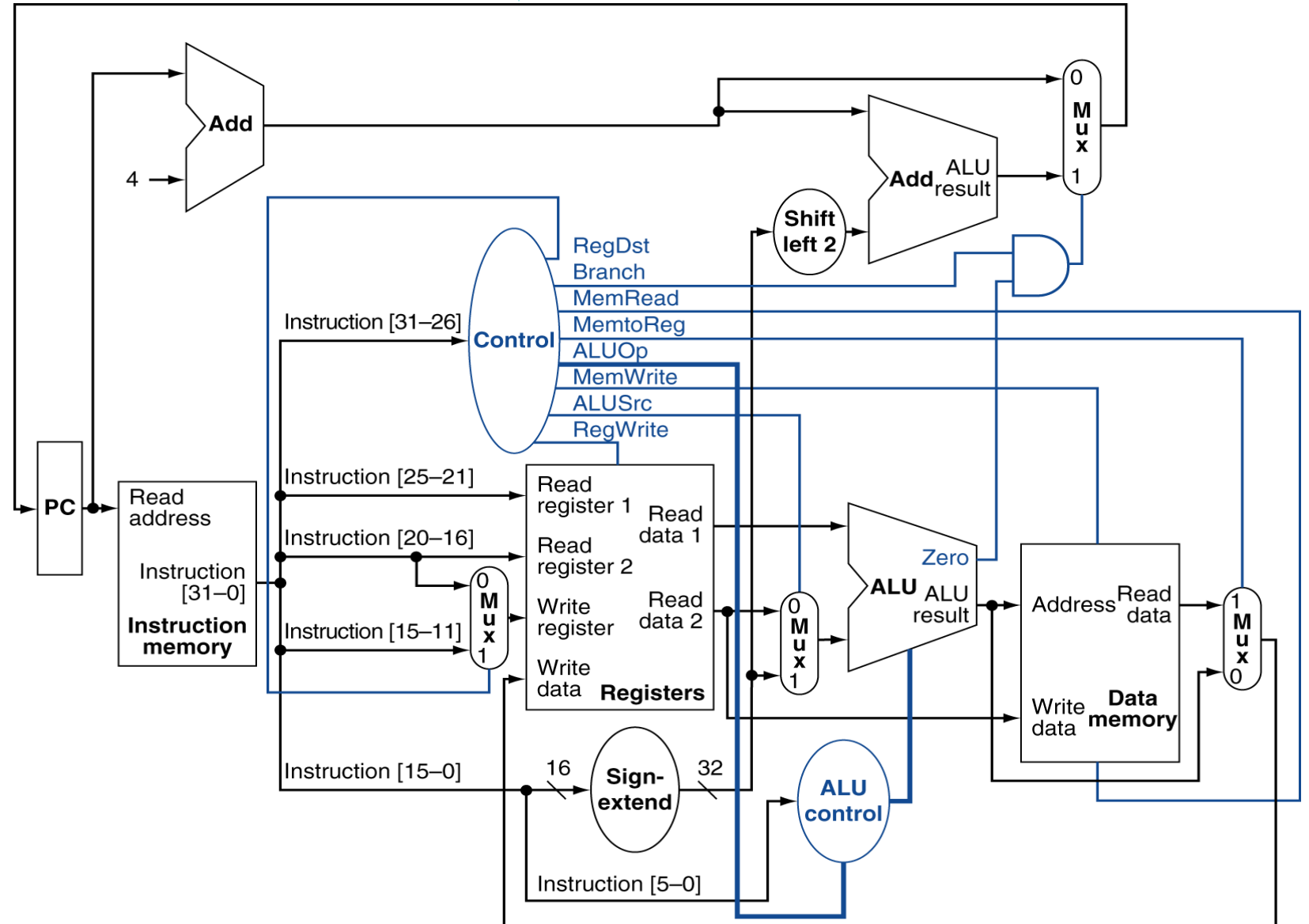

# Datapath with Control: Read opcode

11

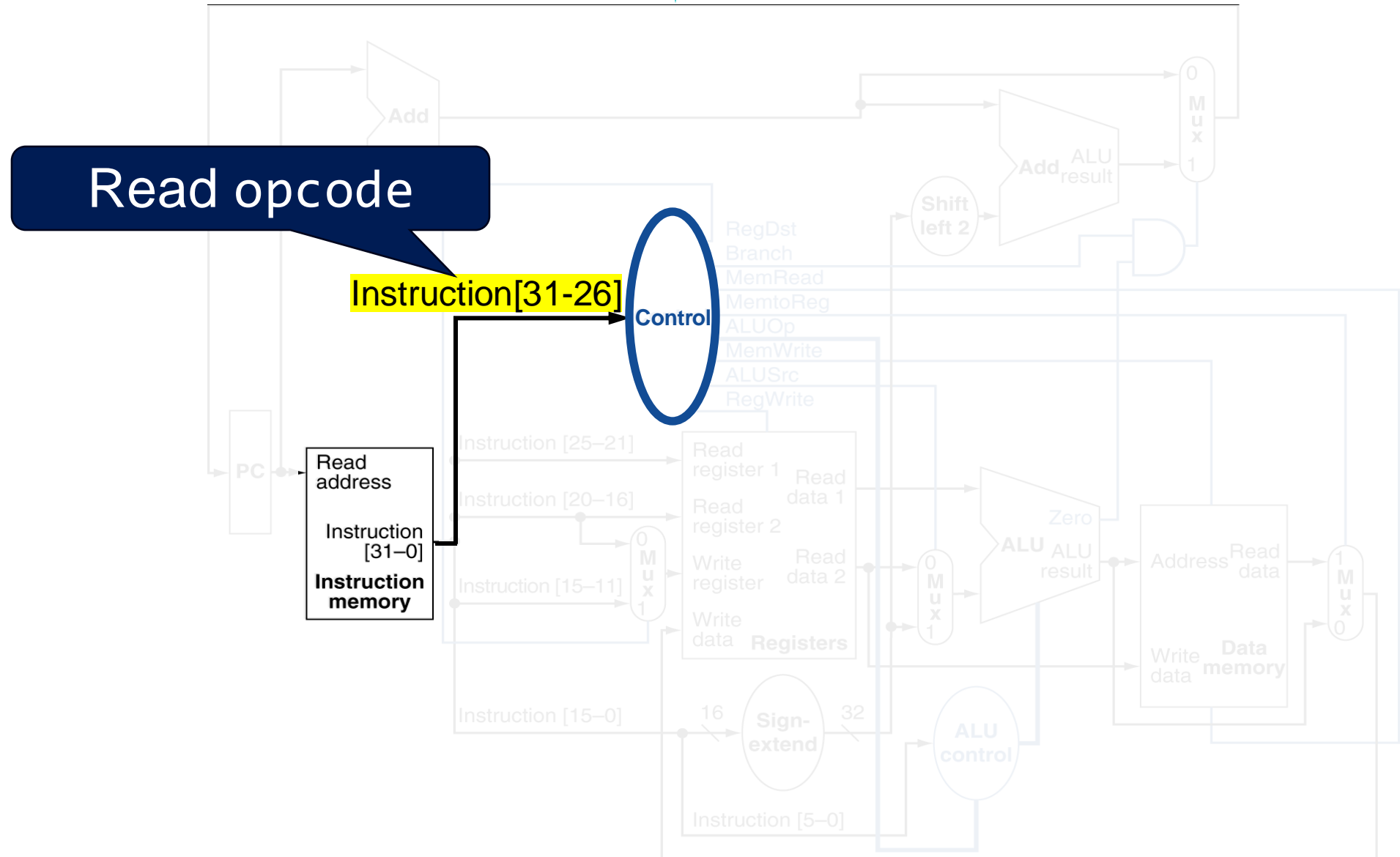

# Datapath with Control: Read opcode

12

Read opcode

Instruction[31-26]

Control

Read address  
Instruction [31-0]  
Instruction memory

R-type:

op	rs	rt	rd	shamt	funct
31:26	25:21	20:16	15:11	10:6	5:0

I-type:


op	rs	rt	Address
31:26	25:21	20:16	16:0

J-type:

op	address
31:26	26:0


# Datapath with Control: Send Signals

13

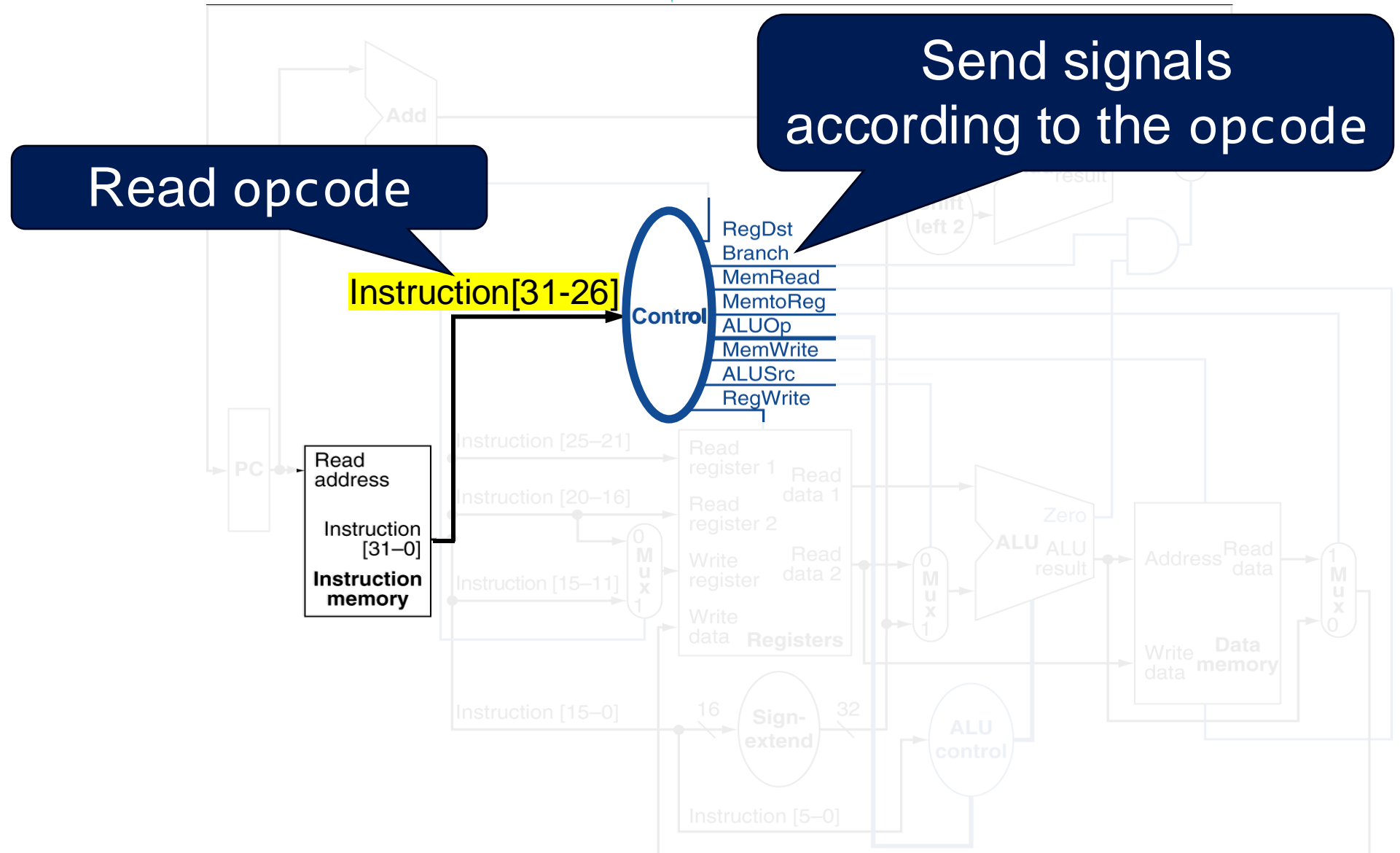

# Control Signal Example: RegDst

14

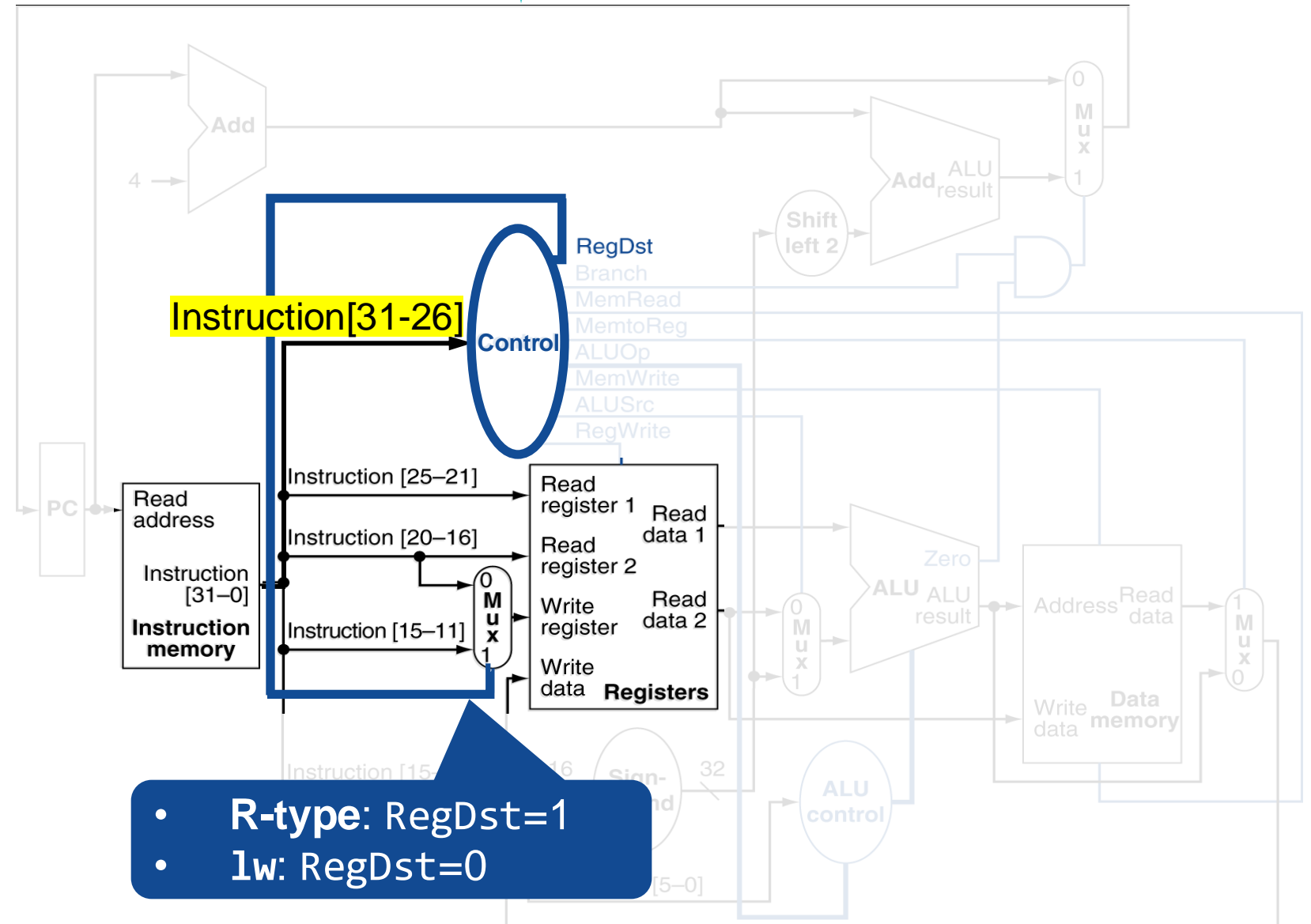


# Example: RegDst with R-type Instruction

15

add instruction

$R[rd] = R[rs] + R[rt]$

R-type:

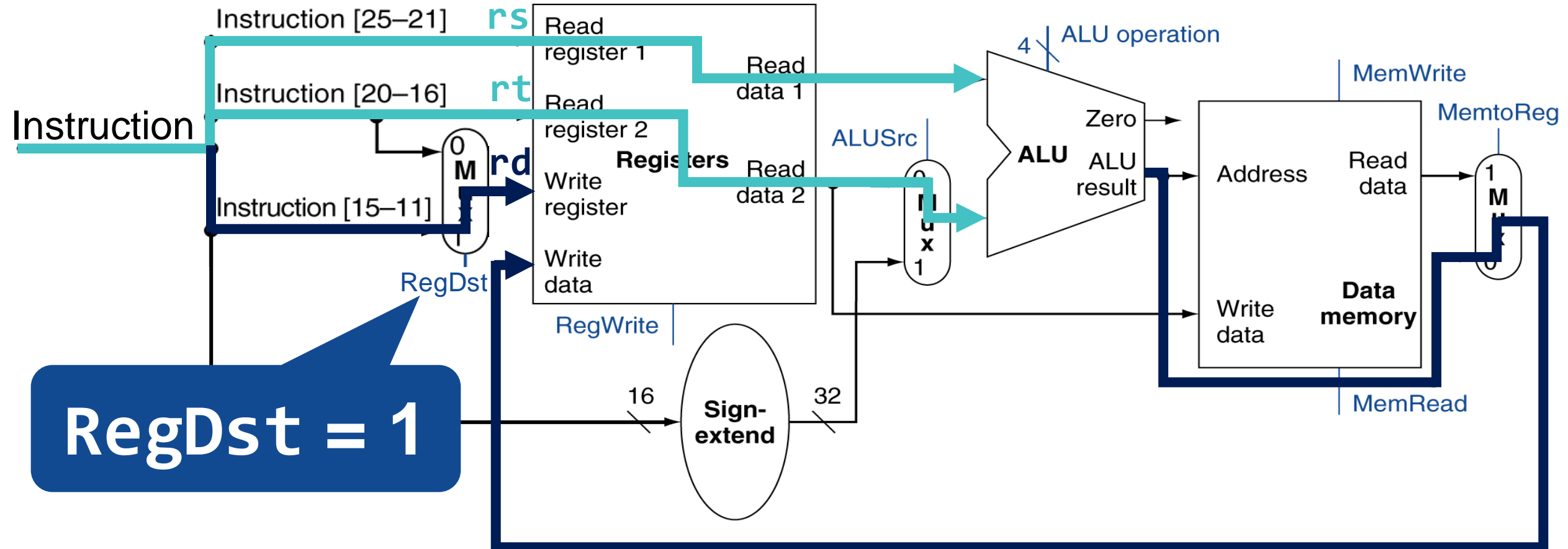


# Example: RegDst with R-type Instruction

16

add instruction

$R[rd] = R[rs] + R[rt]$

R-type:

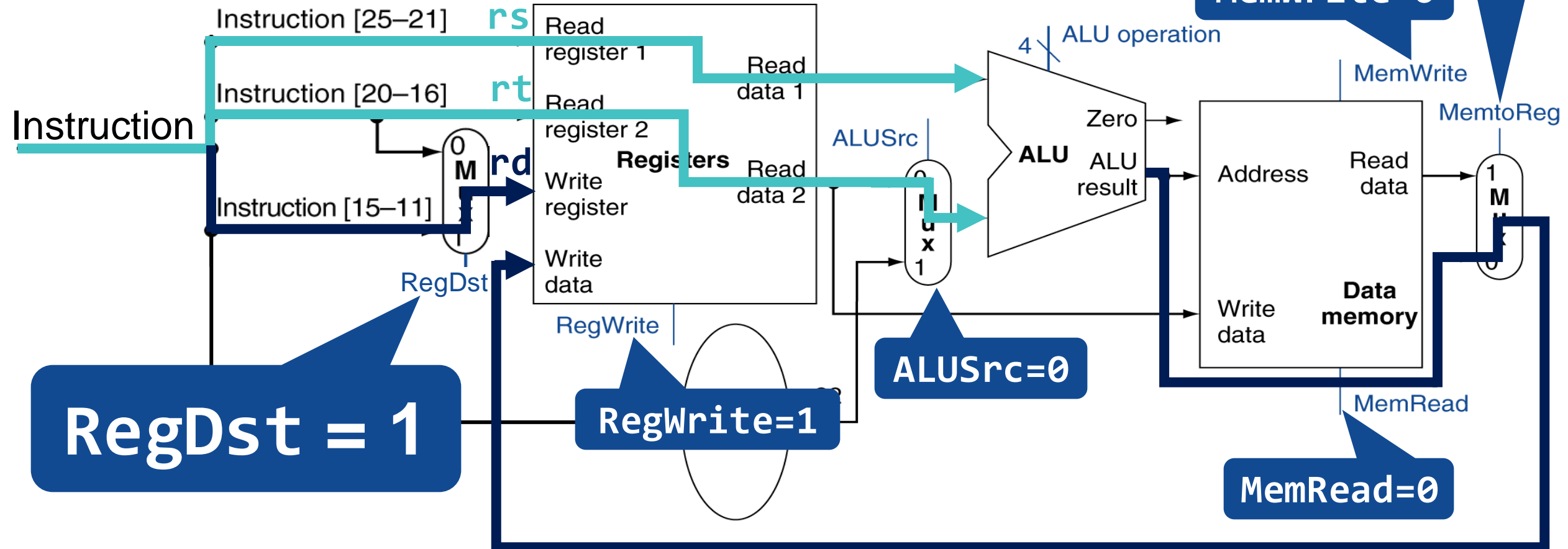



# Example: RegDst with Load Instruction


17

lw instruction

I-type:



$$R[rt] = M[R[rs] + \text{SignExtImm}]$$

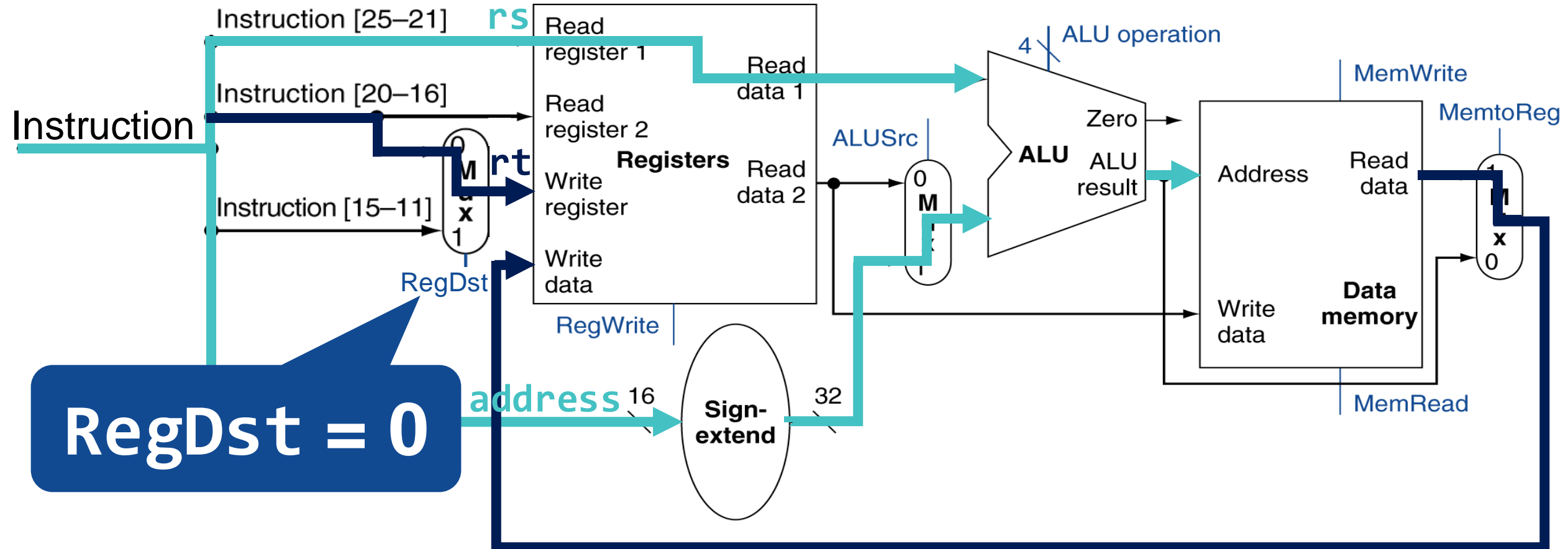

# Example: RegDst with Load Instruction


18

lw instruction

I-type:




$$R[rt] = M[R[rs] + \text{SignExtImm}]$$

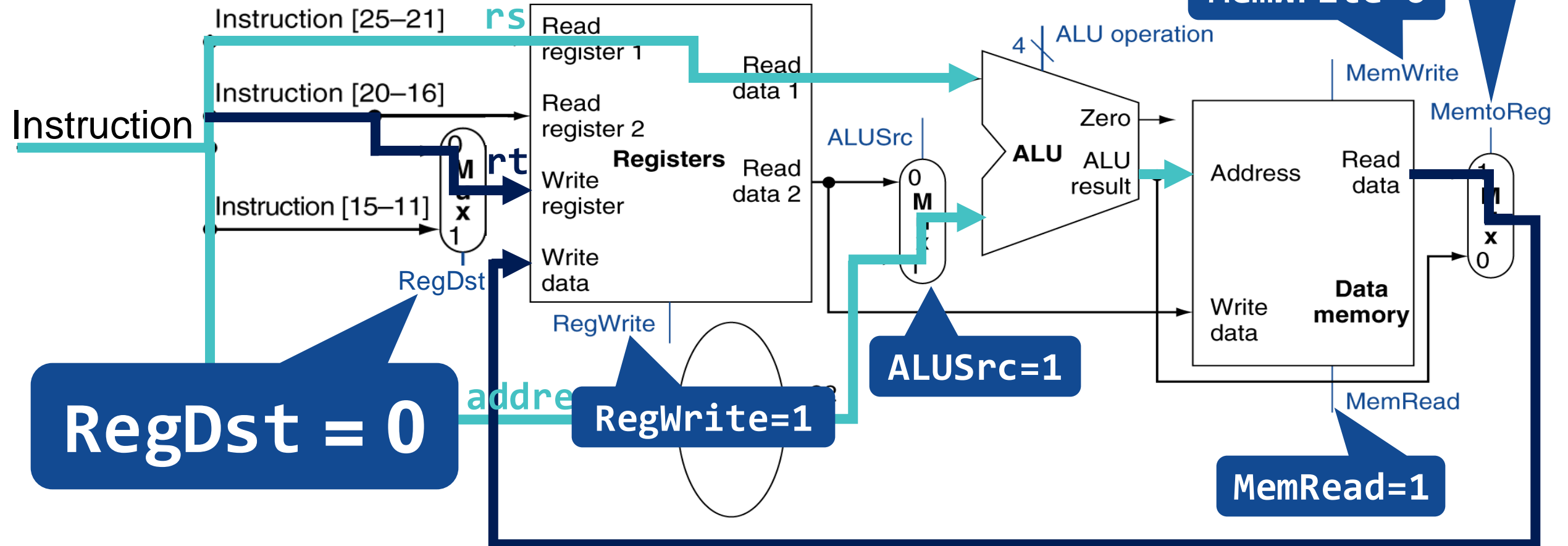

# Introduction to ALU

19

How it can be determined?

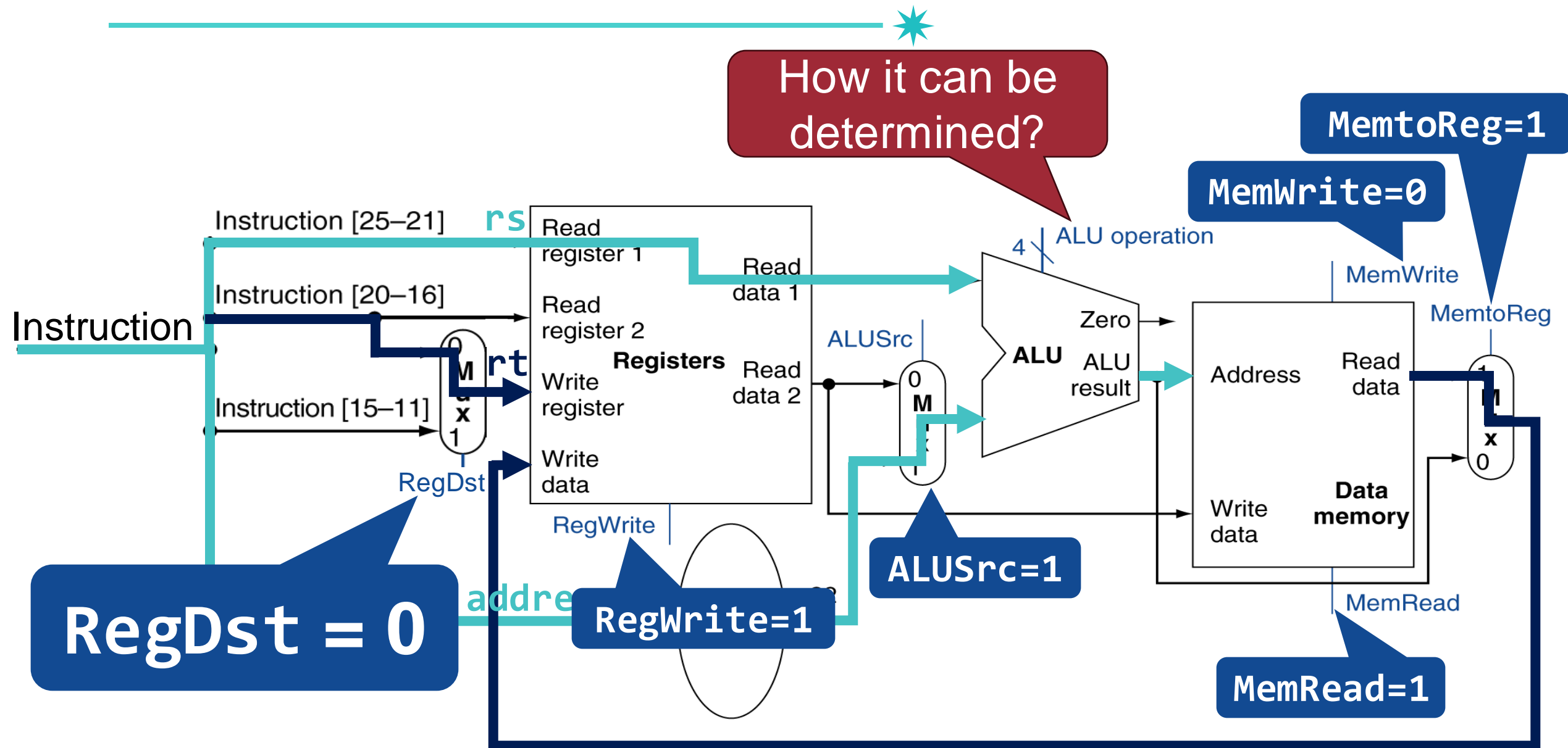

**First of all, let's take a look  
at the details of the ALU**

# Arithmetic Logic Unit (ALU)

---




Perform arithmetic and logic operations on binary numbers

# ALU with 4-bit Control Signals

Perform arithmetic and logic operations on binary numbers


4-bit control signals

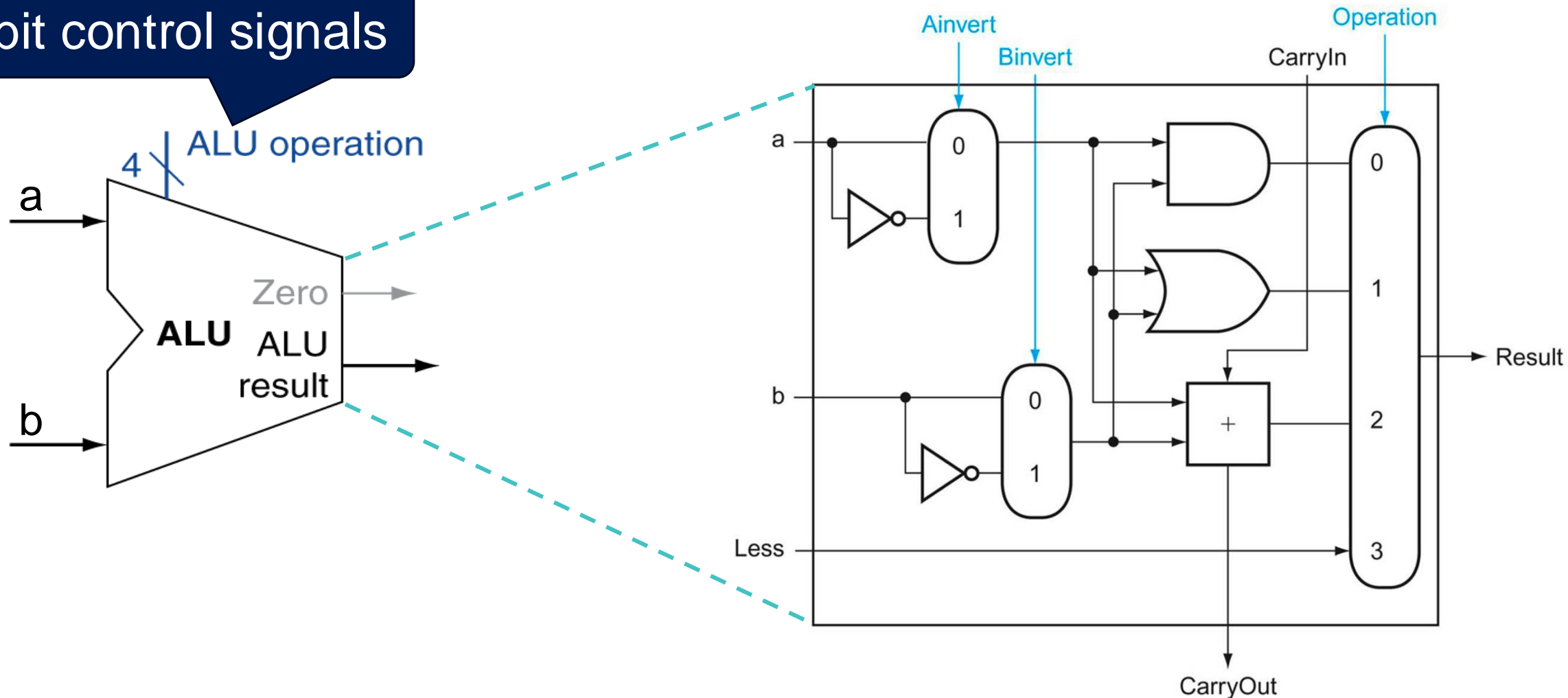

# ALU with 4-bit Control Signals


Perform arithmetic and logic operations on binary numbers

ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

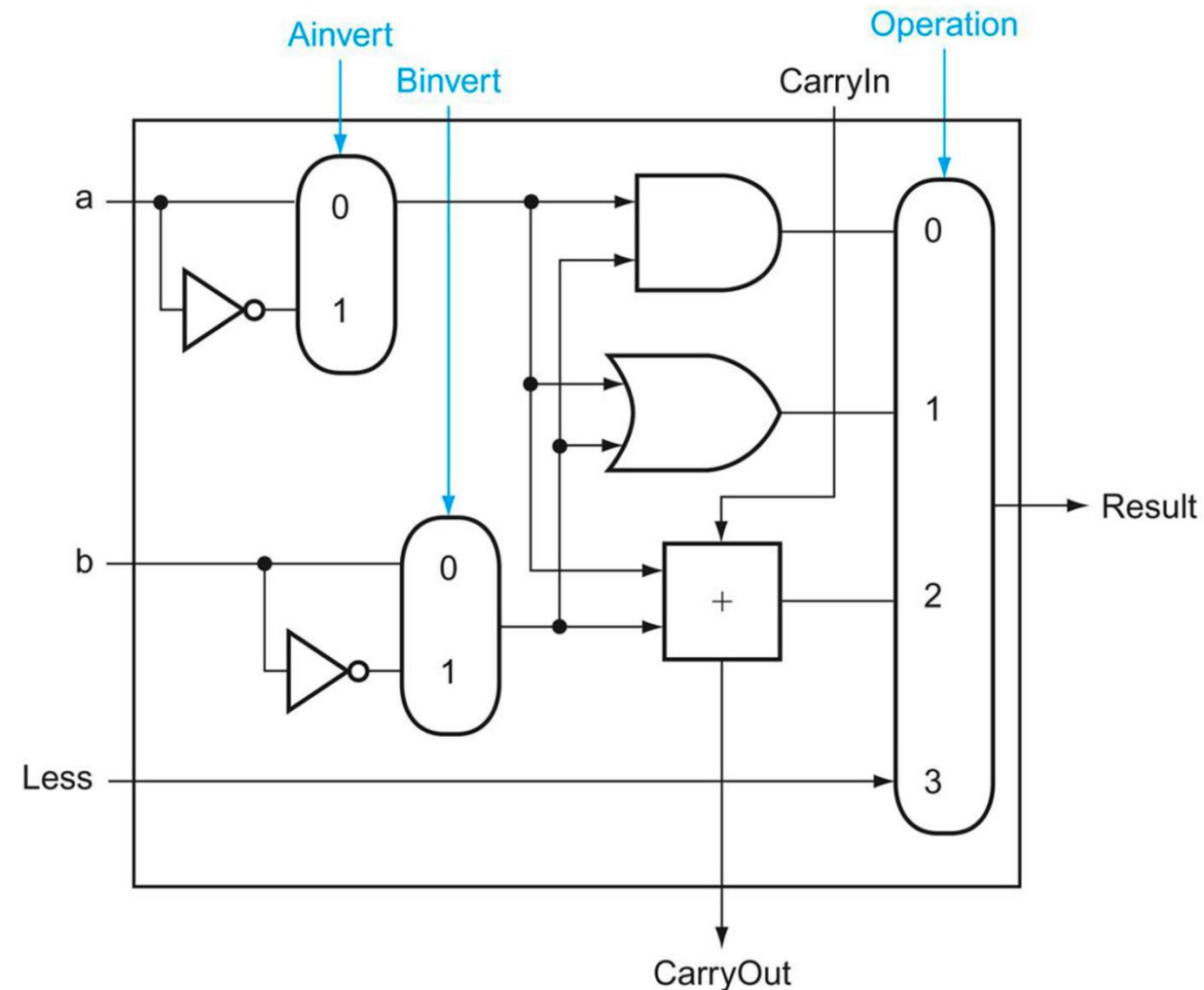

# ALU with 4-bit Control Signals

ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

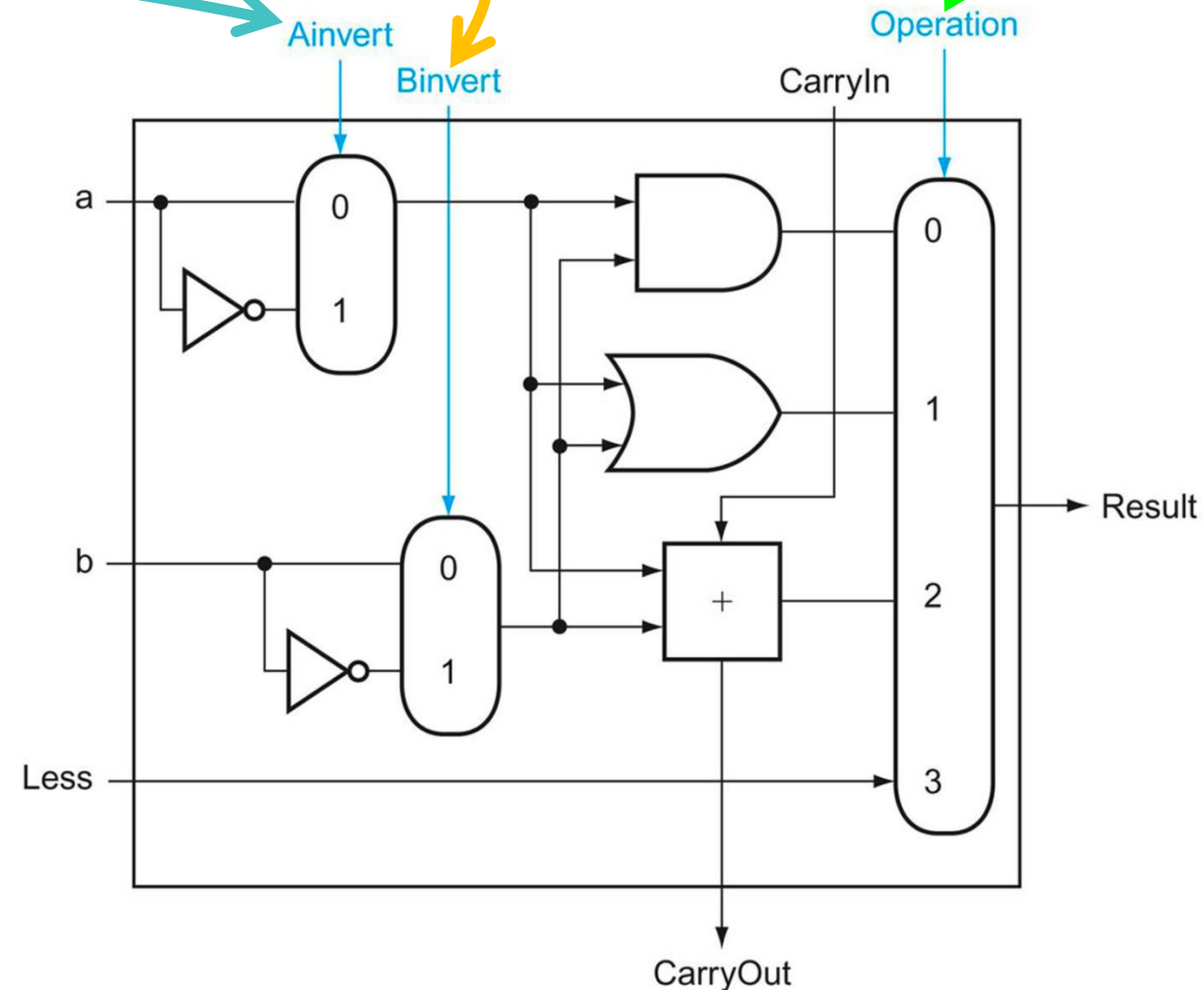




# ALU with 4-bit Control Signals: And


25

ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

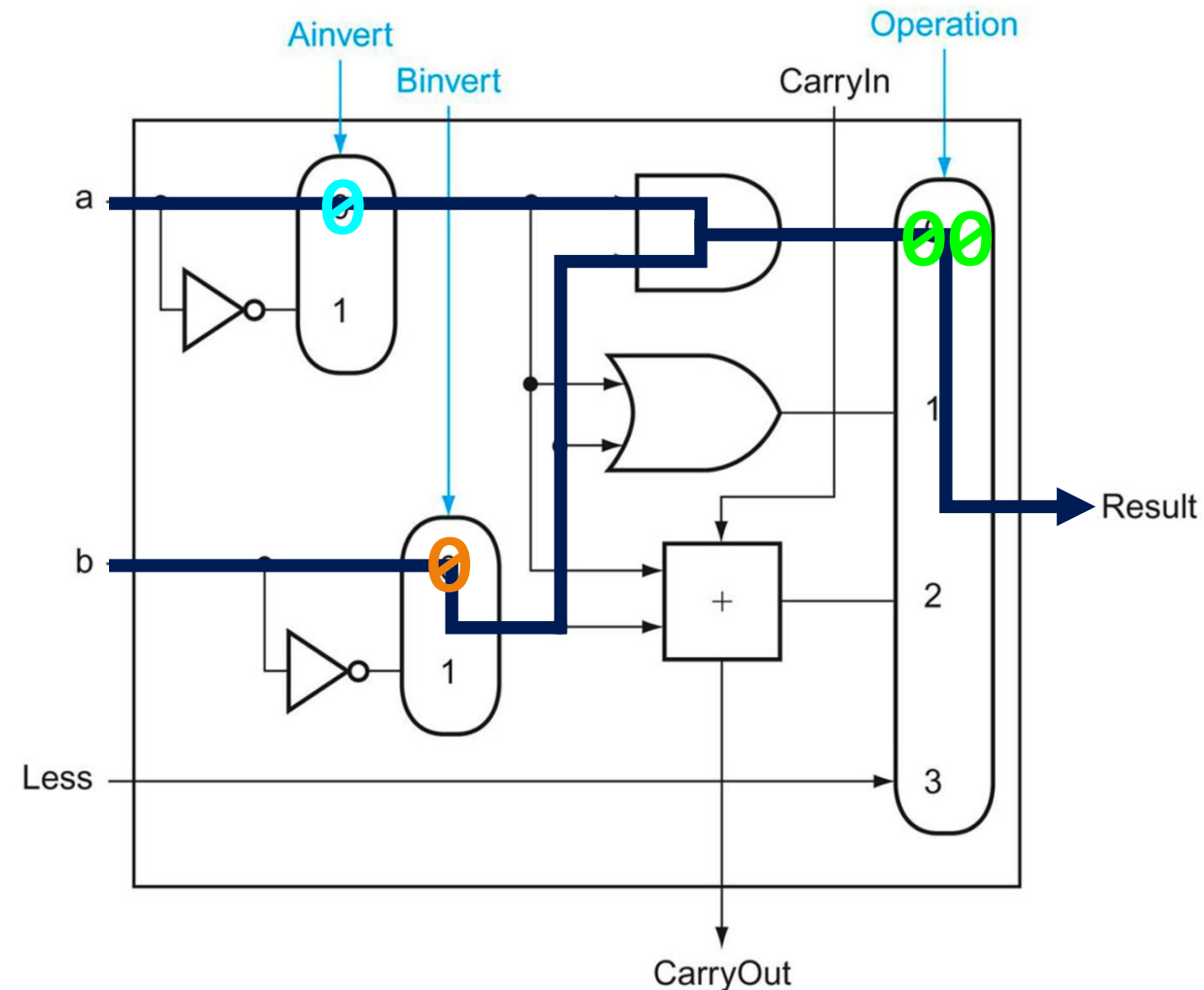

# ALU with 4-bit Control Signals: Or


ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

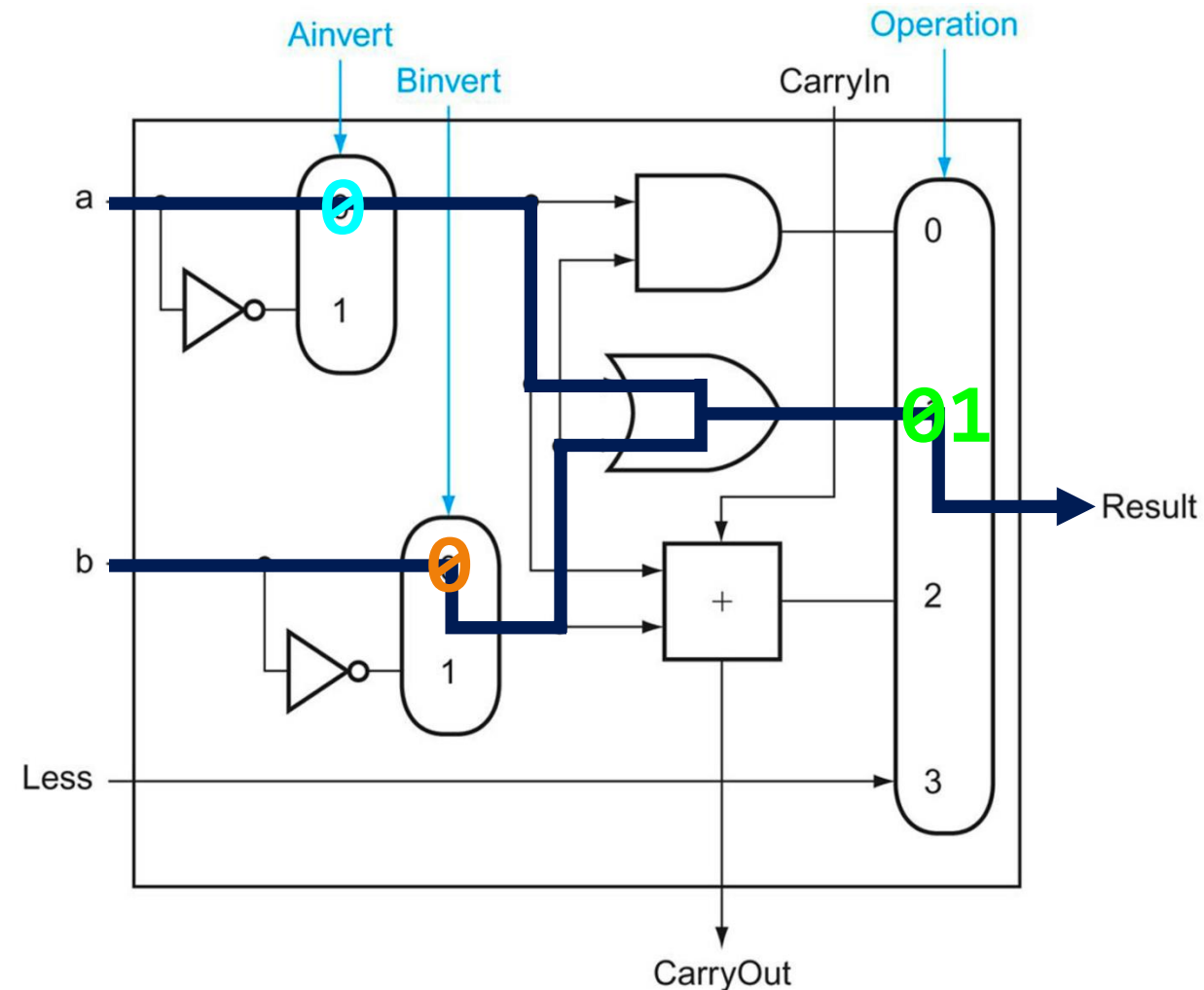

# ALU with 4-bit Control Signals: Add

27


ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

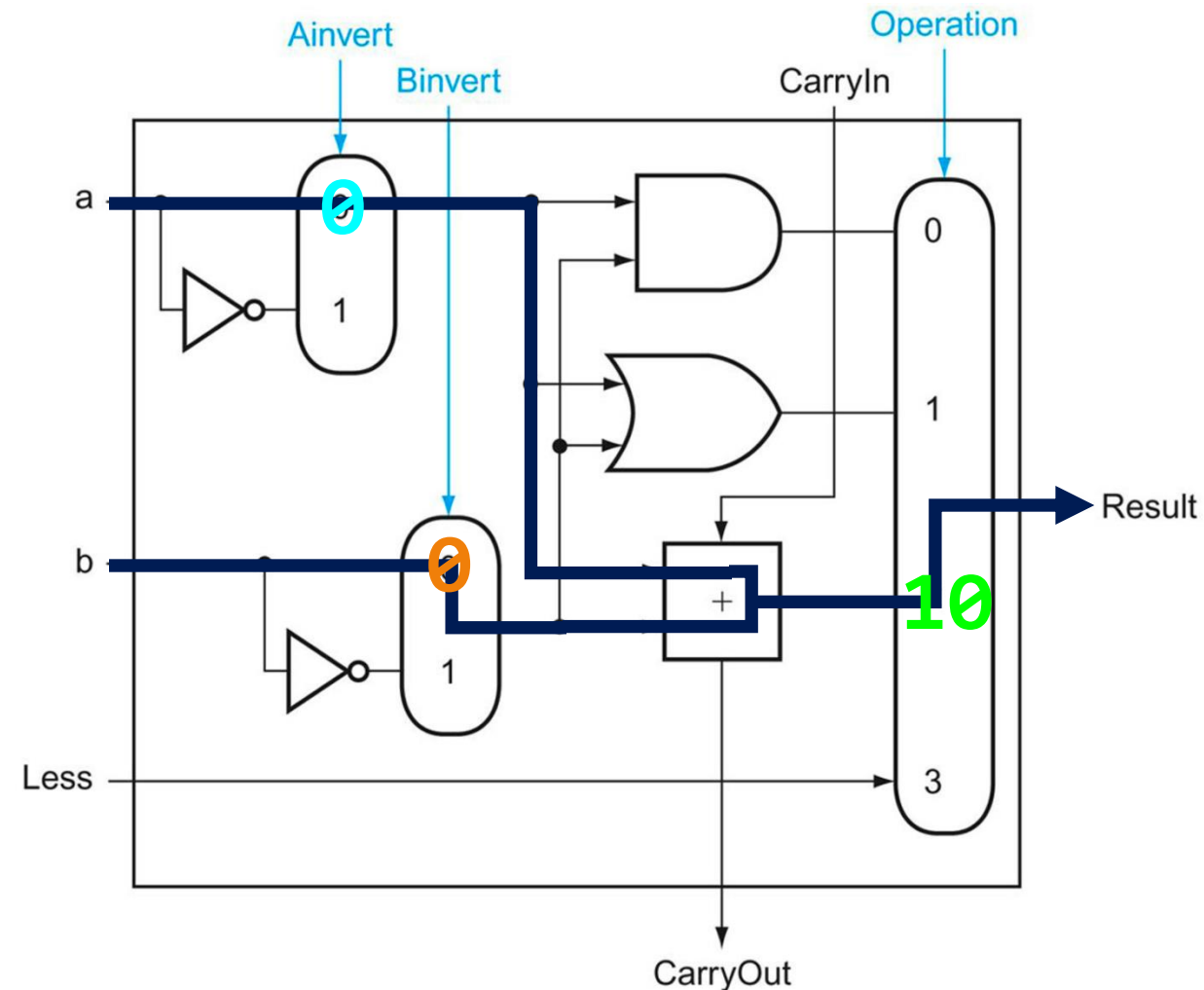

# ALU with 4-bit Control Signals: Subtract

28


ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

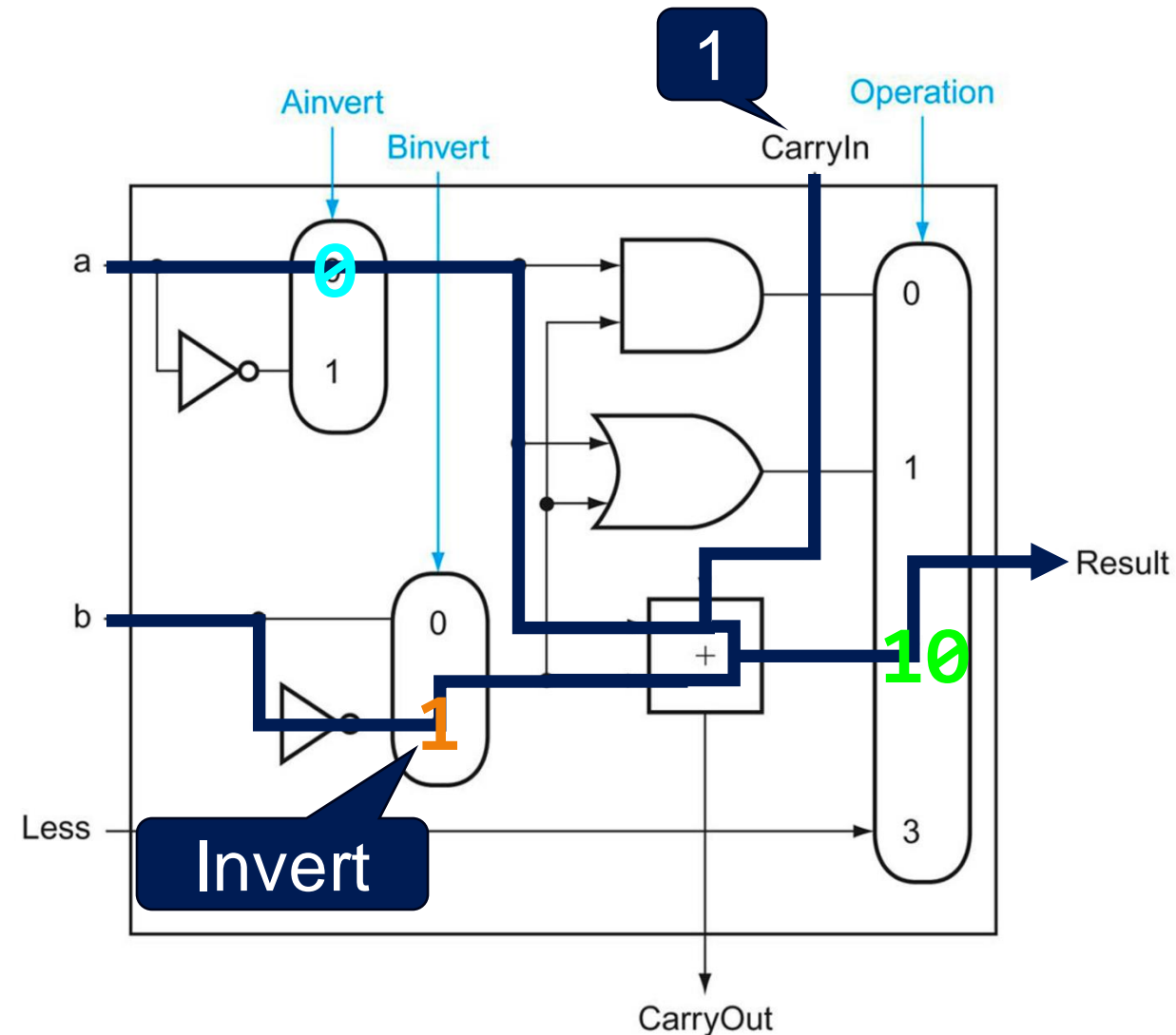

# ALU with 4-bit Control Signals: Subtract


29

ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
<b>0110</b>	<b>Subtract</b>
0111	Set on less than
1100	Nor

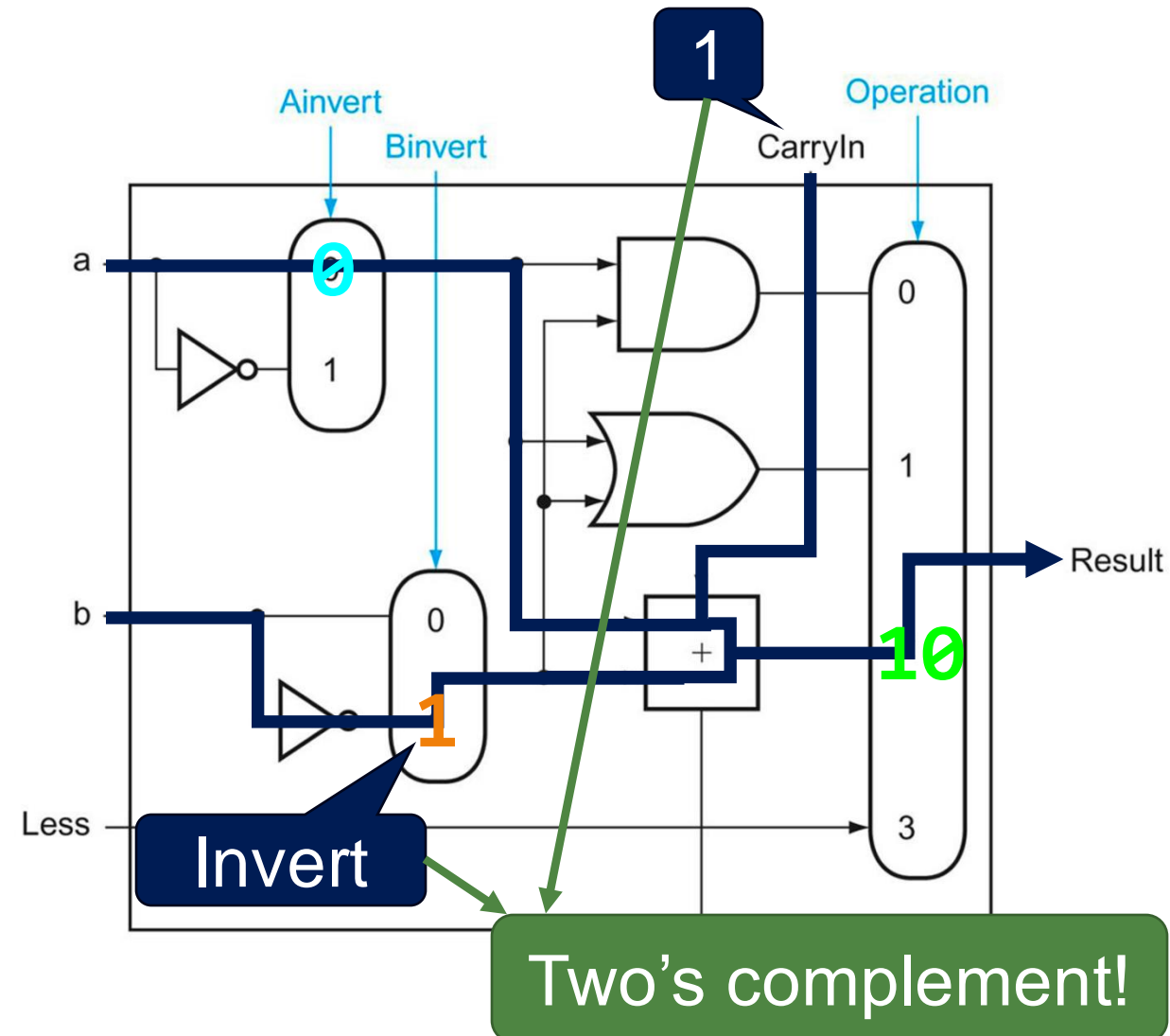

# ALU with 4-bit Control Signals


ALU control (4-bit control signal)	Function
0000	And
0001	Or
0010	Add
0110	Subtract
0111	Set on less than
1100	Nor

 

# ALU with 4-bit Control Signals: SLT

ALU control (4-bit control signal)	Function
0000	(Skip the detailed HW)
0001	if $a - b < 0$ : # $a < b$
0010	Less = 1
0110	else:
0111	Less = 0
1100	Set on less than
1100	Nor

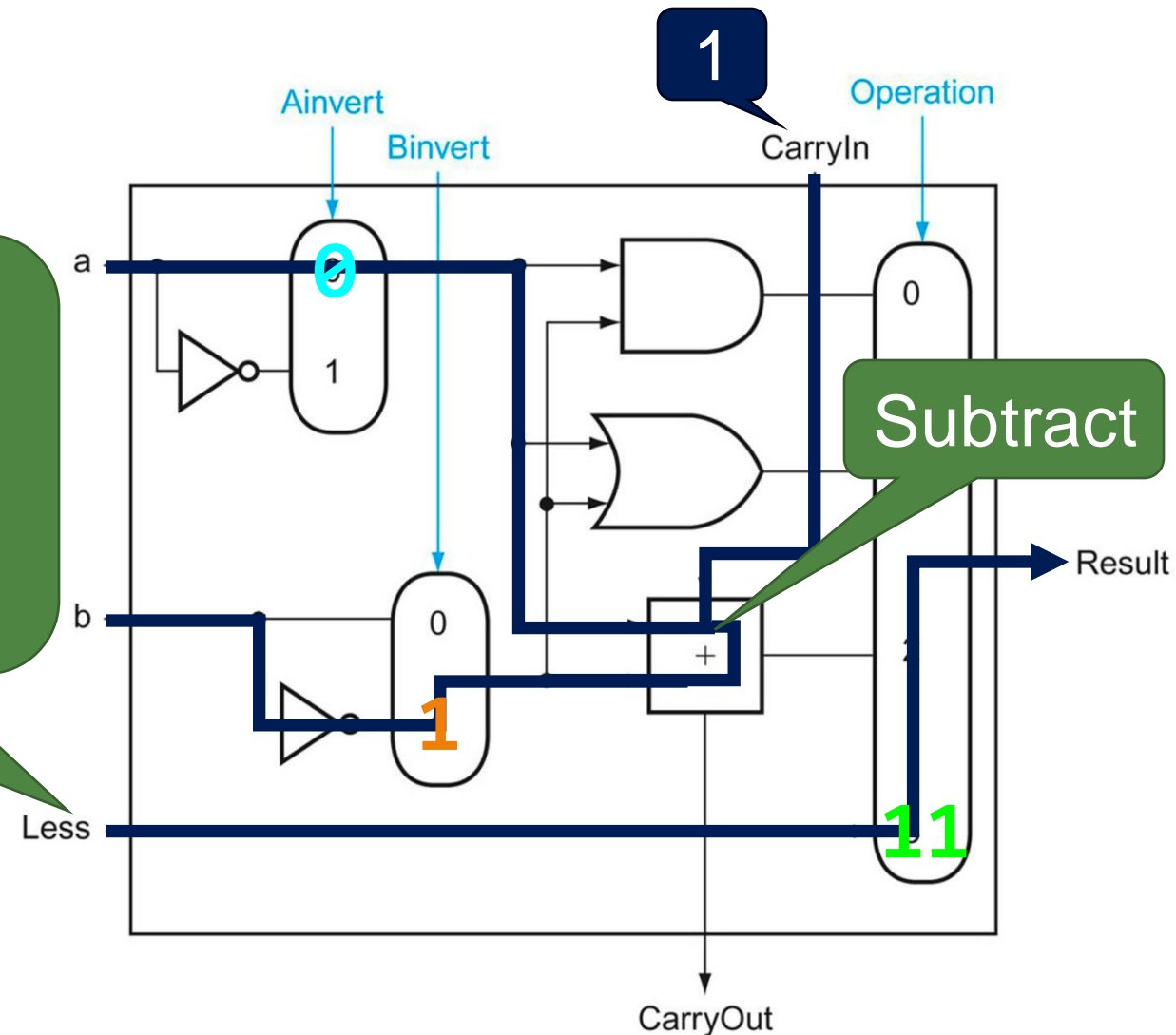(Skip the detailed HW)  
if  $a - b < 0$ : #  $a < b$   
Less = 1  
else:  
Less = 0



 
# Introduction to ALU Control




- The ALU operation signals must be provided differently based on the instruction

Arithmetic / Logic  
Instructions  
(R-format)




Depending on the  
instruction

lw, sw  
(I-format)

 

Addition

beq  
(I-format)

 


Subtraction



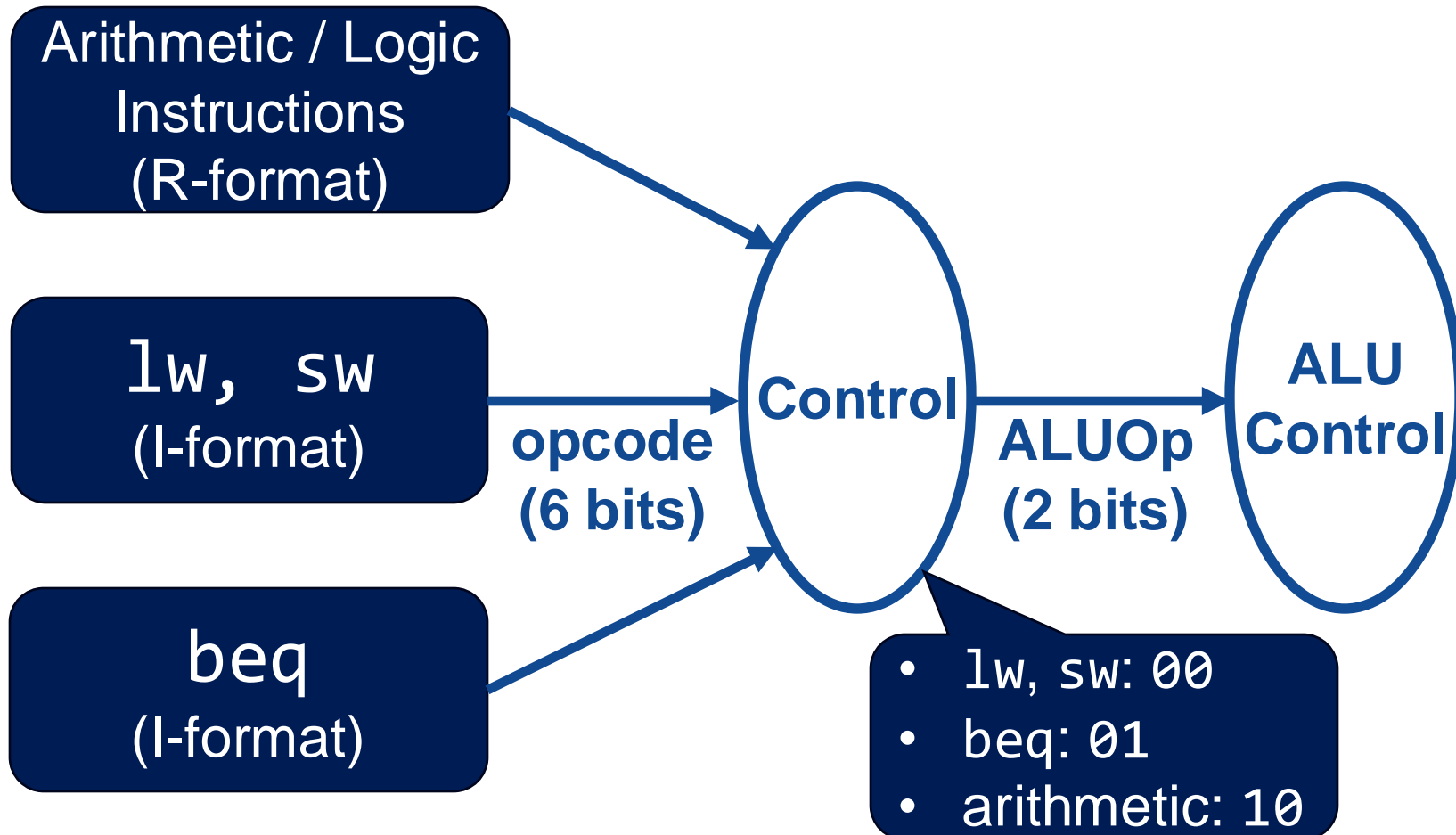
# Introduction to ALU Control

- The ALU operation signals must be provided differently based on the instruction



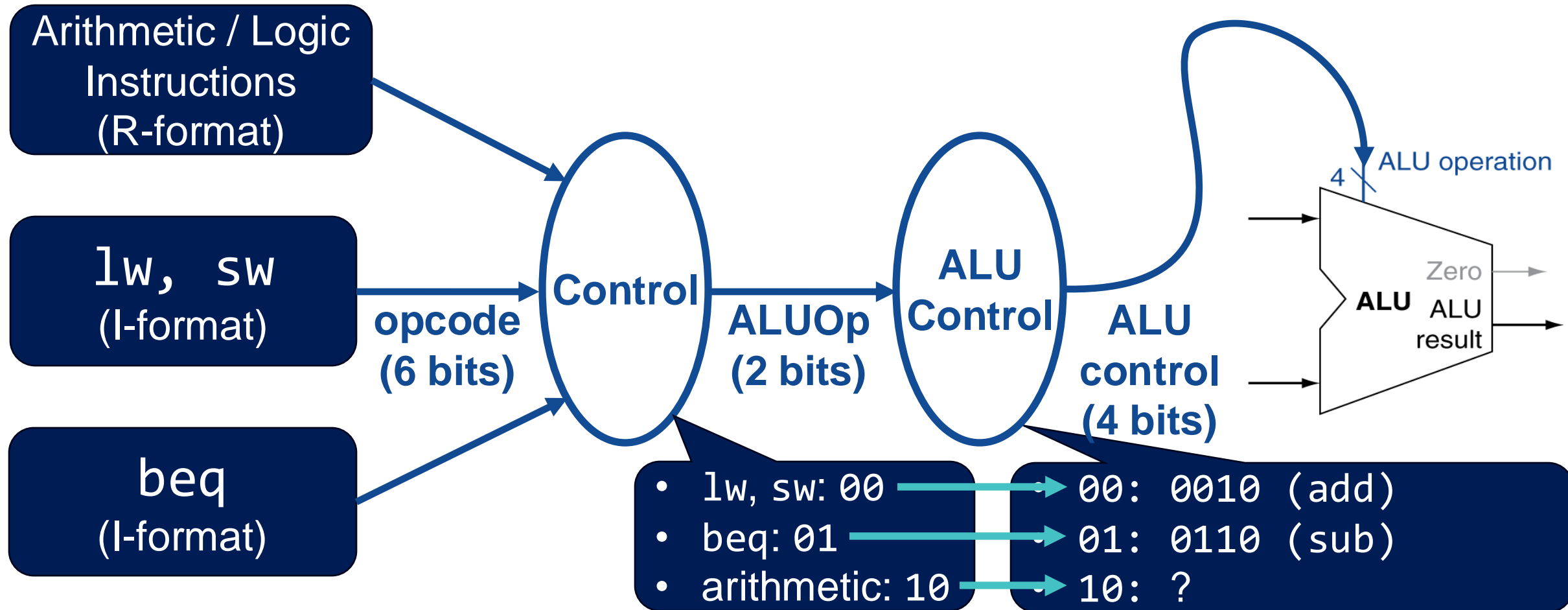
# Introduction to ALU Control

- The ALU operation signals must be provided differently based on the instruction



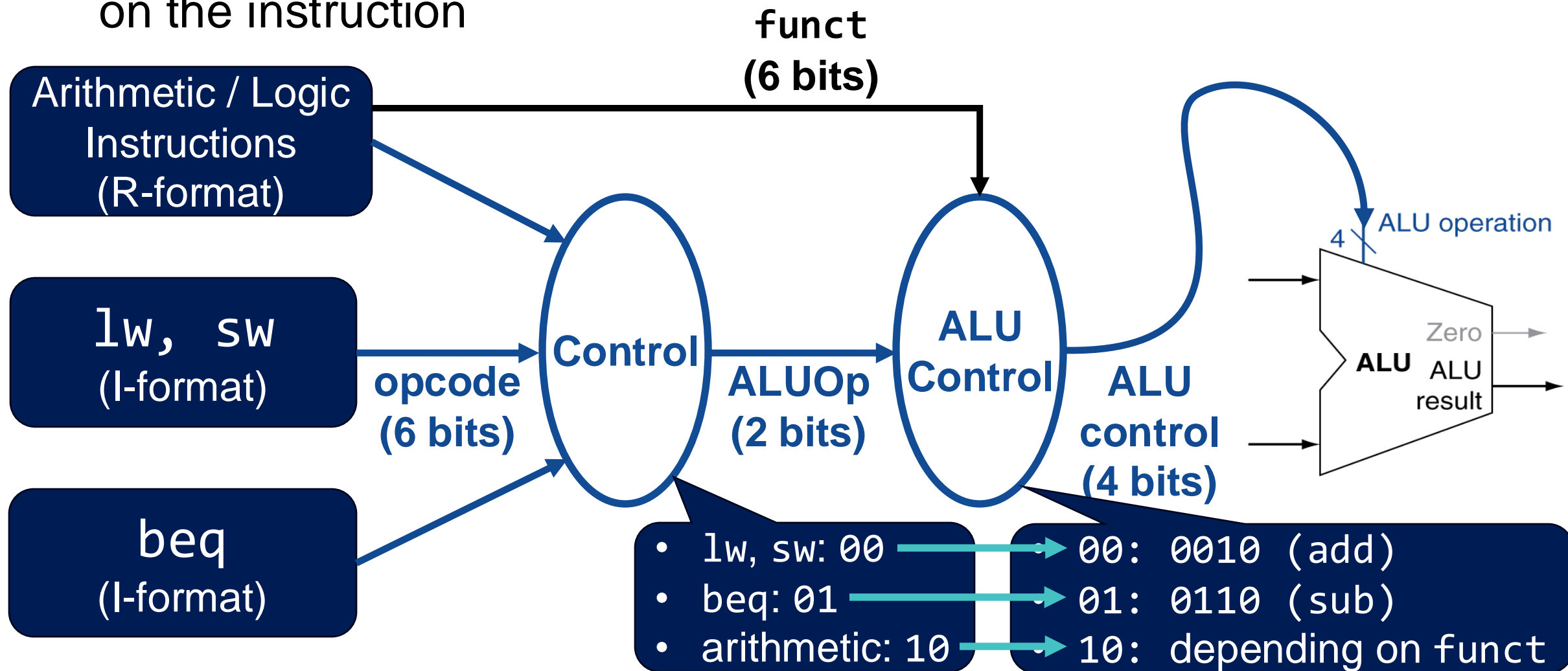
# Introduction to ALU Control

- The ALU operation signals must be provided differently based on the instruction



# Datapath with ALU Control

36

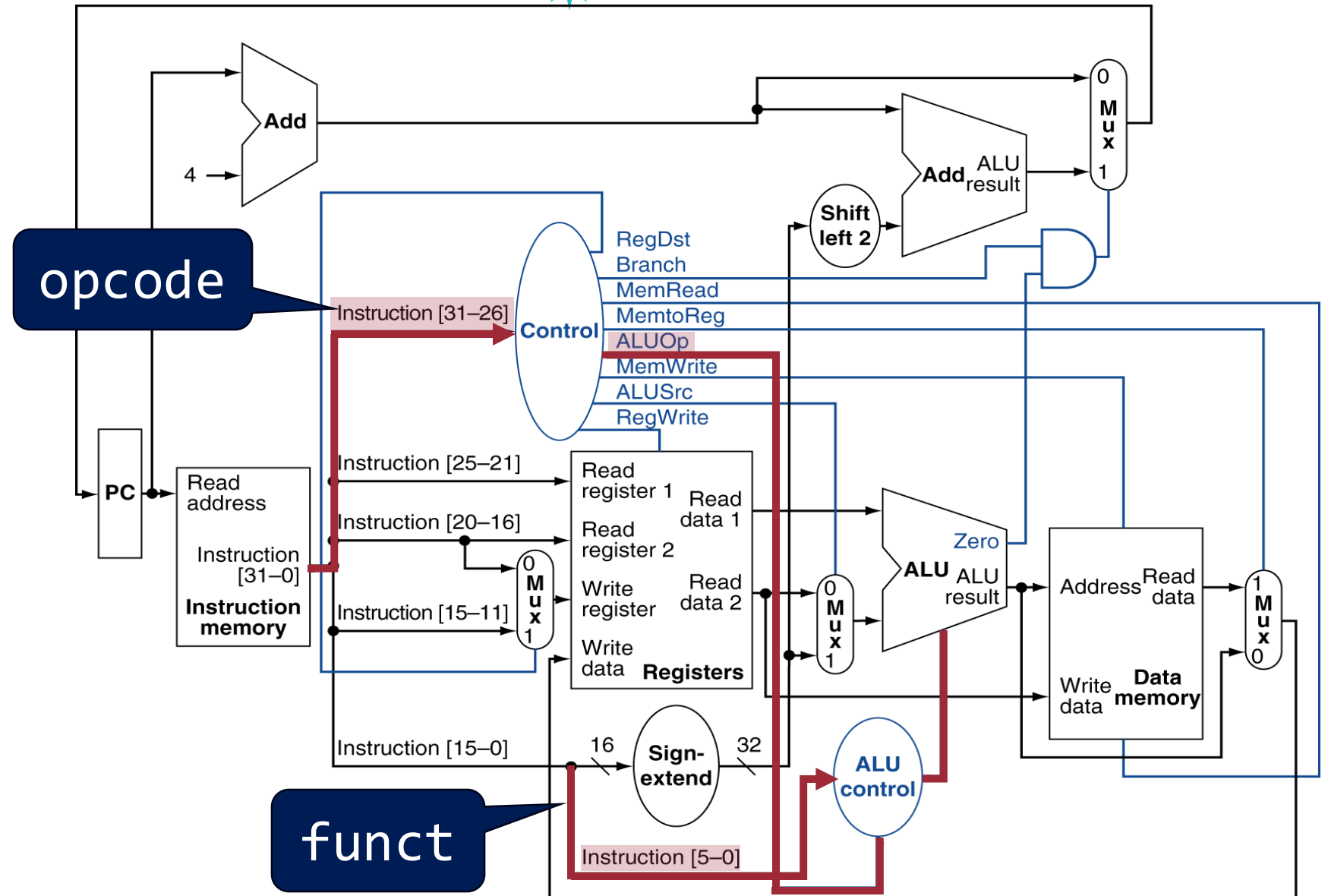

# Summary: ALU Control



- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control
  - What's the benefit of multi-level decoding for ALU control?

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

# Summary: ALU Control




- Assume 2-bit ALUOp derived from opcode
  - Combinational logic derives ALU control
  - What's the benefit of multi-level decoding

X: "Don't care"  
about the value

opcode	ALUOp	Operation	funct	ALU operation	ALU control
lw	00	load word	XXXXXX	add	0010
sw	00	store word	XXXXXX	add	0010
beq	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
		subtract	100010	subtract	0110
		AND	100100	AND	0000
		OR	100101	OR	0001
		set-on-less-than	101010	set-on-less-than	0111

# One More Thing! Datapath for a Branch

39

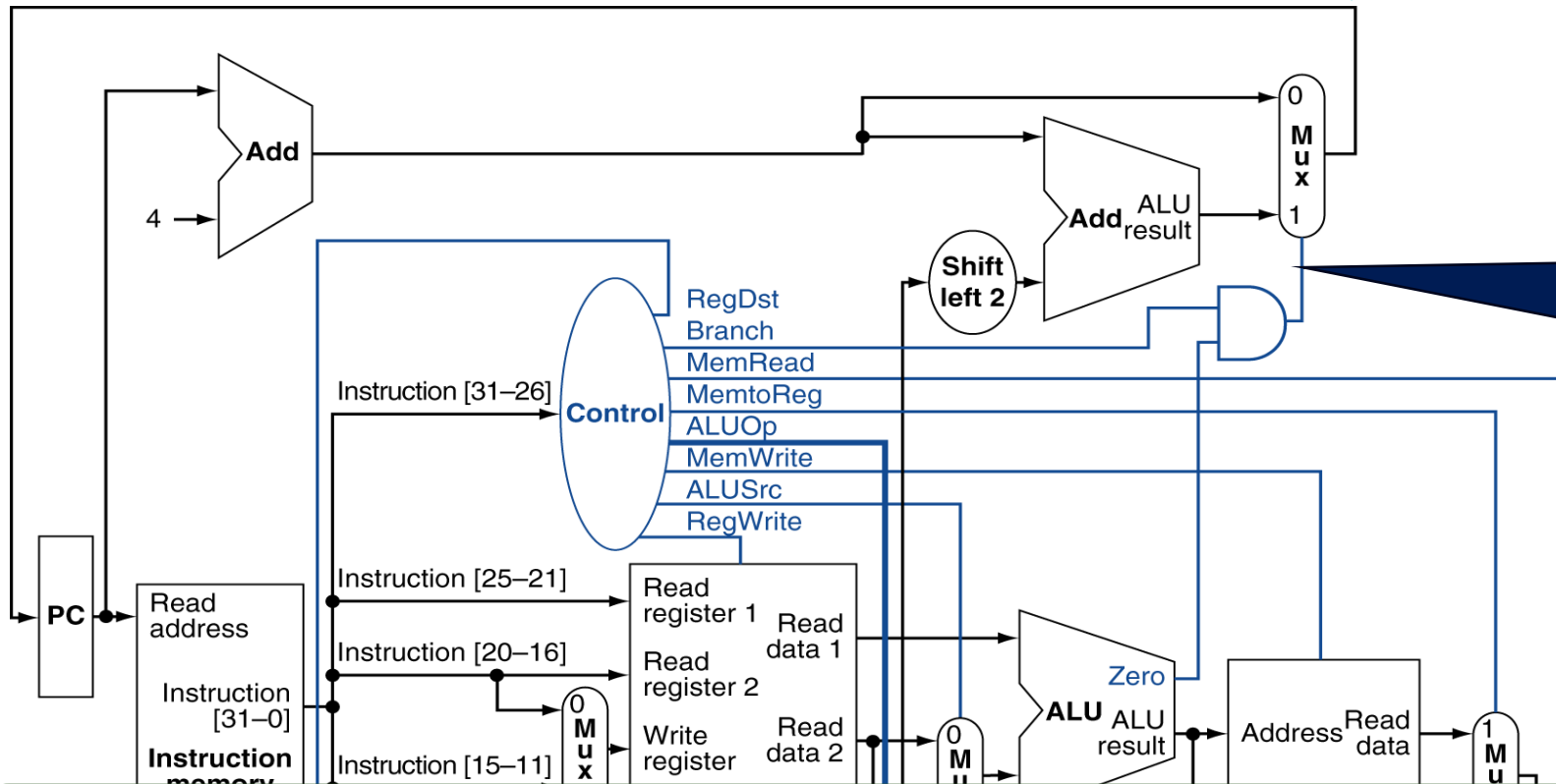

PCsrc =  
Branch && Zero

sub can also enable the Zero flag. Therefore, it's essential to check the opcode of the instruction to determine whether it is a branch instruction or not!


# Summary: Control Signals



Signal name	Effect when deasserted	Effect when asserted
RegDst	The register destination number for the Write register comes from the rt field (bits 20:16).	The register destination number for the Write register comes from the rd field (bits 15:11).
RegWrite	None.	The register on the Write register input is written with the value on the Write data input.
ALUSrc	The second ALU operand comes from the second register file output (Read data 2).	The second ALU operand is the sign-extended, lower 16 bits of the instruction.
PCSrc	The PC is replaced by the output of the adder that computes the value of PC + 4.	The PC is replaced by the output of the adder that computes the branch target.
MemRead	None.	Data memory contents designated by the address input are put on the Read data output.
MemWrite	None.	Data memory contents designated by the address input are replaced by the value on the Write data input.
MemtoReg	The value fed to the register Write data input comes from the ALU.	The value fed to the register Write data input comes from the data memory.




# Implementing Jumps

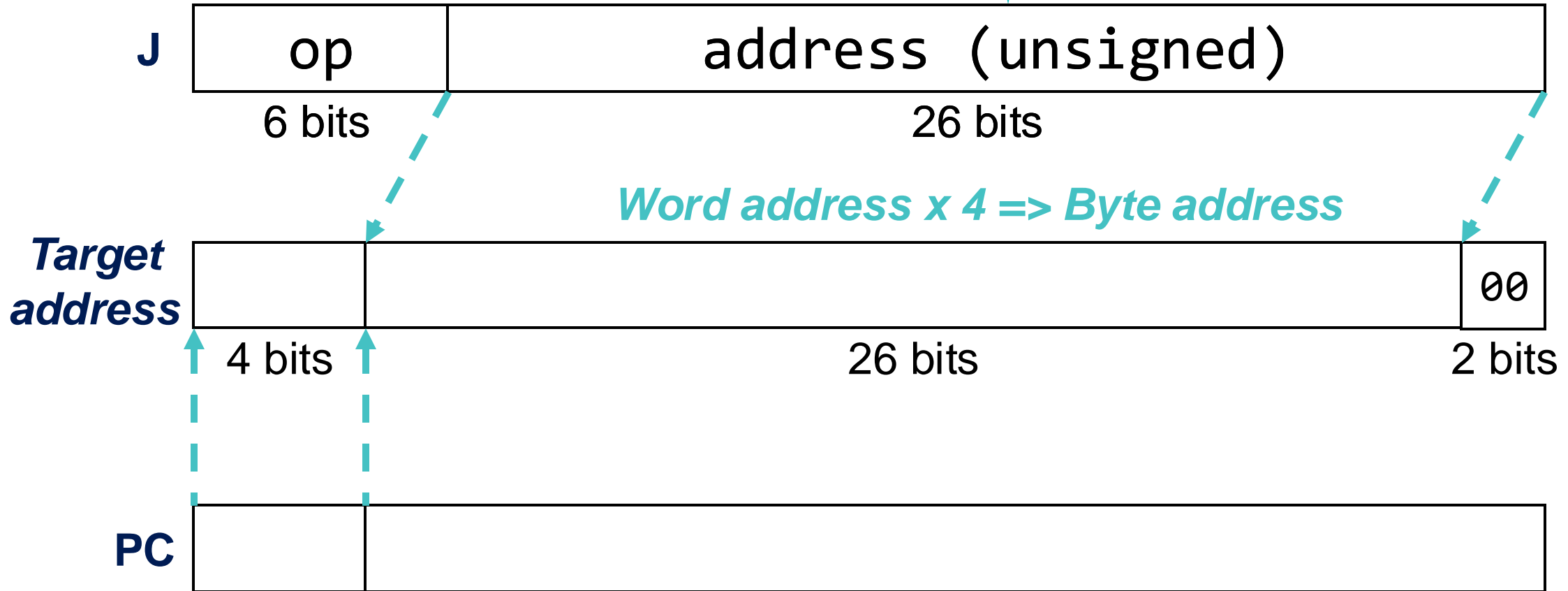

Need an **extra control signal** decoded from opcode


# Datapath with Jumps Added

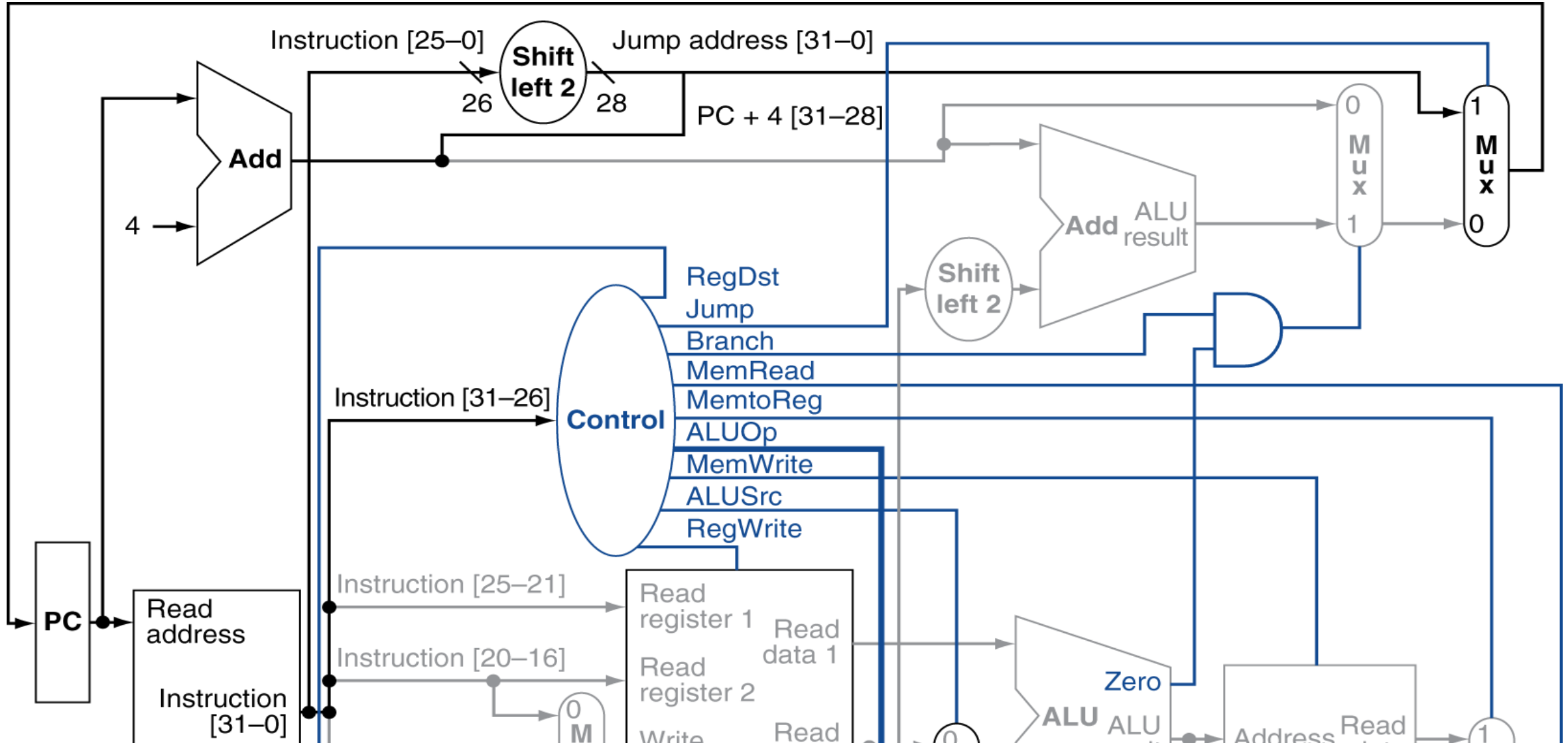

# Datapath with Jumps Added


Extra control signal:  
Jump

PC[31:28] && (address<<2)

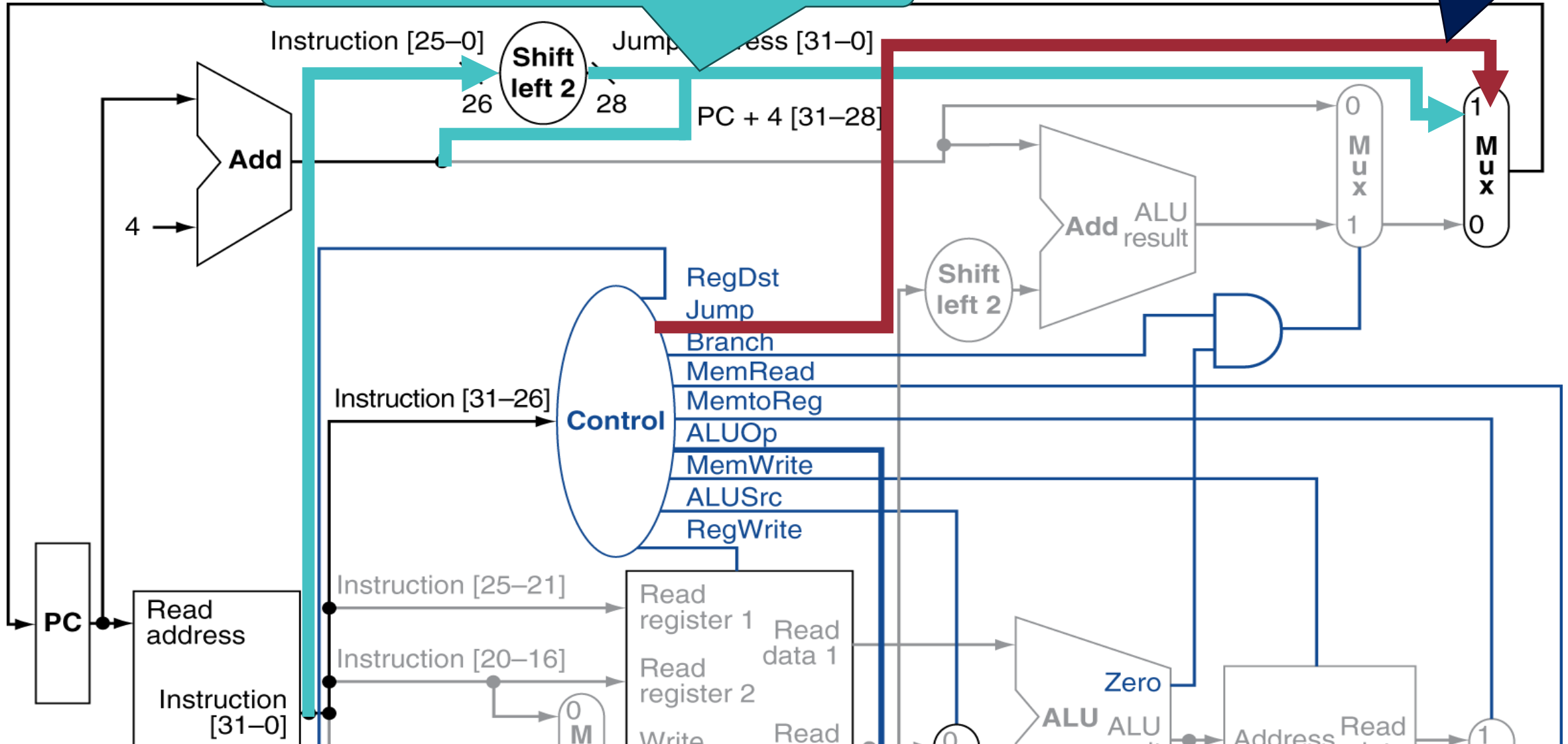

# Final Version of Single Cycle Datapath

48

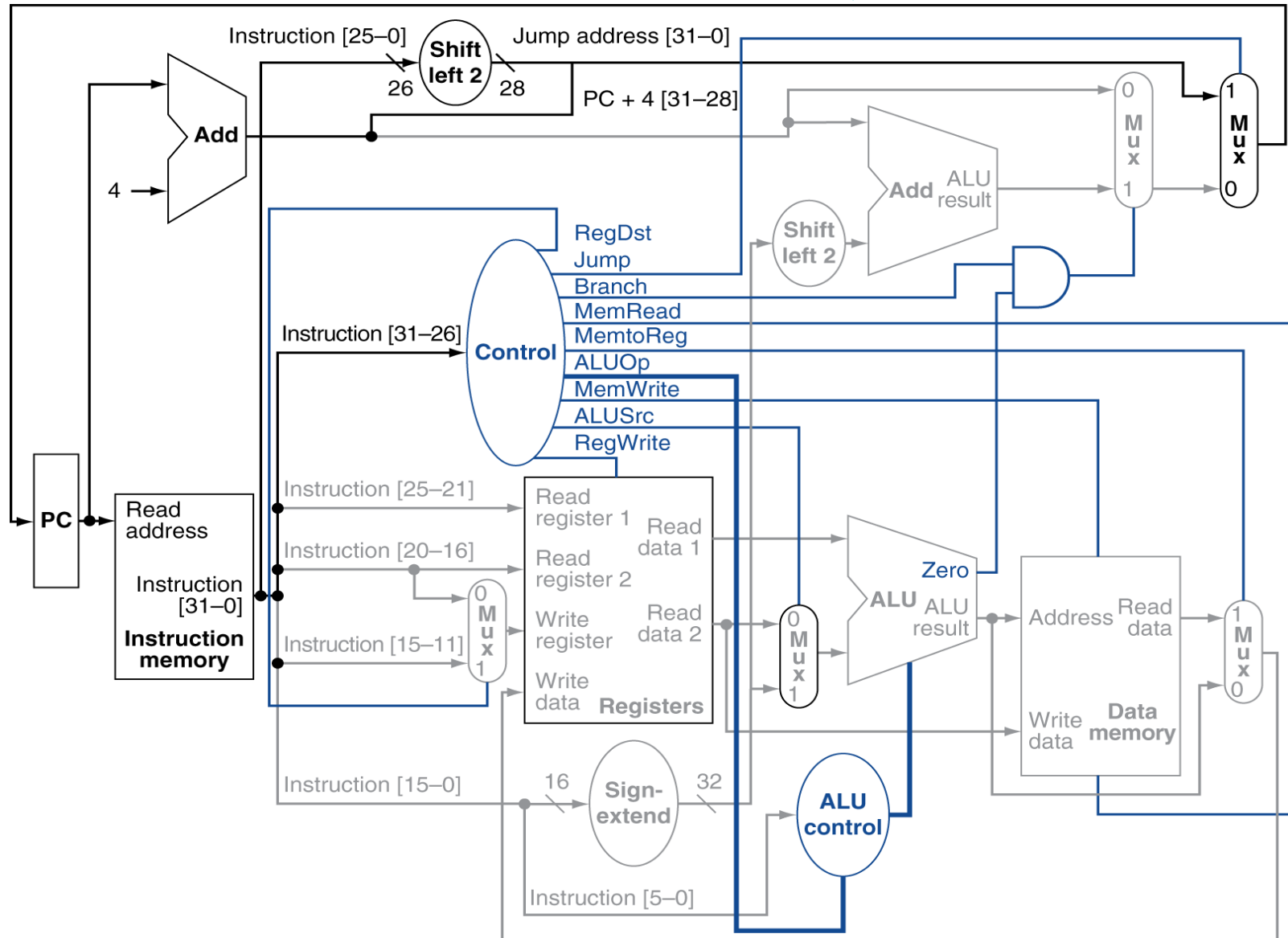


# Our Assumption: Single Cycle Datapath

49

We have considered a ***single clock cycle datapath***

 - Each instruction is executed in one clock cycle in the CPU




Let's look at the detailed scenario

# Our Assumption: Single Cycle Datapath


50

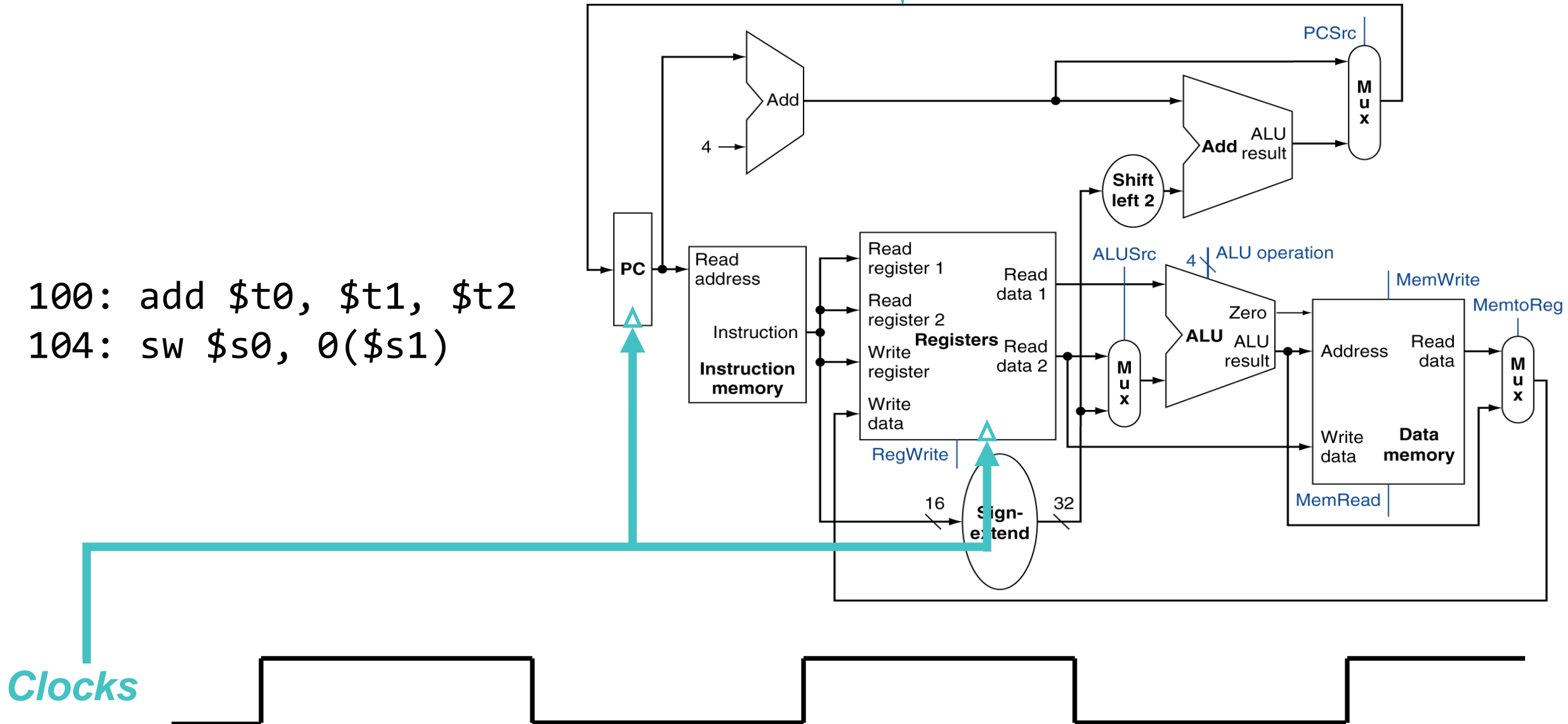100: add \$t0, \$t1, \$t2  
104: sw \$s0, 0(\$s1)



 **(Before Execution) add \$t0, \$t1, \$t2**

```
100: add $t0, $t1, $t2
104: sw $s0, 0($s1)
```




# (Execution) `add $t0, $t1, $t2`

100: `add $t0, $t1, $t2`  
 104: `sw $s0, 0($s1)`

Wait until all computations  
in the combinational circuit  
have settled down

Clocks

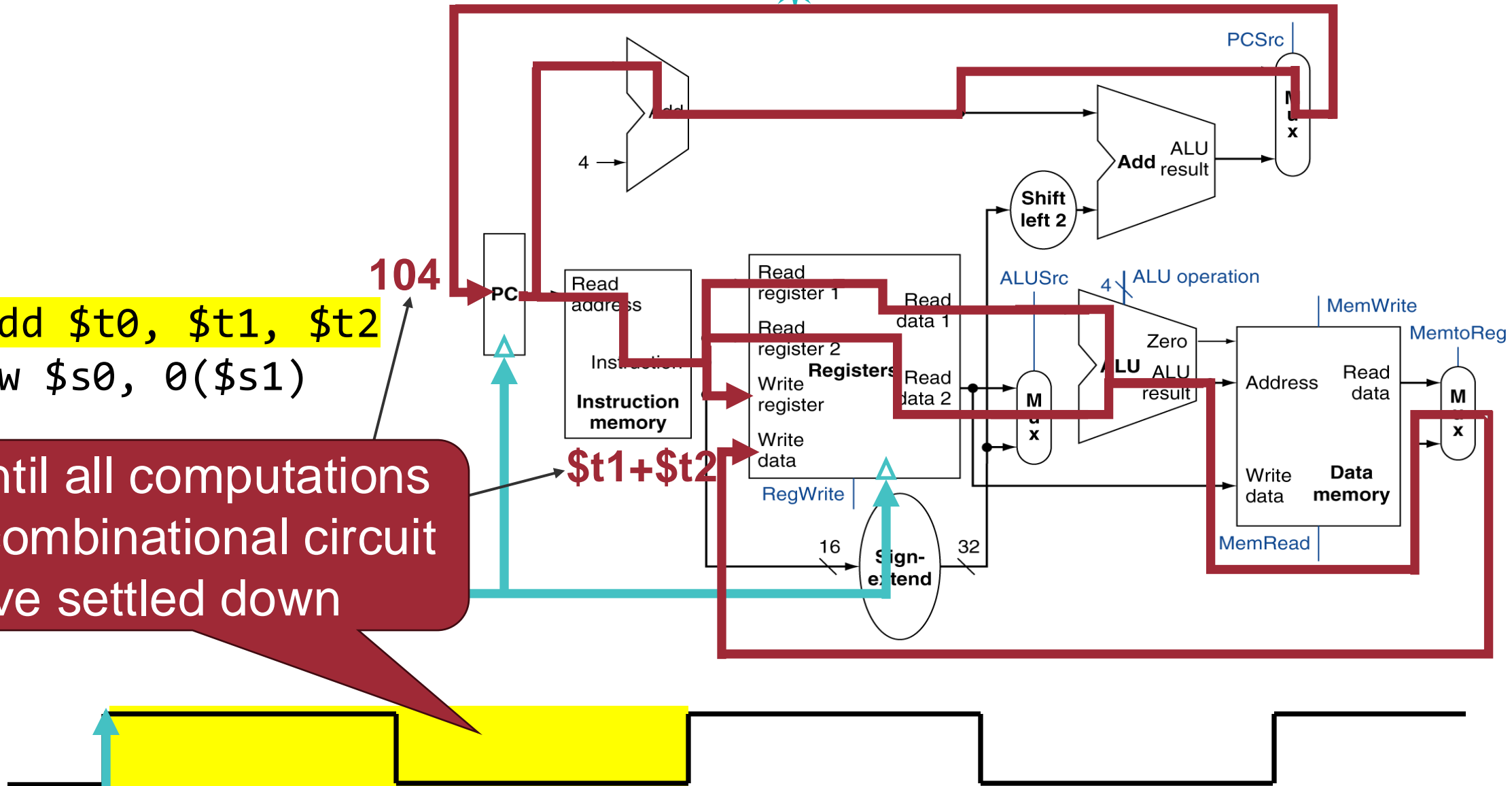





# (Before Execution) `sw $s0, 0($s1)`

53

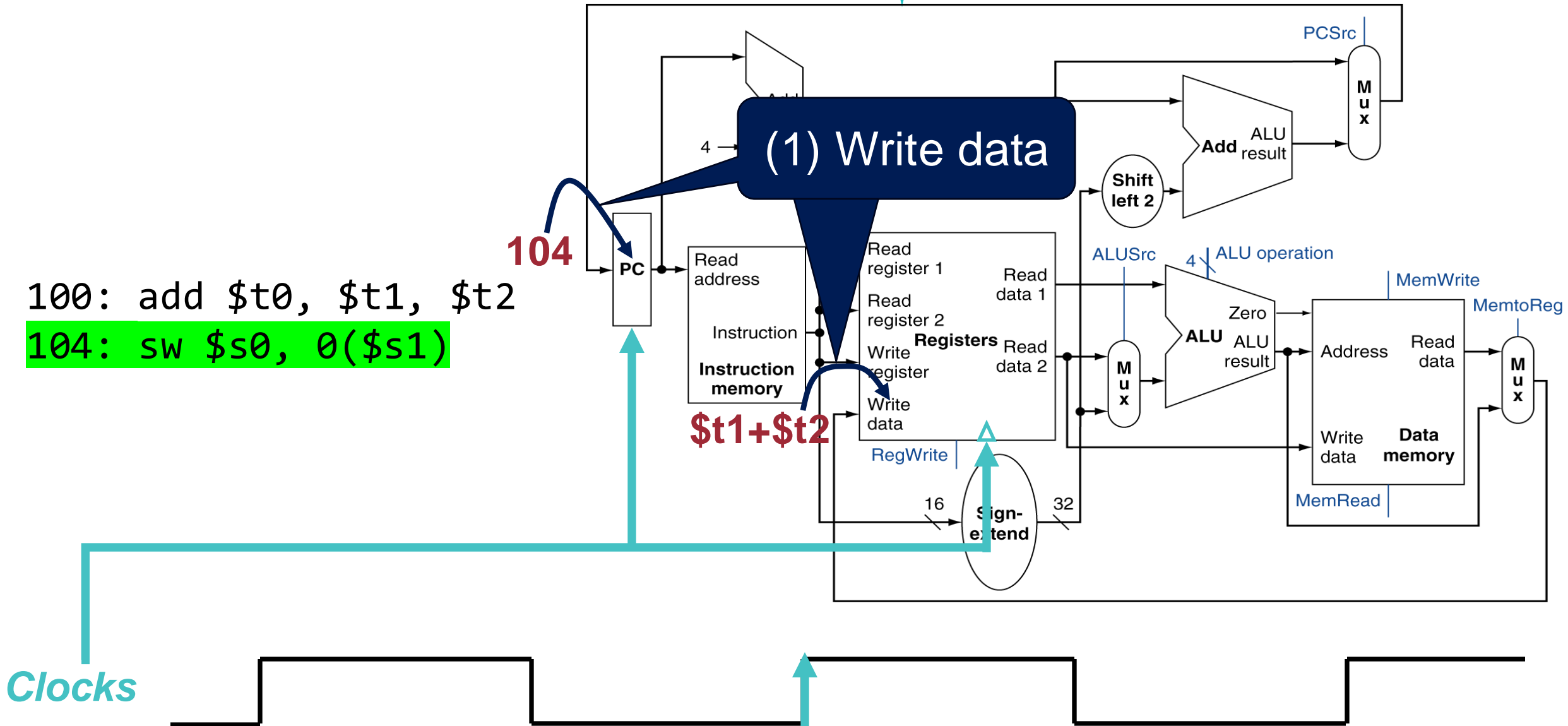100: add \$t0, \$t1, \$t2  
104: sw \$s0, 0(\$s1)




**(Before Execution)** `sw $s0, 0($s1)`

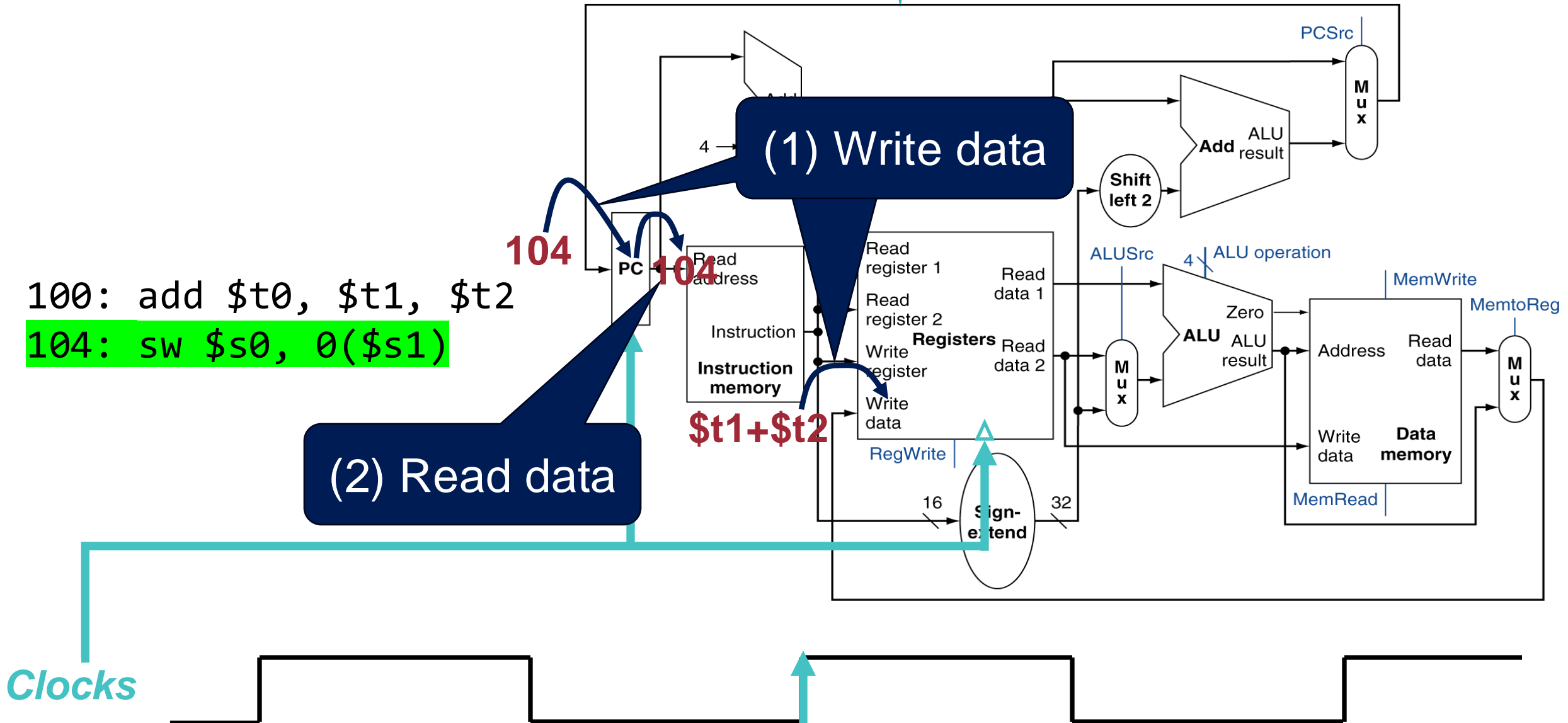

(Before Execution)

**sw \$s0, 0(\$s1)**


55

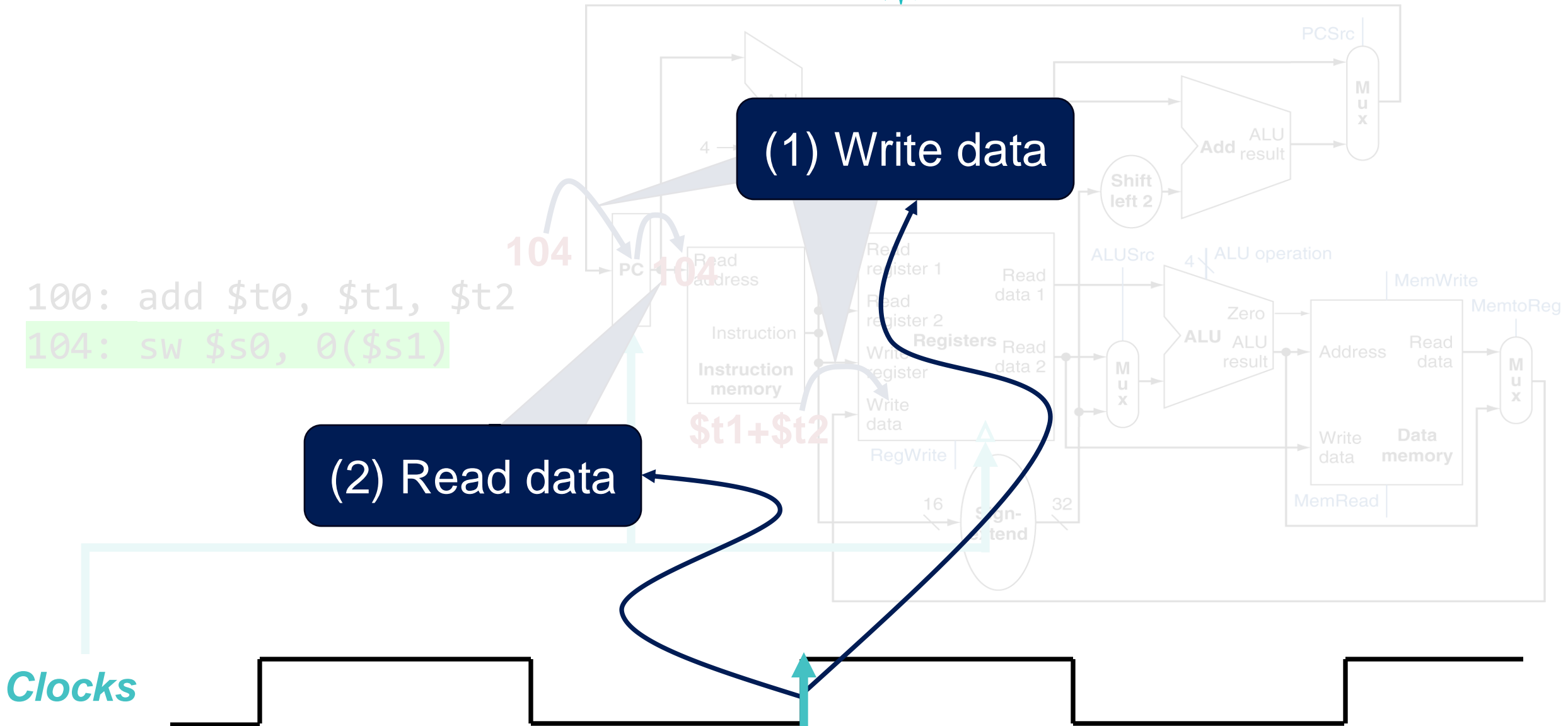

# Recap: Clocking Methodology Example


56

`addi $t5, $t1, 100`

 

# Discussion Points (1): Critical Path

57

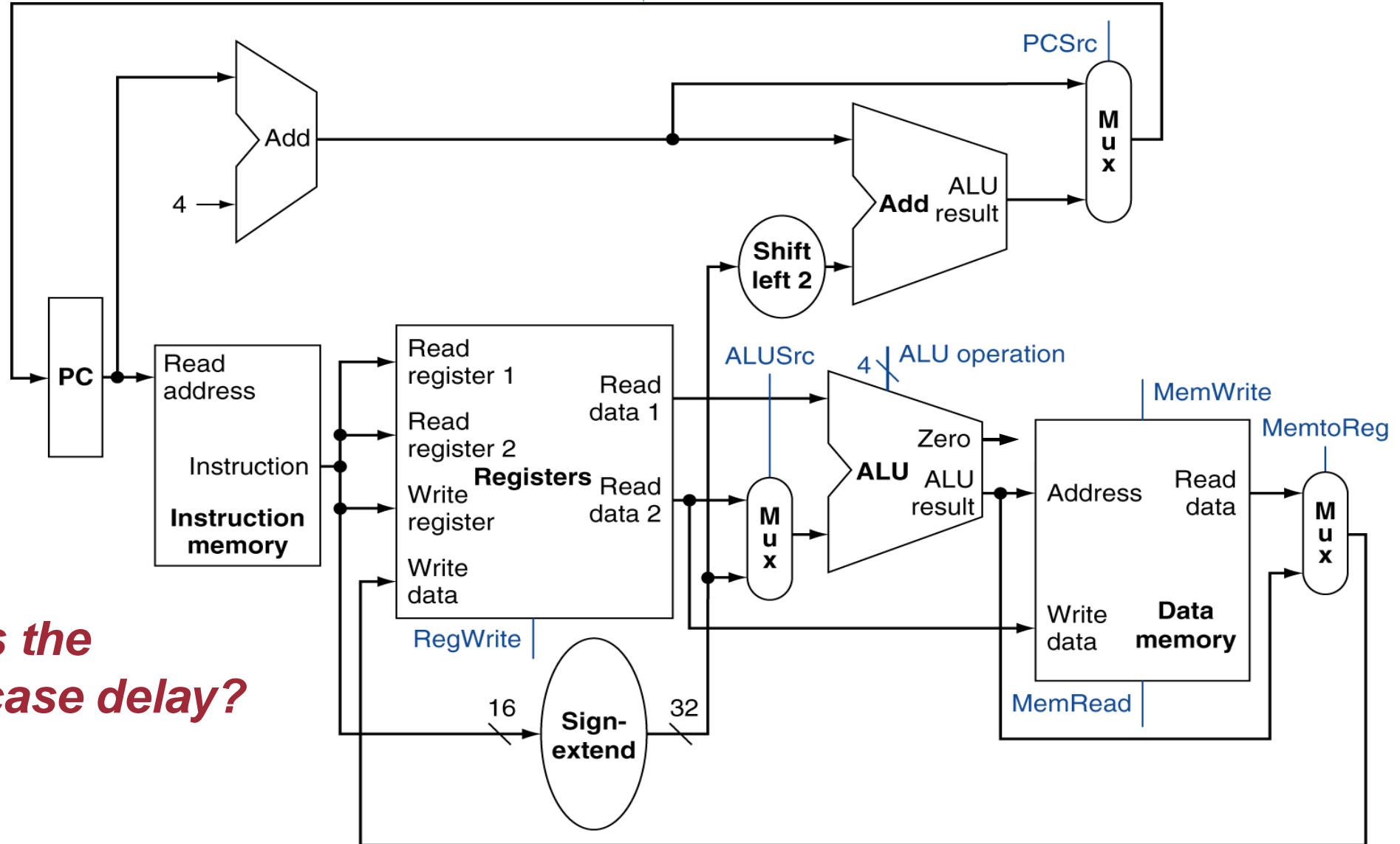

*What is the worst case delay?*

# Discussion Points (1): Critical Path

- Calculate cycle time assuming negligible delays except:
  - Memory access (200ps), ALU (100ps), Register access (50ps)

Instruction	Functional units used by the instruction class					
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back	
R-type	200ps	50ps	100ps		50ps	➔ 400ps
Load word	200ps	50ps	100ps	200ps	50ps	➔ 600ps
Store word	200ps	50ps	100ps	200ps		➔ 550ps
Conditional Branch	200ps	50ps	100ps			➔ 350ps
Jump	200ps					➔ 200ps

# Discussion Points (1): Critical Path

## Critical path!

The clock cycle time (period) with single clock will be determined by the longest instruction, which is 600ps

		decode	Execution	Access	Write-back	
R-type	200ps	50ps	100ps		50ps	→ 400ps
Load word	200ps	50ps	100ps	200ps	50ps	→ 600ps
Store word	200ps	50ps	100ps	200ps		→ 550ps
Conditional Branch	200ps	50ps	100ps			→ 350ps
Jump	200ps					→ 200ps

# Discussion Points (1): Critical Path

## Critical path!

The clock cycle time (period) with single clock will be determined by the longest instruction, which is 600ps

		decode	Execution	Access	Write-back	
R-type	200ps	50ps	100ps		50ps	→ 400ps
Load word	200ps	50ps	100ps	200ps	50ps	→ 600ps

CPI = 1

$$\begin{aligned}
 \text{Execution Time} &= \text{Instruction \#} * \text{CPI} * \text{Clock Cycle Time} \\
 &= \text{Instruction \#} * 600\text{ps}
 \end{aligned}$$



# Limitation of a Single-Cycle Datapath

- Clock Cycle Time = 600ps

Even though it could finish early, it has to wait for 600ps

Instruction	Functional units used by the instruction				
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back
R-type	200ps	50ps	100ps		50ps
Load word	200ps	50ps	100ps	200ps	50ps
Store word	200ps	50ps	100ps	200ps	
Conditional Branch	200ps	50ps	100ps		
Jump	200ps				

# Limitation of a Single-Cycle Datapath

- Clock Cycle Time = 600ps


Even though it could finish early, it has to wait for 600ps

Instruction	Functional units used by the instruction				
	Instruction fetch	Instruction decode	Execution	Memory Access	Register Write-back
R-type	200ps	50ps	100ps		50ps
Load word	200ps	50ps	100ps	200ps	50ps
Store word	200ps	50ps	100ps	200ps	

## *Why a Single-Cycle Implementation is Not Used Today?*

Although the CPI is 1, the overall performance of a single-cycle implementation is likely to be poor, since the clock cycle is too long.
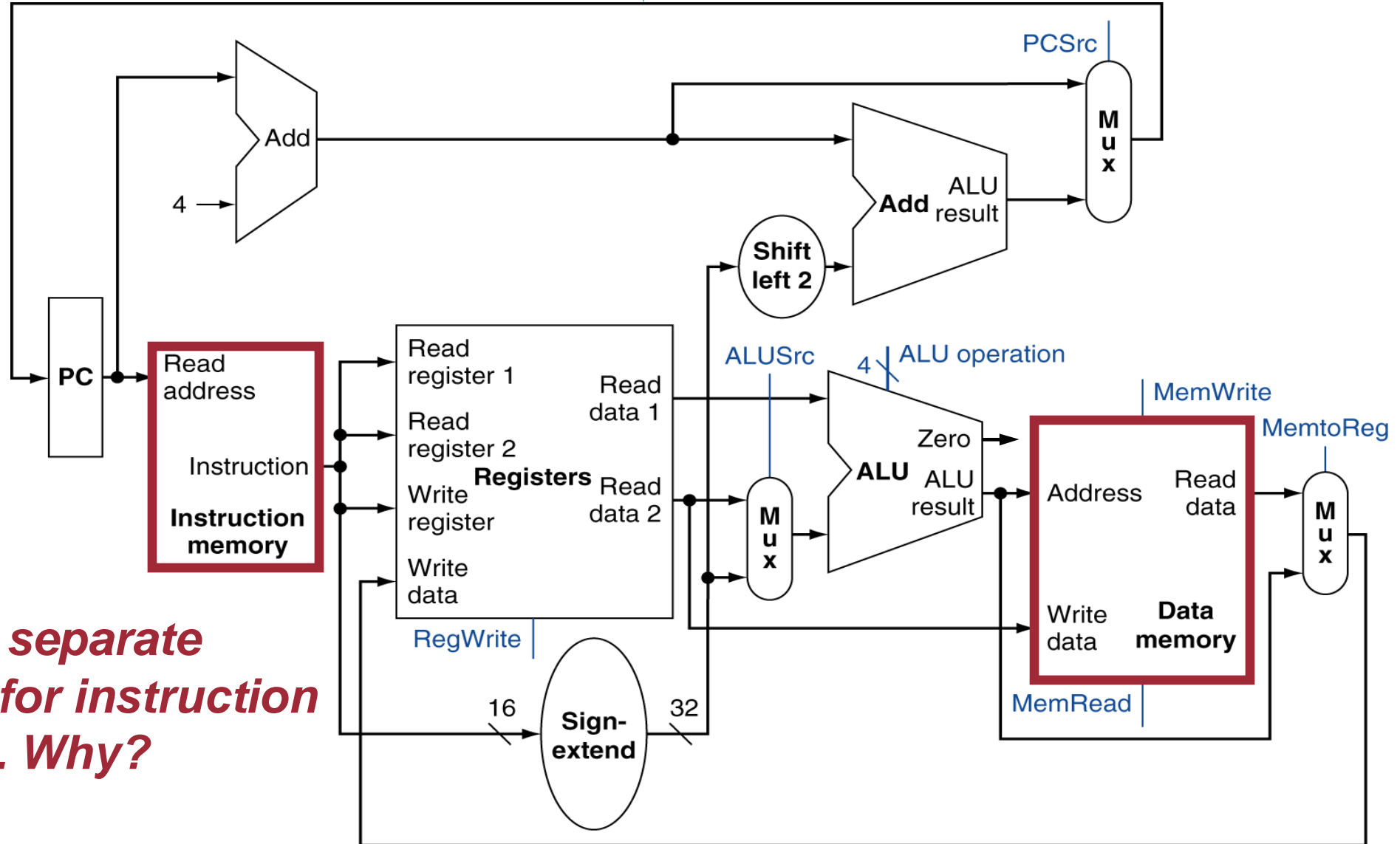
# Discussion Points (2): Memory Separation<sup>63</sup>



*We need separate memory for instruction and data. Why?*



# Discussion Points (2): Memory Separation

64



- Why do we need a memory for instructions separate from one for data?
  - No datapath resource can be ***used more than once per instruction***, so any element needed more than once must be duplicated

**Question?**