

CSE261: Computer Architecture

8. Logic Design Basics

Seongil Wi

The Score for HW1 will be Announced Soon



We discovered that several students committed plagiarism

Recap: Academic Integrity


- DO NOT share the course contents (e.g., assignments or exams) with others
 - E.g., Github public repository, chegg.com, etc
- DO NOT discuss the **details of solutions** with others
- DO NOT plagiarize
 - Submit your own work
- Any integrity violation: at **LEAST F**

UNIST CSE Policy on Cheating and Plagiarism


Note: The term **solution** means program code, mathematical derivation, experimental setup, etc., for any type of deliverable, homework assignment, or projects in class.

The purpose of this document is to make our expectations in CSE as clear as possible in regard to the Honor Code at UNIST. The basic principle under which we operate is that each of you is expected to **submit your own work in your courses**. In particular, attempting to take credit for someone else's work by turning it in as your own constitutes plagiarism, which is a serious violation of fundamental academic standards. However, you are also encouraged to work as a team and collaborate with each other, and it is usually appropriate to ask others—the TA, the instructor, or other students—for direction and debugging help or to talk generally about

Where Are We?

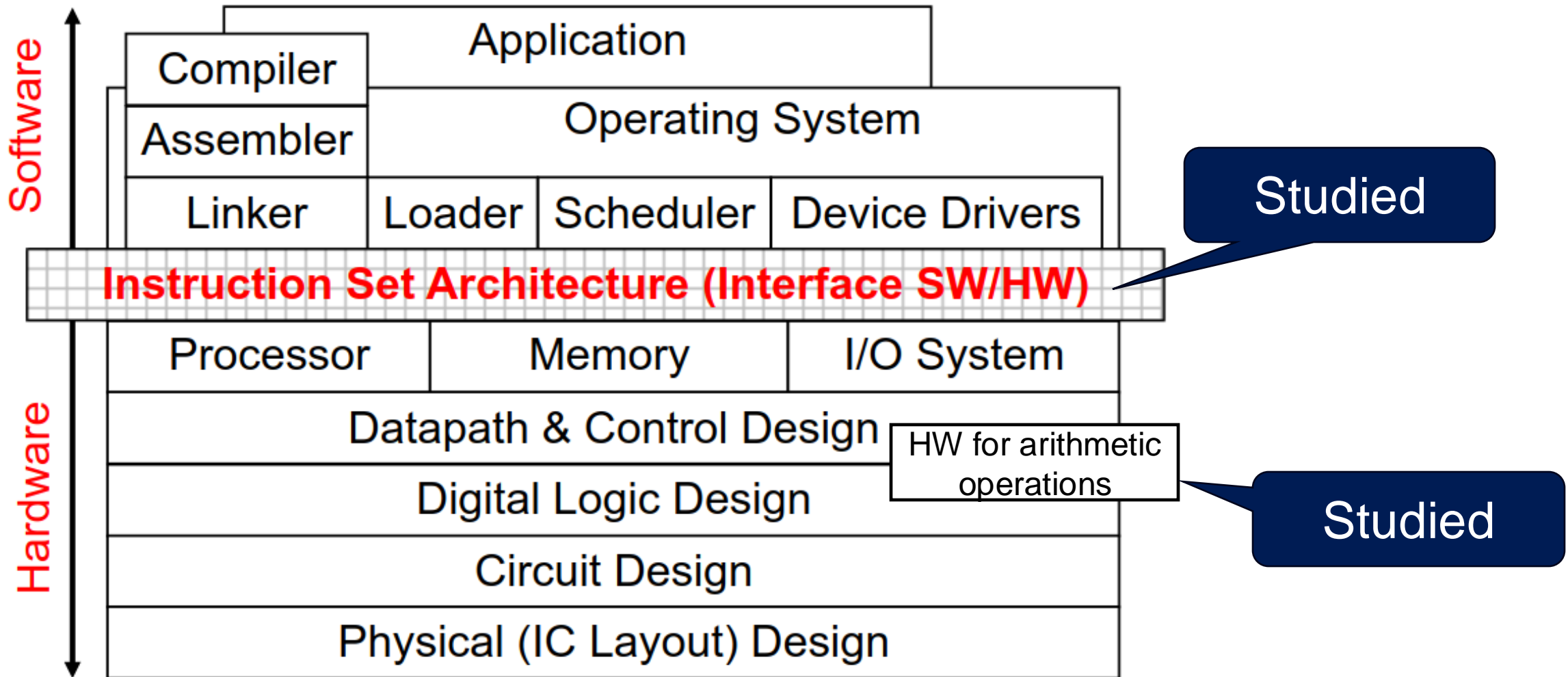

Today's Topic

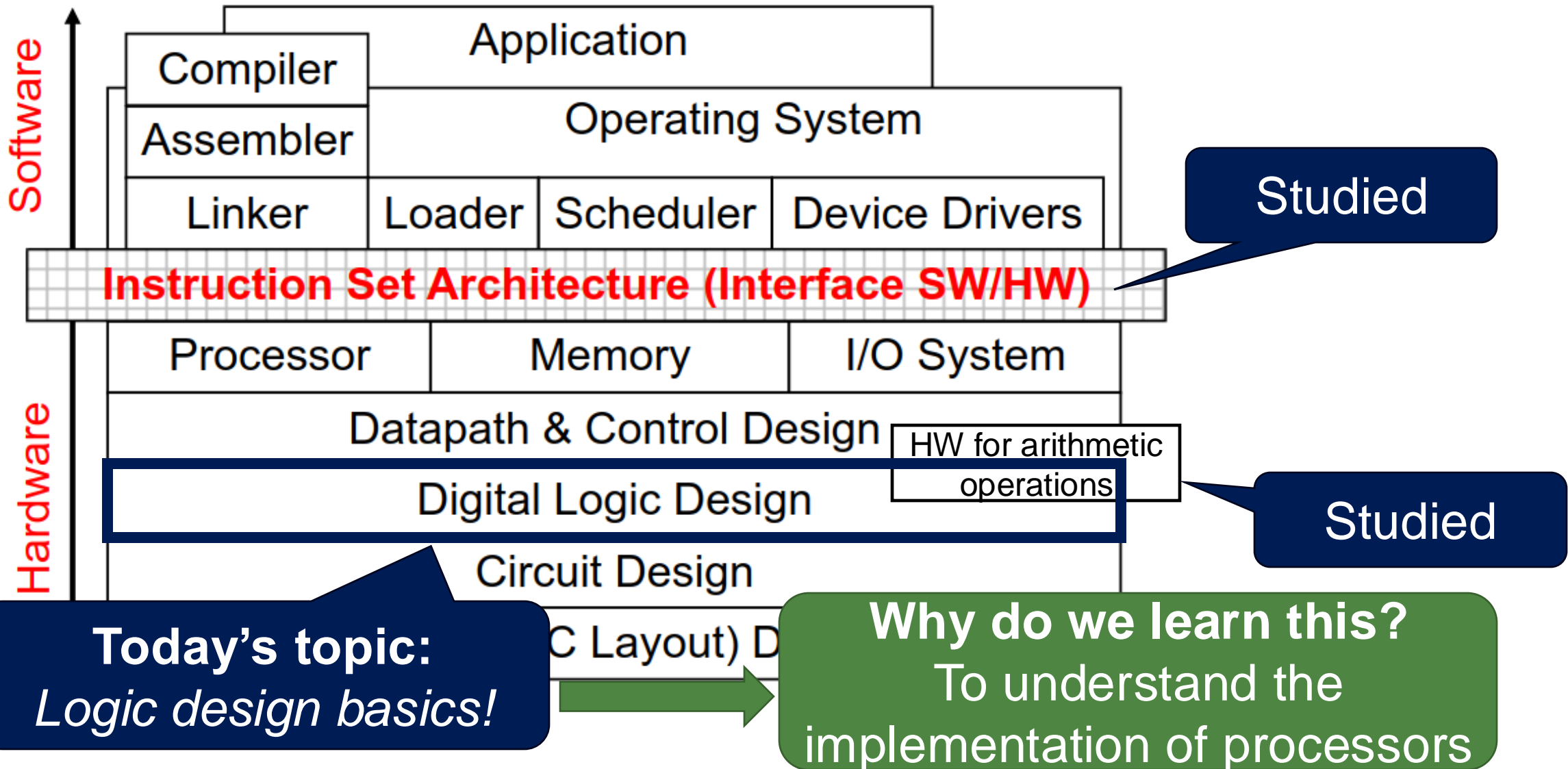

Logic Design




Basic organization of the circuitry of a digital computer

Logic Design Basics



 - Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses



One wire per bit

Two Types of Logic Circuits



- **Combinational circuit**
- **Sequential circuit**

Two Types of Logic Circuits


- **Combinational circuit**

- Outputs only depends on the current inputs



- **Sequential circuit**

Combinational Logic Circuits

 

Input		Output
a	b	
0	0	0
0	1	0
1	0	0
1	1	1

Outputs only depends on the current inputs

Combinational Circuits: AND, OR, NOT

11

AND




Input		Output
a	b	
0	0	0
0	1	0
1	0	0
1	1	1

OR



Input		Output
a	b	
0	0	0
0	1	1
1	0	1
1	1	1


NOT

 

Input	Output
0	1
1	0

Basic blocks for creating
combinational circuits

Combinational Circuits: NAND

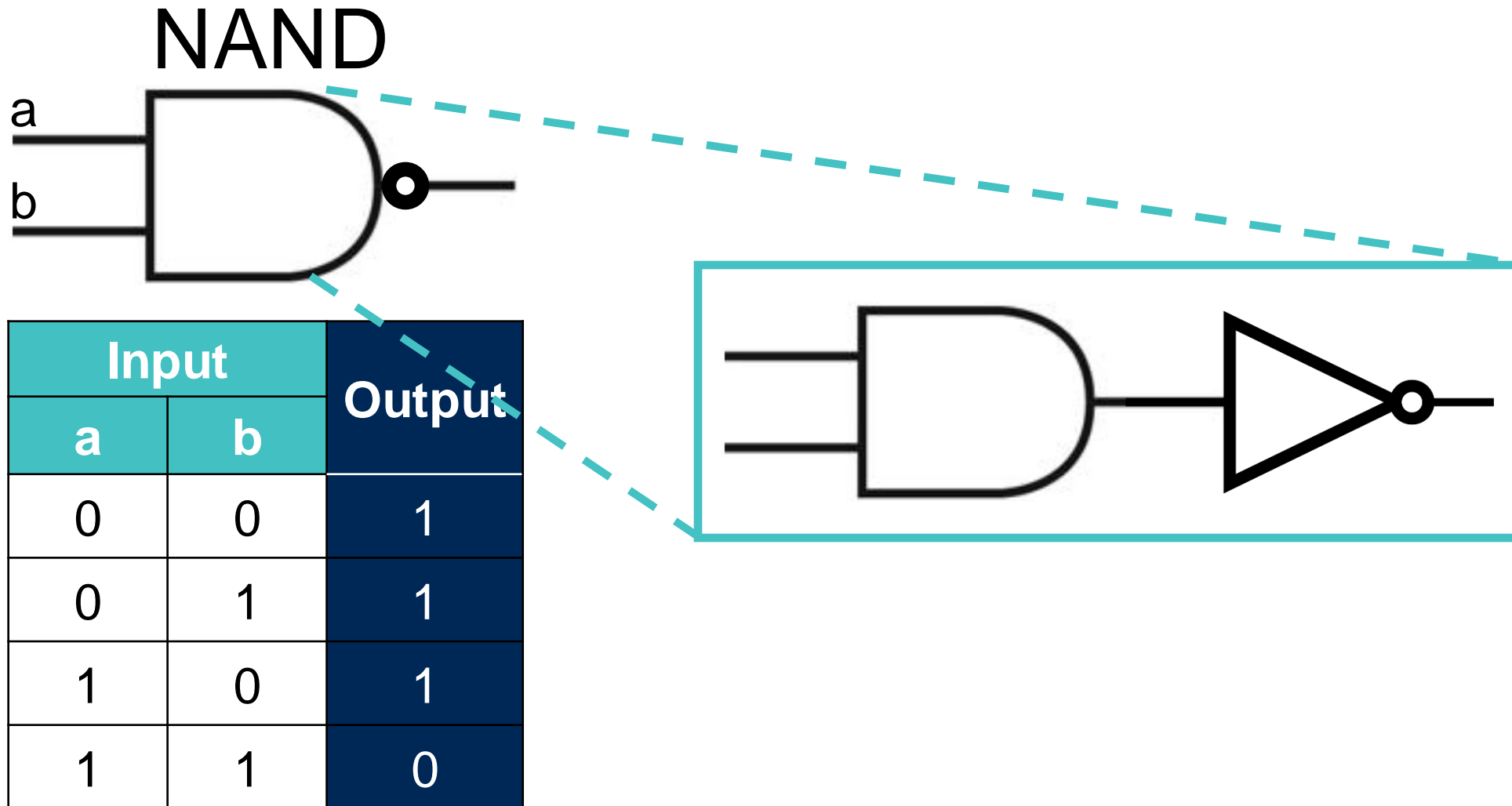

Combinational Circuits: NOR

13

NAND




Input		Output
a	b	
0	0	1
0	1	1
1	0	1
1	1	0



NOR



Input		Output
a	b	
0	0	1
0	1	0
1	0	0
1	1	0

 

Combinational Circuits: XOR

  



0	0	1
0	1	1
1	0	1
1	1	0

0	0	1
0	1	0
1	0	0
1	1	0

Input		Output
a	b	
0	0	0
0	1	1
1	0	1
1	1	0

Combinational Circuits: Adder

Adder

  


Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Combinational Circuits: Multiplexor

16

Multiplexor
(a.k.a., MUX)

 


Input	Output
S	
0	A's Input
1	B's Input

Combinational Circuits: Multiplexor

17


Multiplexor
(a.k.a., MUX)

 

Input	Output
S	
0	A's Input
1	B's Input

Combinational Circuits: Multiplexor


Multiplexor
(a.k.a., MUX)

 

Input	Output
S	
0	A's Input
1	B's Input

Combinational Circuits: Decoder

Decoder

 


Input		Output			
A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Combinational Circuits: Decoder

20

Decoder

 

Input		Output			
A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

 

Two Types of Logic Elements

- **Combinational circuit**

- Outputs only depends on the current inputs



- **Sequential circuit**

- Outputs depends on the current inputs and current state

Two Types of Logic Elements


- **Combinational circuit**

- Outputs only depends on the current inputs



- **Sequential circuit**

 - Outputs depends on the current inputs and current state




Sequential Circuit



- **Sequential circuit**

 - Outputs depends on the current inputs and current state




Sequential Circuit: Example

```
addi $t1, $t1, 100
```

- **Sequential circuit**

 - Outputs depends on the current inputs and current state




Sequential Circuit: Example

`addi $t1, $t1, 100`


- **Sequential circuit**

 - Outputs depends on the current inputs and current state



Sequential Circuit: Final View


26

 

Motivation: Clocks




 Q. When should an element that contains state be updated?




CPU Clocking

 
- Operation of digital hardware governed by a constant-rate clock




Motivation: D-Latch and D Flip-flop

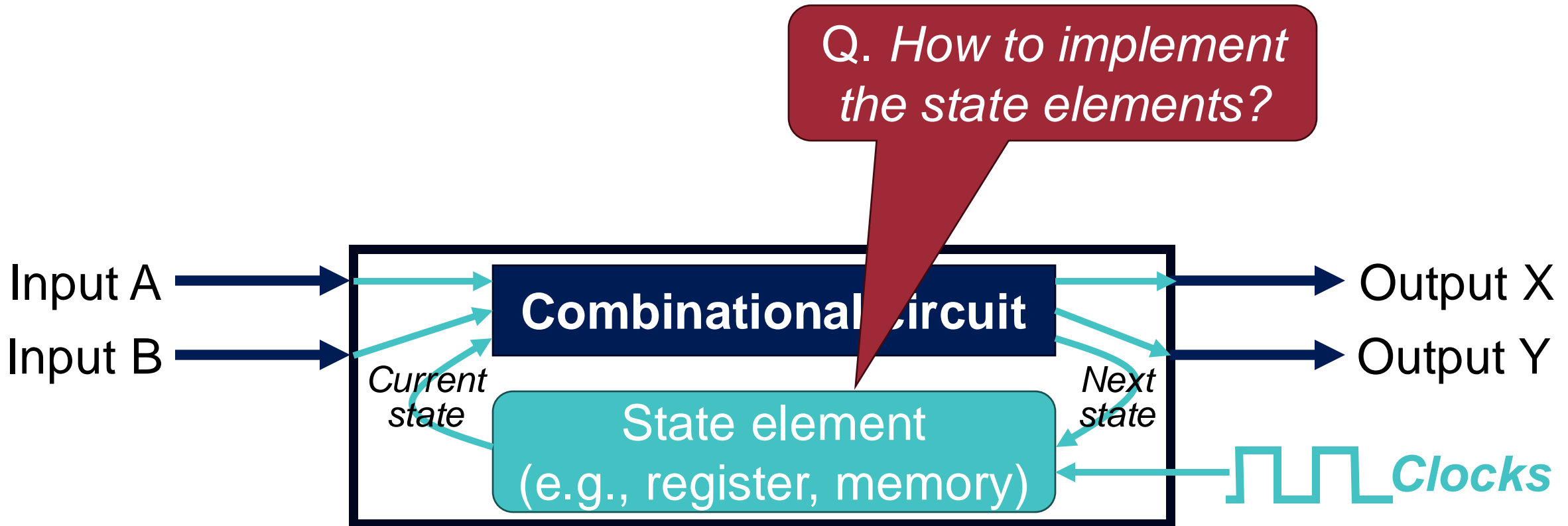


State Element #1: D-Latch

 


State Element #1: D-Latch

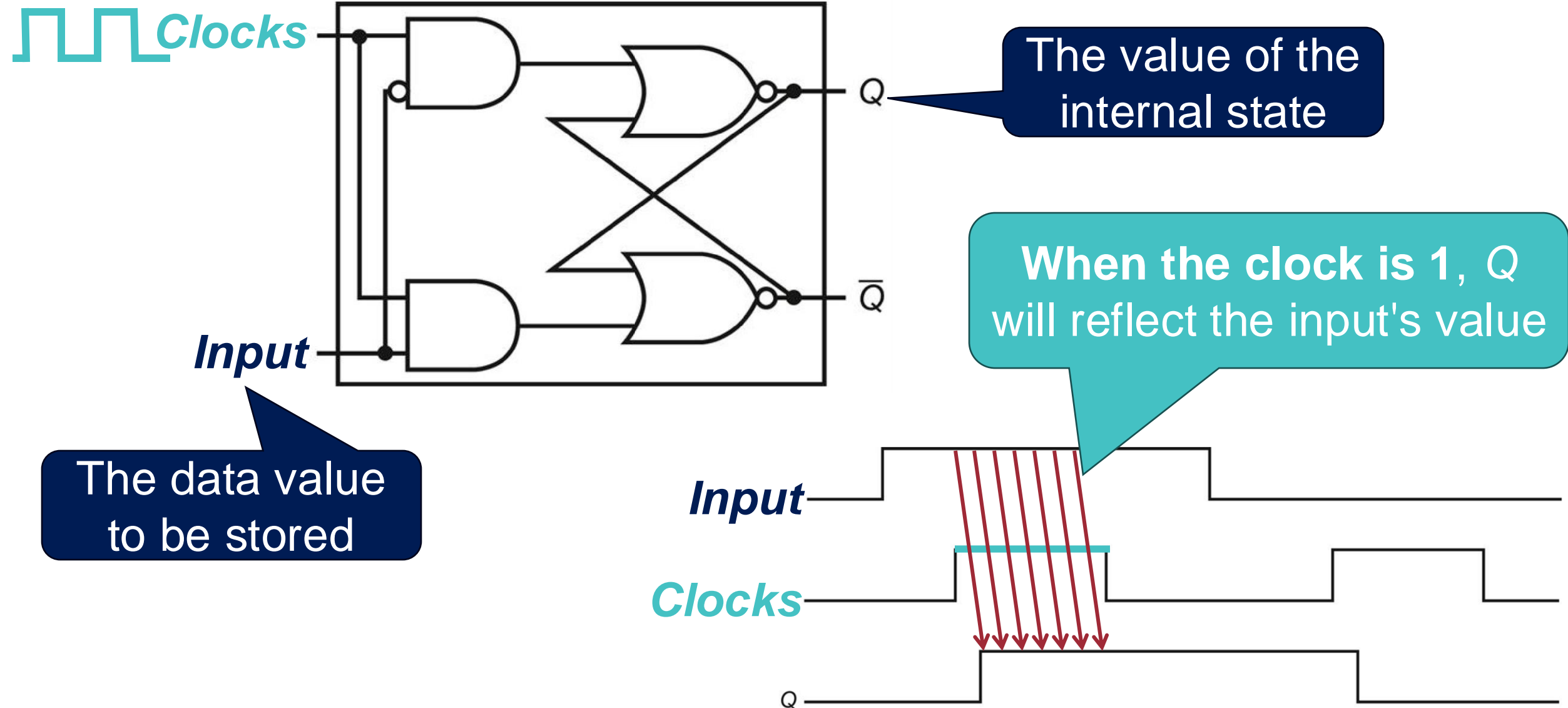

State Element #1: D-Latch


 


State Element #1: D-Latch

 


State Element #2: D Flip-flop

  - Output changes ***only on the clock edge***




State Element #2: D Flip-flop

 - Output changes **only on the clock edge**



 Output changes **only on the rising edge**




This Course



We consider about ***rising-edge triggered D flip-flop***

Clocking Methodology in Sequential Circuit


37

 

Clocking Methodology Example

38


`addi $t5, $t1, 100`

 

Clocking Methodology Example

39


`addi $t5, $t1, 100`

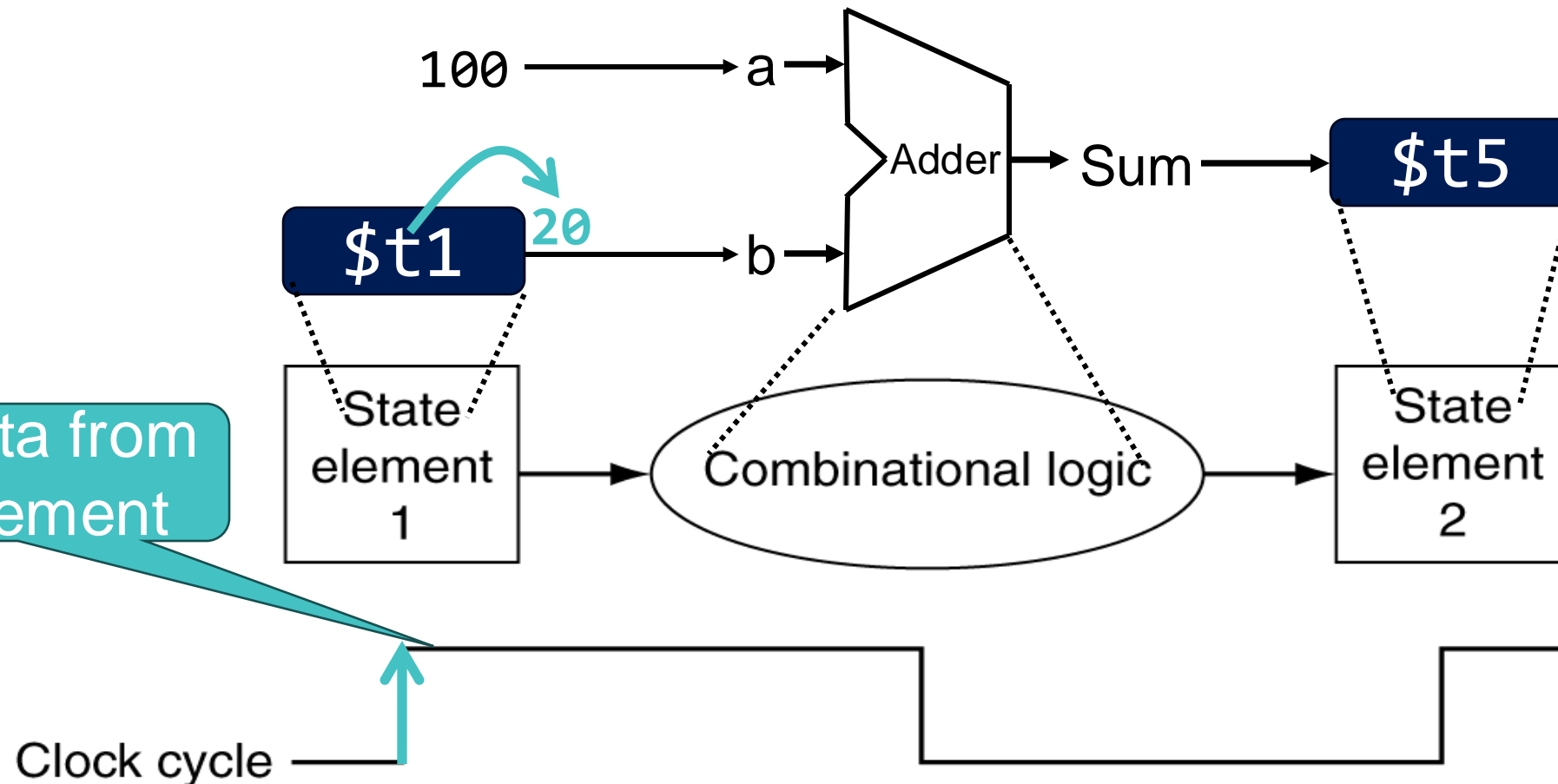

Clocking Methodology Example

40


`addi $t5, $t1, 100`

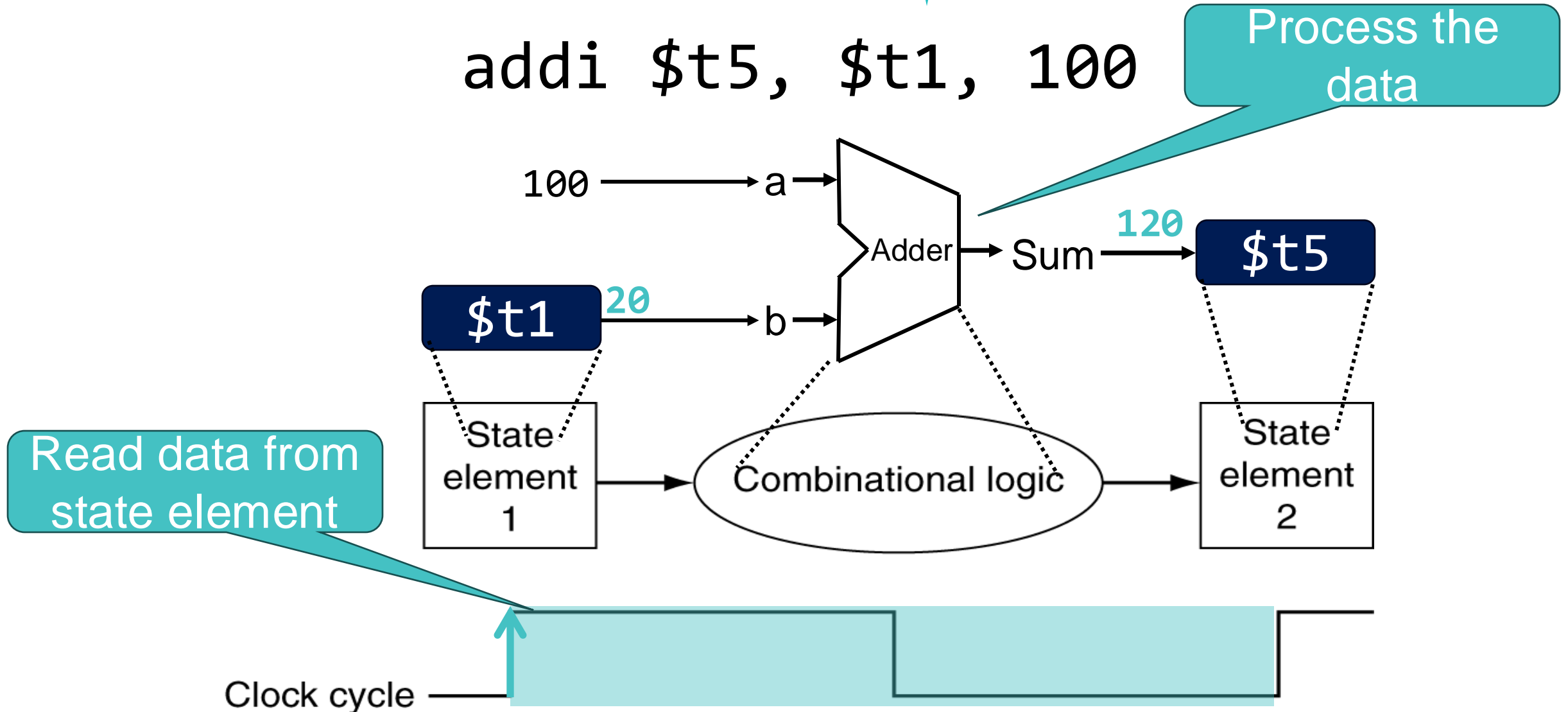

Clocking Methodology Example


41

`addi $t5, $t1, 100`

 


Clocking Methodology Summary

42

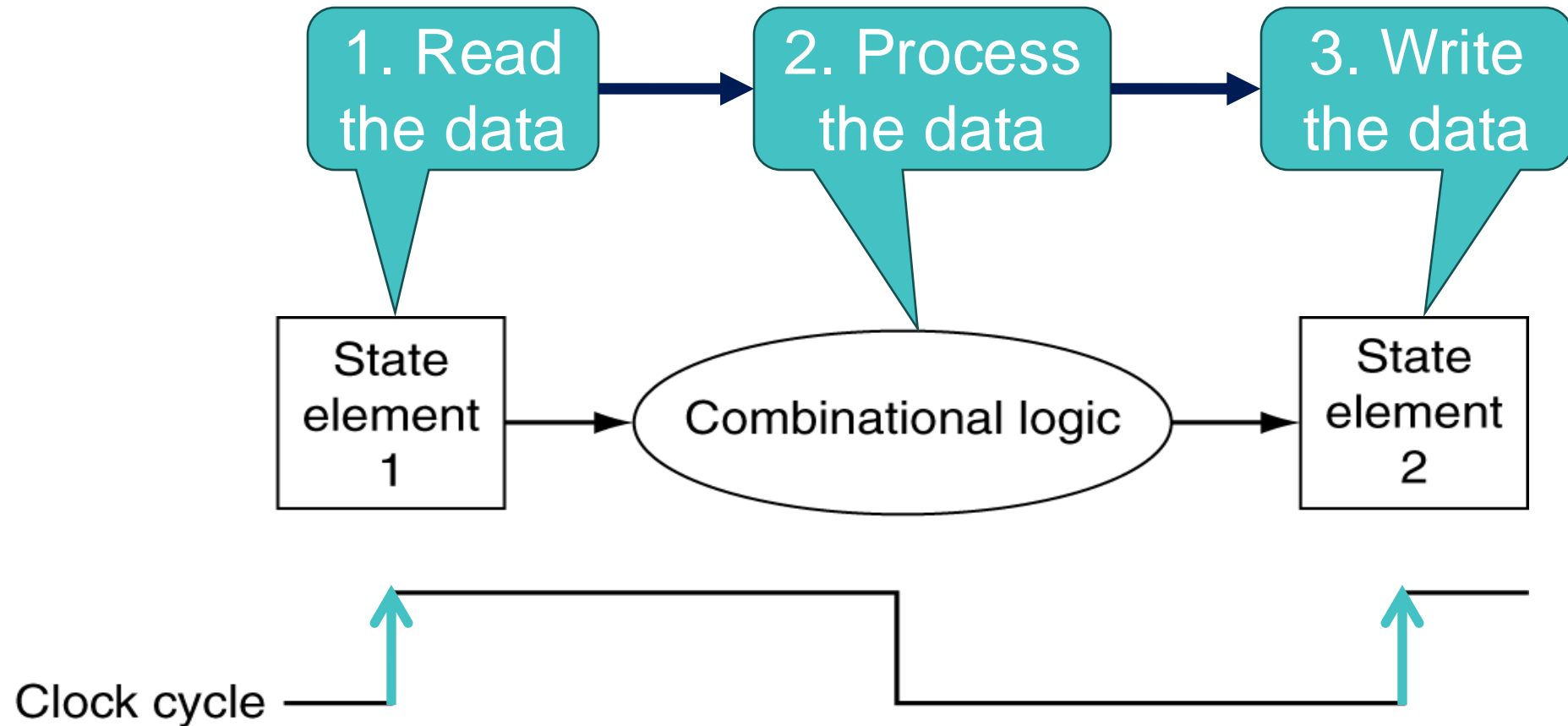

Critical Path


43

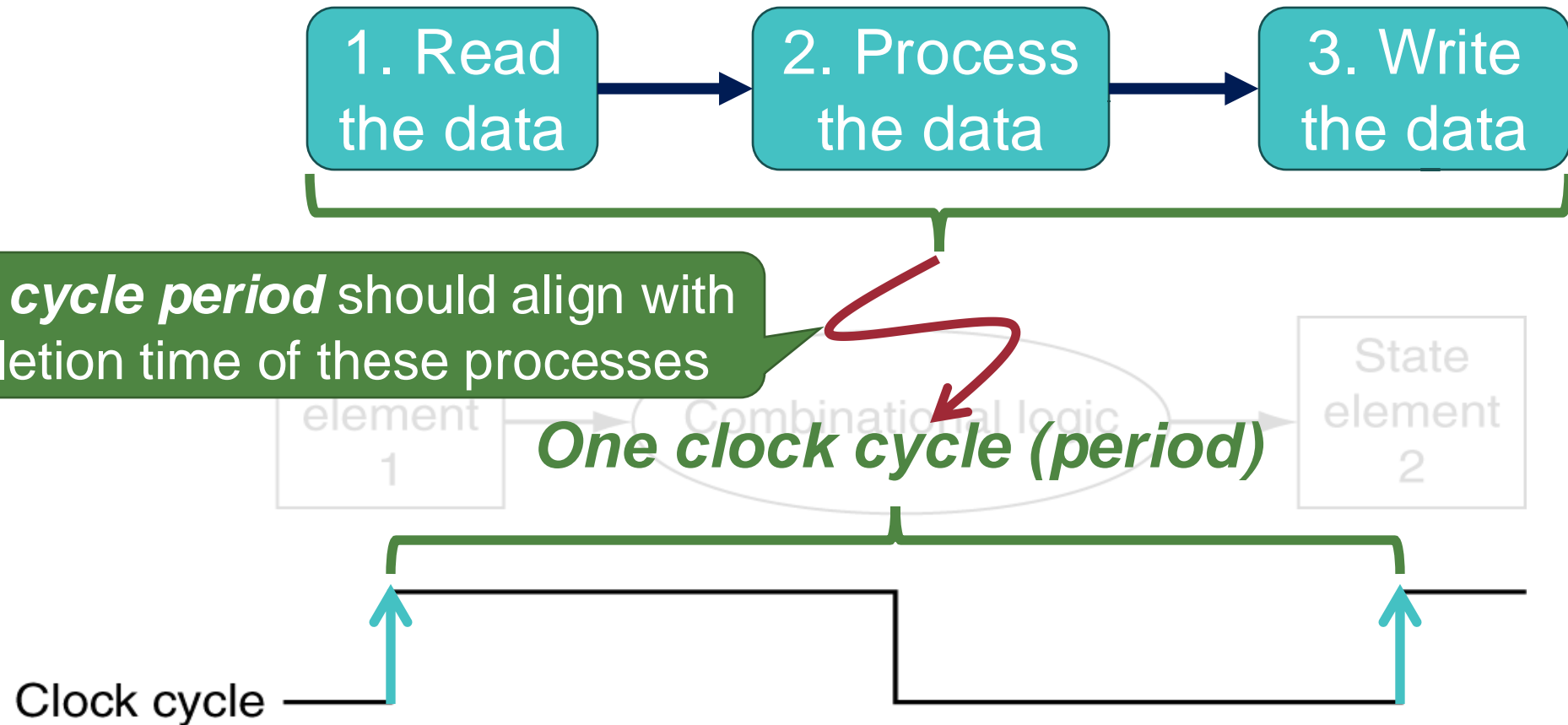

Critical Path


44

 The bottleneck to increase the clock frequency more!



The *clock cycle period* should align with the completion time of these processes

One clock cycle (period)

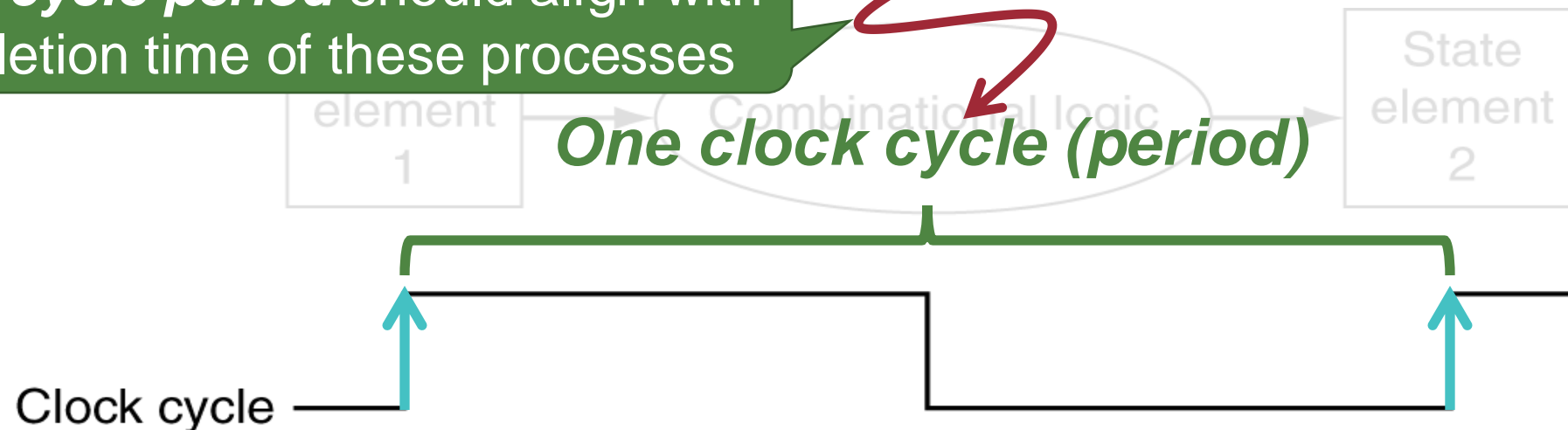

Critical Path



- The clock cycle period is fixed by **the longest delay (= Critical Path)**
- CPU designers analyze the paths to ensure that all operations can complete within a single clock cycle

Summary


- **Combinational circuit**

- Outputs only depends on the current inputs



- **Sequential circuit**

 - Outputs depends on the current inputs and current state



Summary


- **Combinational circuit**

- Outputs only depends on the current inputs

Mainly used for data operations



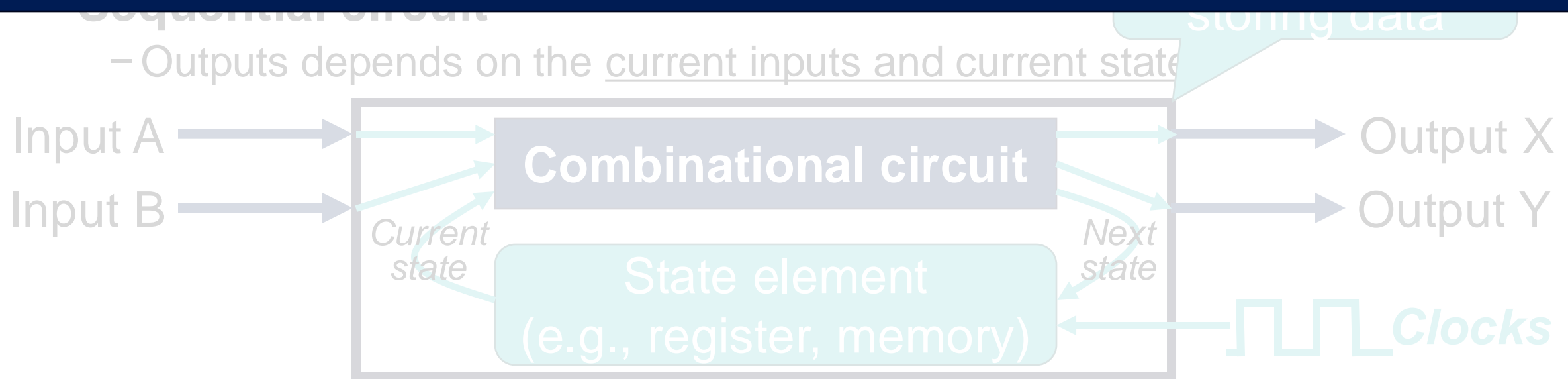For more details, refer to the
EEE202: Digital Logic and Laboratory course!



Question?